

Chaper 1

P1.3-1 3.5 nC

P1.3-3 3.204 nA

P1.5-1 (a) A and D, (b) B and C, (c) 60mW, (d) -60mW, (e) 60mW

P1.7-3 The reference direction of the resistor between node b and d has been reversed.

Chaper 2

P2.4-5 $i_1=4A$, $i_2=-8A$, R_1 absorbs 800W and R_2 absorbs 1600W.

P2.4-6 $V_1=-0.4V$, $V_2=0.8V$, R_1 absorbs 20mW, R_2 absorbs 40mW.

P2.6-5 (a) $V_R=165A$
(b) 30Ω resistor supplies -750W,
5A current source supplies 825W,
15V voltage source supplies -75W

P2.6-6 (The resistor changes to 30Ω , the voltage source changes 15V)

(a) $i_R=-1.5A$
(b) 30Ω resistor supplies -7.5W,
2A current source supplies 30W,
15V voltage source supplies -22.5W

P2.6-7 $V_b = 5V$

Chapter 3

- P3.2-4 The $5\ \Omega$ resistor absorbs 80W,
the $6\ \Omega$ resistor absorbs 24W,
the $9\ \Omega$ resistor absorbs 81W.
- P3.2-6 The 4mA current source supplies -8mW,
the 2mA current source supplies 20mW.
- P3.2-14 (The answer is dependent on the reference directions that one chooses.)
The $10\ \Omega$ resistor on the top: $i_1=-1.5A$, $V_1=-15V$
The $10\ \Omega$ resistor in the middle: $i_5=1A$, $V_5=10V$
The $10\ \Omega$ resistor on the bottom: $i_8=-0.5A$, $V_5=-5V$
The $25\ \Omega$ resistor on the left: $i_4=-0.4A$, $V_4=-10V$
The 5V voltage source: $i_4=1.1A$
The 15V voltage source: $i_6=0.1A$
The 1.5A current source: $i_3=20V$
The 0.5A current source: $i_7=10V$
- P3.2-27 $V_6=-12V$
- P3.3-4 $V=-8V$
- P3.6-1 (a) $R=64\ \Omega$,
(b) $i=1/2A$, $V=32V$,
(c) $i=1/3A$.
- P3.6-4 (a) $R_1=12\ \Omega$, $R_2=8\ \Omega$,
(b) $i_a=3A$, $i_b=2.25A$,
(c) $i_2=1.125A$, $V_1=-20V$

Chapter 4

P4.2-4 $R_1=250 \Omega$, $R_2=500 \Omega$.

P4.3-6 (a) $R=12k\Omega$, (b) $1.4V$.

P4.4-8 The power supplied by the dependent source is $1.04W$.

P4.4-23 $V_1=88V$, $V_2=-40V$, $V_3=-16V$.

P4.5-4 $i_a=-5.4mA$, $i_b=-7.8mA$

P4.5-6 (a) The power supplied by $12V$ source is $0.48W$;
the power supplied by $8V$ source is $0.32W$.
(b) The power absorbed by the 30Ω resistor is $0.048W$.


P4.6-4 $V_c=-7.95V$

P4.7-12 $i_x = -0.29 A$ [corrected 2013-02-12; previously had $0.146A$]

P4.11-5 The mesh currents are not correct.

Chaper 5

5.5-2 $I_a=2 \text{ A}$

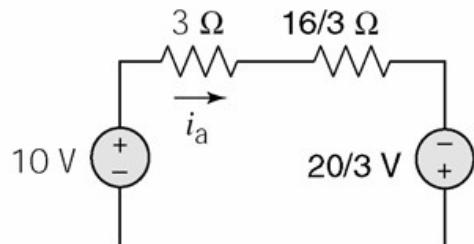

5.2-9 $P= 117.72\text{W}$

5.3-1 $A=1/4, b=3/5$

5.3-4 $v=v_1+v_2=40+60=100$

5.3-8 $i_x=i_1+i_2=2/3-1/2=1/6$

5.4-4 $v_{oc}=12 \text{ V}, R_t=6\Omega$

5.4-6 $v_{oc}=18 \text{ V}, I_{sc}=-6 \text{ A}, R_t=-3\Omega$

5.5-3 $I_{sc}=-7.5 \text{ A}, R_t=2\Omega$

5.6-5 $v_{oc}=3 \text{ V}, I_{sc}=1 \text{ A}, R_t=3\Omega=R_L, P_{max}=3/4$

5.6-8 $v_{oc}=-27 \text{ V}, R=R_t=196\Omega, P_{max}=0.93$

Chaper 6

$$6.3-7 \quad i_o = \frac{R_2 + R_3}{R_1 R_3} v_s \quad v_o = \frac{R_2 R_4}{R_1 R_3} v_s$$

$$6.3-10 \quad \frac{v_o}{i_s} = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$

for having $\frac{v_o}{i_s} = 20 \frac{V}{mA}$, e.g. $R_1 = 5 \text{ k } \Omega$ and $R_2 = R_3 = 10 \text{ k } \Omega$

6.4-5

6.4-6 $v_a = -24/13$, $v_c = -30/13$

6.4-7 $v_o = 12 \text{ V}$, $i_o = -0.7 \text{ mA}$

6.4-11 $v_o = 4 v_s$