

Simplifications to get solutions

Use a mixture of methods, sometimes iteratively.

REDRAW make neater, easily understood

REDUCE remove details not needed for what we're studying


COMBINE join multiple components into an equivalent

DIVIDE {voltage} division — useful rules
 {current}


TRANSFORM choose more convenient equivalents

REDRAWING

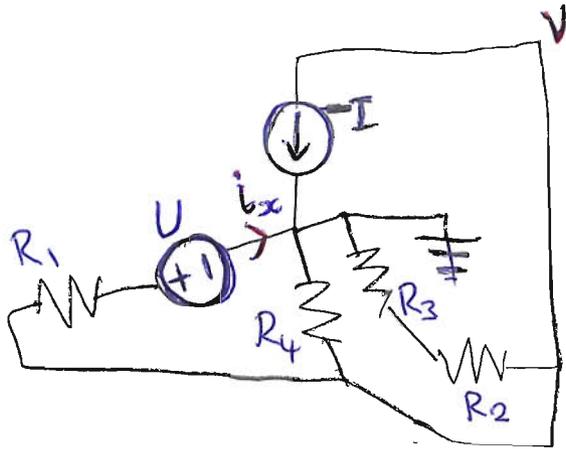the same circuit (components, connections, markings i_x , u_y)
but differently drawn




equivalent

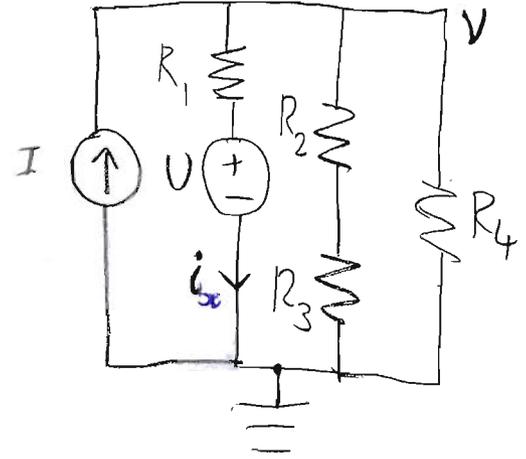

Redrawing might make a solution much easier to see.
Of it might waste time and allow a transcription error...
THE BEST CHOICE depends on you and the circuit.


tips for re-drawing :

- **be systematic** : in a complicated case, number the nodes and check
 - check each component is present
 - check each component connects to right nodes
 - check directions relative to nodes
 - count connections (terminals) on each node.

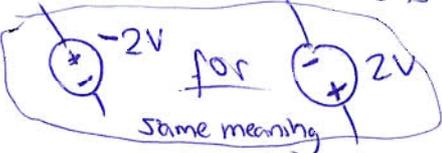
- identify nodes with many connections ... place bottom or top.
- consider swapping 
- keep mainly vertical and horizontal.
- etc

REDUCE

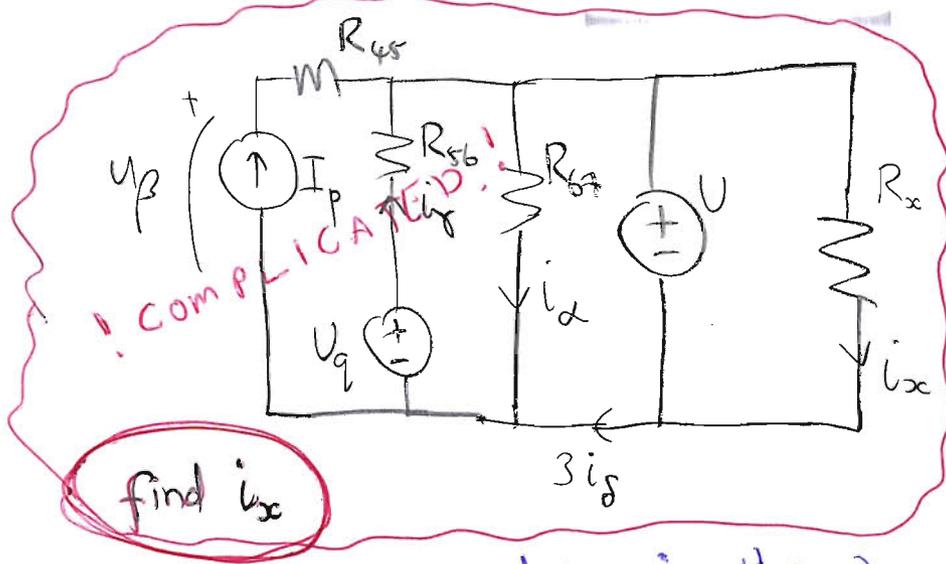When redrawing, we might not need all the details



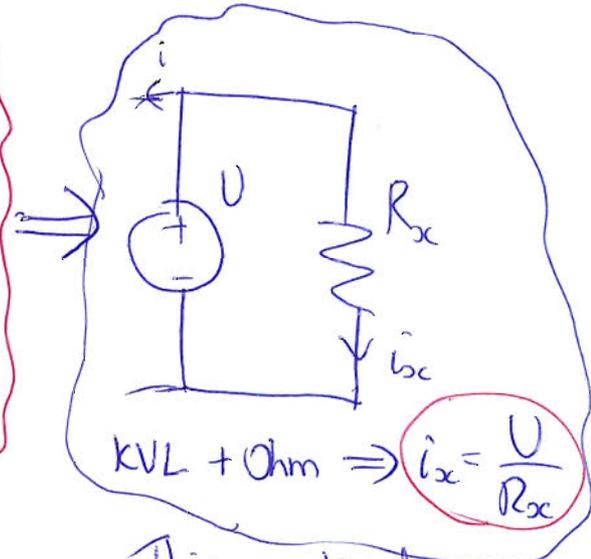If the task is to find just i_x then in this circuit we don't need to know what happens the other side of the voltage source! KVL in one loop fixes the value of i_x .



This simplified circuit is ok for finding i_x . (But not for "what power does the source U deliver!")

----- but sometimes every component and marking
is relevant to the solution, so we can't reduce.
except by COMBINING components into equivalents.


(i_x in the circuit that we redrew is an example
where all components are relevant.)

So how do we combine components?


COMBINE

Probably familiar:

SERIES
resistors

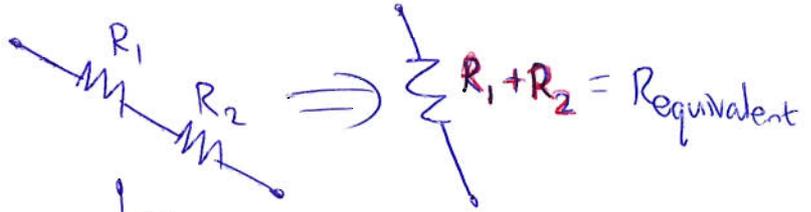

PARALLEL
resistors

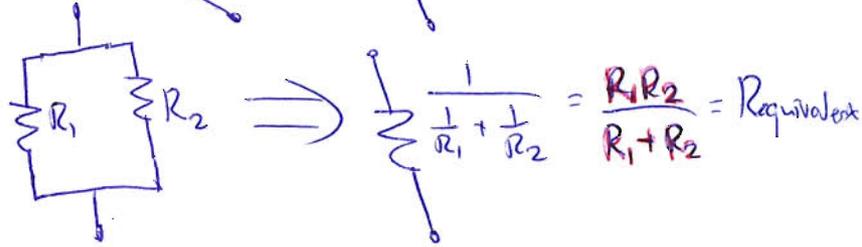

actual
circuit, with
two terminals

an equivalent that
"looks the same"
at the two terminals


combining into an
equivalent means
replacing with a
component of the same
 u, i behaviour.

There are also theorems for components connected with
three or more terminals
We stay with just two for now!

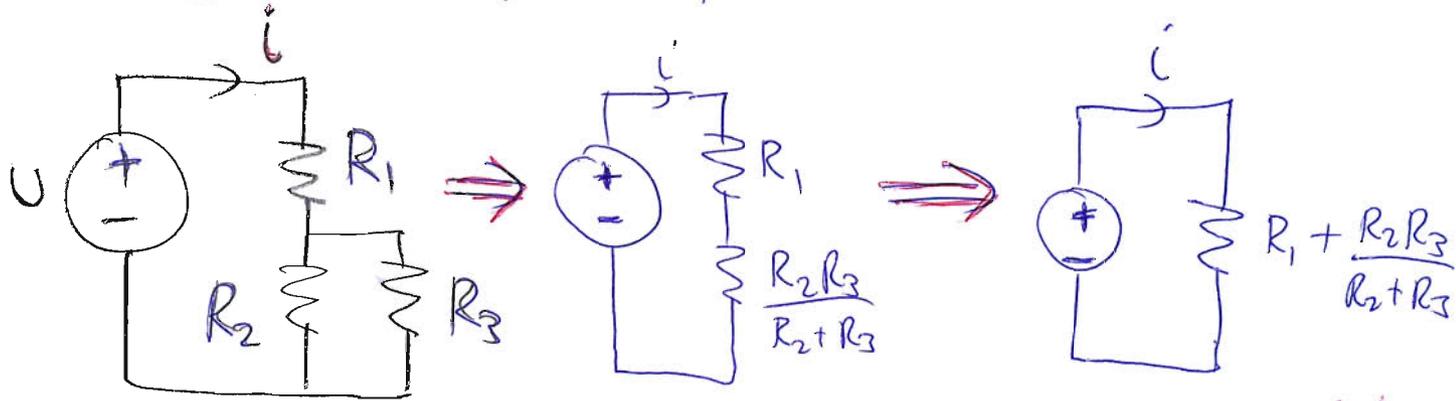example



Combining resistors often helps get solutions.



combine parallel

combine series

calculate




$$\bar{i} = \frac{U}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$$

simplify

$$\bar{i} = \frac{U(R_2 + R_3)}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$




Could have solved by writing several KVL or KCL equations. But combining can be neat.

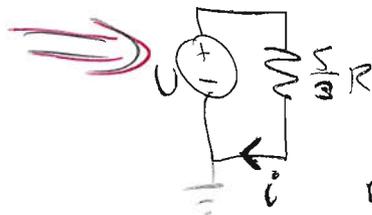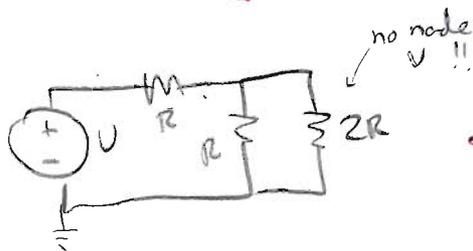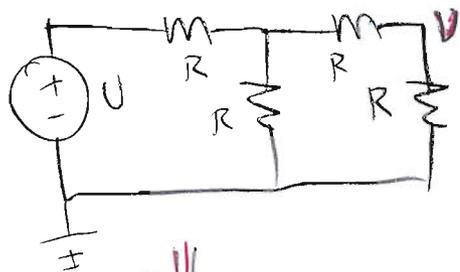Another example: find V given that $U = 10V$ and $R = 2\Omega$



now define current i ,

$$i = \frac{U}{R} \cdot \frac{3}{5}$$

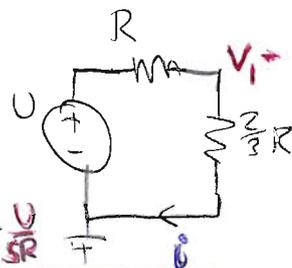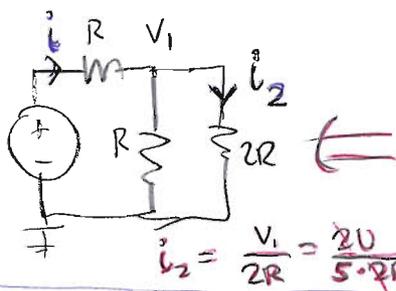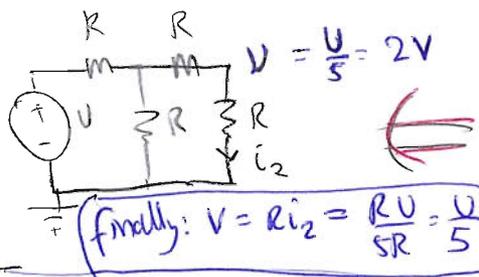

start removing combination



$$V_1 = \frac{2}{3}R \cdot \frac{U}{5R} = \frac{2}{5}U$$

It's not trivial. Some simultaneous KVL or KCL could do it. Or we can combine resistors. If we combine, we lose the node where V is defined! But we can do this to solve something else, then work backward for V .




A warning.

Resistors in series or parallel can be made into an equivalent.

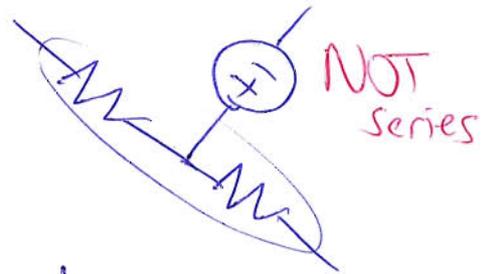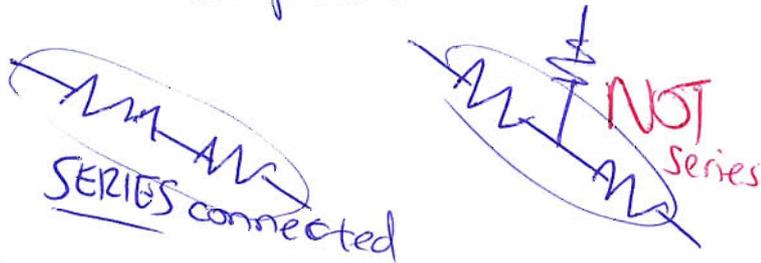SERIES means all current in one passes in the other too ... they should have one terminal of each connected, but not to a third component



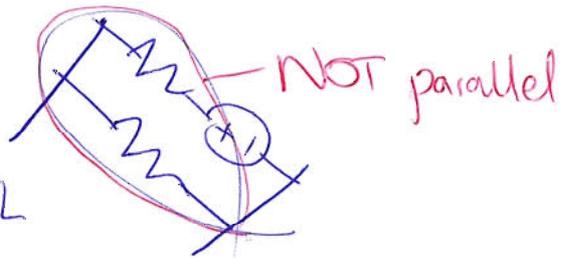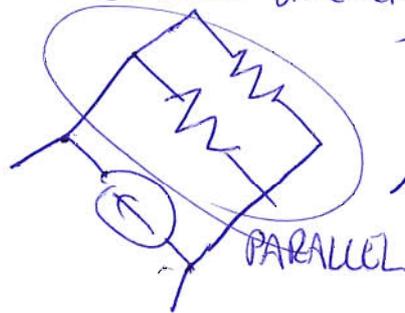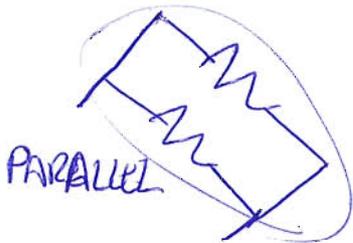
PARALLEL means both connect directly between the same two nodes.



combining resistors to an equivalent two-terminal model is typically useful when solving something elsewhere in the circuit.


Or sometimes we solve elsewhere, then solve something inside the set of resistors that we had equivalenced, like the previous example.

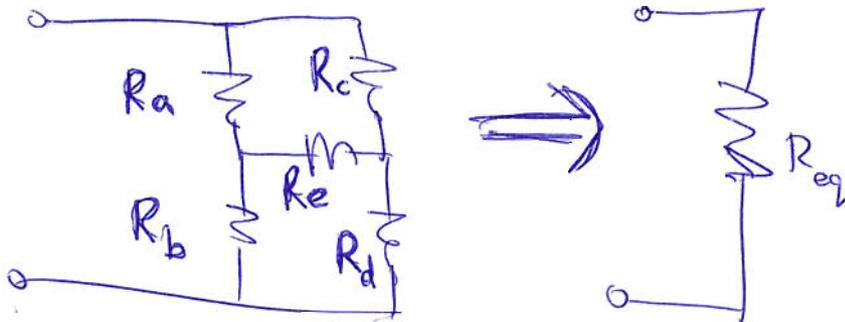Making these equivalents is **not** always possible by just the series/parallel rules:



≠ an R_{eq} exists but you won't find it by series/parallel reasoning, as nothing is series or parallel here!

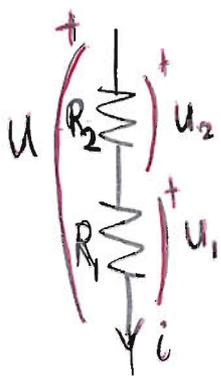resistors in series and parallel : how to show the relation.




$$U = U_1 + U_2 \left. \begin{array}{l} \text{KVL,} \\ \text{(potential vdding)} \end{array} \right\}$$

$$\left. \begin{array}{l} U_1 = iR_1 \\ U_2 = iR_2 \end{array} \right\} \text{Ohm}$$

implicitly, by KCL, we see i is same in both resistors.

$$\Rightarrow U = i(R_1 + R_2) = i R_{eq}$$

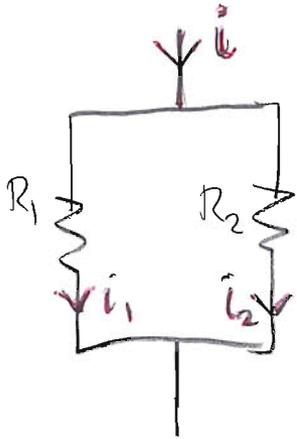a resistor of R_{eq} will behave with the same U, i relationship



$$\bar{i} = \bar{i}_1 + \bar{i}_2 \left. \begin{array}{l} \text{KCL} \end{array} \right\}$$

$$\left. \begin{array}{l} \bar{i}_1 = \frac{U}{R_1} \\ \bar{i}_2 = \frac{U}{R_2} \end{array} \right\} \text{Ohm}$$

implicitly, by KVL, we see U is same for both


$$\Rightarrow \bar{i} = U \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\stackrel{\text{so}}{=} U = \bar{i} \cdot \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \bar{i} R_{eq}$$

$$= \bar{i} \frac{R_1 R_2}{R_1 + R_2}$$

DIVIDERS : $\left\{ \begin{array}{l} \text{Voltage} \\ \text{current} \end{array} \right\}$ division are quick formulas useful with series or parallel resistors

Voltage division

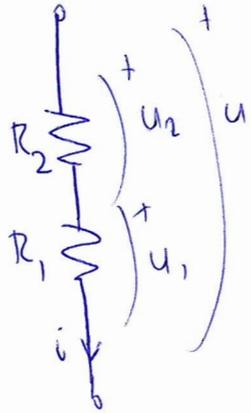

Voltage U is divided between R_1 and R_2 .
How can we find U_1 , if we know U ?


$$U_1 = \bar{i} R_1$$

$$\bar{i} = \frac{U}{R_1 + R_2}$$

equivalent resistance

$$\therefore U_1 = U \frac{R_1}{R_1 + R_2}$$

Current division

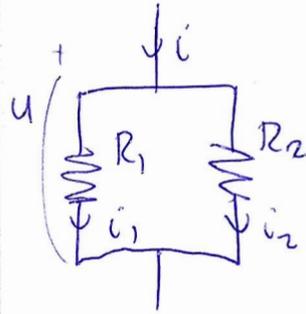

Current \bar{i} is divided between R_1 and R_2 .
How can we find \bar{i}_1 , if we know \bar{i} ?



$$\bar{i}_1 = \frac{U}{R_1} = \bar{i} \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

equivalent resistance

$$\therefore \bar{i}_1 = \bar{i} \frac{R_2}{R_1 + R_2}$$


Other combinations of two components, connected in parallel or series to two terminals, are also of interest.

Can we simplify/combine these pairs?

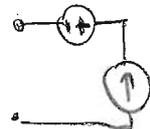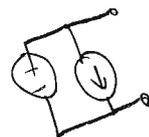


?

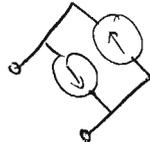There are 12 pairs, if using U, I, R , series or parallel (without considering direction).



They each give one of 4 types of behaviour:



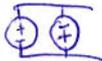
⑤ contradiction/badly defined: 

① behave like 1 component with a value depending on both: $\frac{R_1 R_2}{R_1 + R_2}$

② behave like just 1 of the components — the other is hidden (irrelevant)

③ cannot be simplified to one component, but has well defined behaviour.

Two similar components:

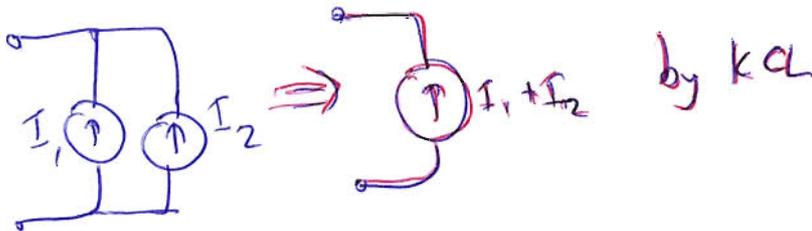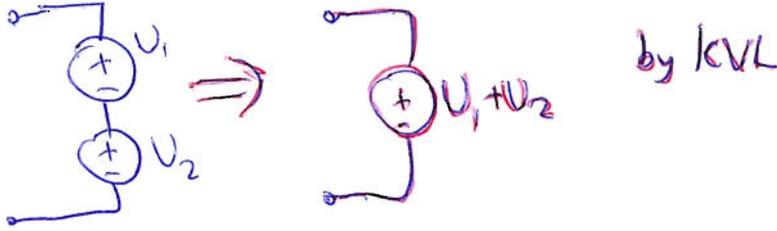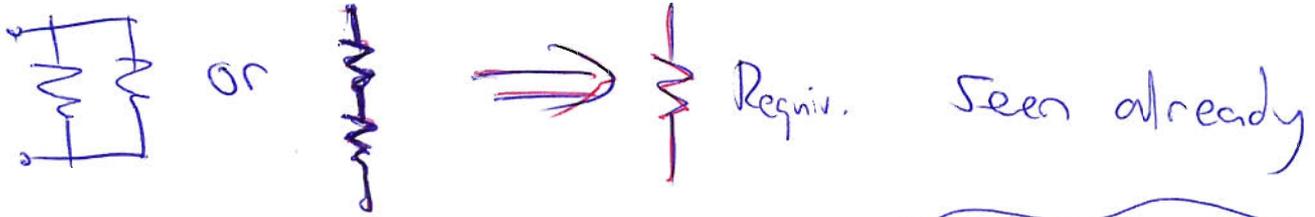


But




Diagram illustrating a circuit configuration that is considered "forbidden" or "strange". It shows two voltage sources, each represented by a circle with a '+' sign at the top and a '-' sign at the bottom, connected in parallel. The top source is labeled V_1 and the bottom source is labeled V_2 . To the right of this, two current sources, each represented by a circle with an upward-pointing arrow, are connected in parallel. The left current source is labeled I_1 and the right current source is labeled I_2 .

are strange "forbidden" cases ... What does Kirchhoff say if $V_1 \neq V_2$ or $I_1 \neq I_2$?
BADLY DEFINED circuit ... contradiction.

Sources U, I together

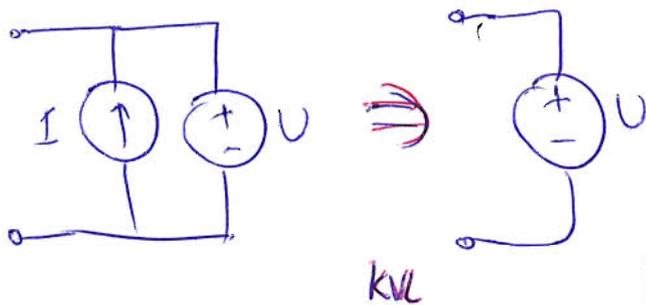


or with resistor

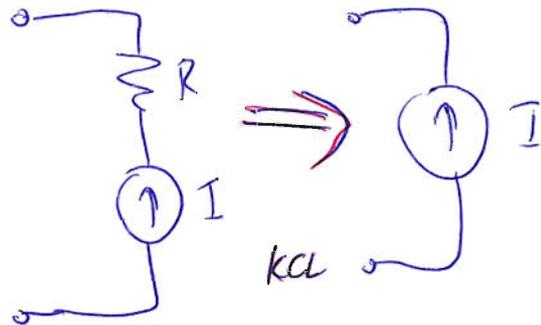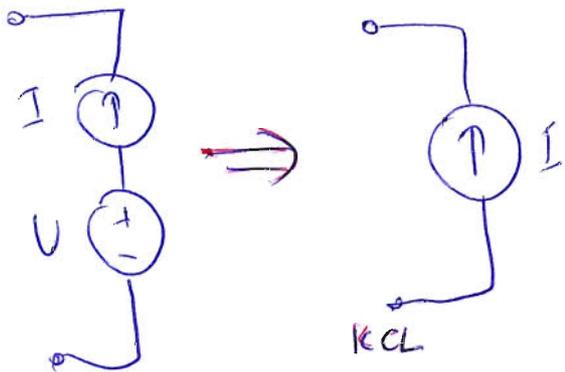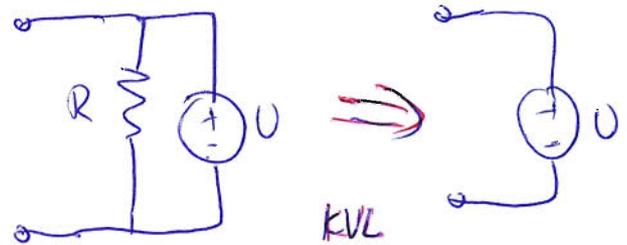


So

SERIES CURRENT source or PARALLEL VOLTAGE source WINS

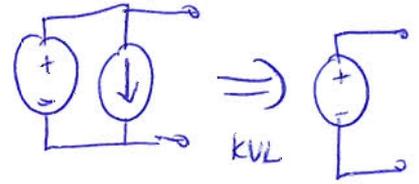If you're suspicious about the earlier page, eg.
then try this reasoning ---





We have:

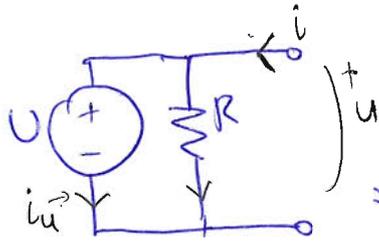

KVL: $u = U$

KCL: $i = \frac{U}{R} + i_u$

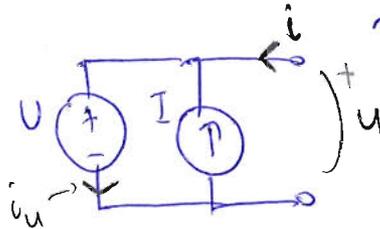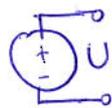


KVL: $u = U$

KCL: $i = -I + i_u$

the voltage sources by definition
fix U and have i_u undetermined
(we can solve i_u by solving the whole circuit including whatever connects to the u, i terminals)
so the total circuit also has a fixed $u = U$ (KVL) and an undefined i --- just like a voltage source with value U

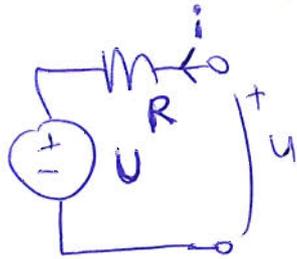Final cases — not like any single component




"Thevenin source"

$$u = U + iR$$

↙ depends on both R & U

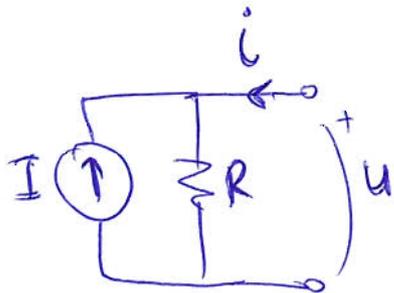notice: these are the same if we choose that $U = IR$



"Norton source"


$$u = (I + i)R = IR + iR$$

↙ depends on both R & I.


Task prove the above relations using KVL/KCL/Ohm's law.

SOURCE TRANSFORMATION: swap between equivalent
Thevenin and Norton sources.

This can help to simplify ...

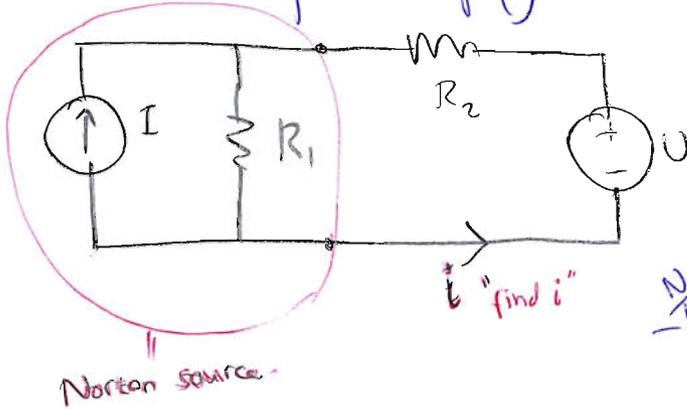

Norton
-Thevenin
transformation

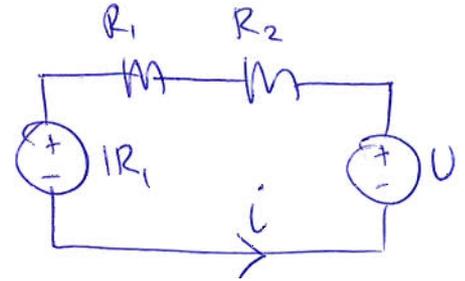

Now it is easier.
KVL gives:

$$i = \frac{U - IR_1}{R_1 + R_2}$$

Remember:

