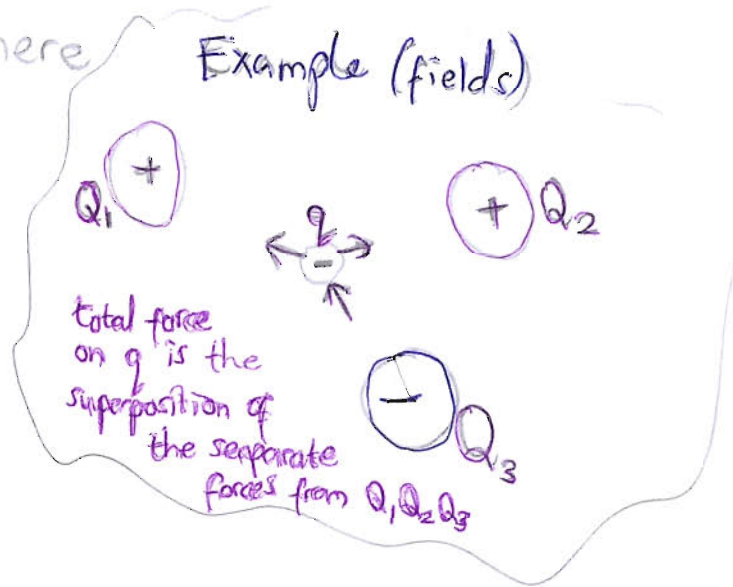


# SUPERPOSITION

- a small but useful subtopic
- familiar from elsewhere




- applies to linear circuits

# BASIC PRINCIPLE

① in a circuit with more than one independent source,

② solve the circuit for one of the sources at a time

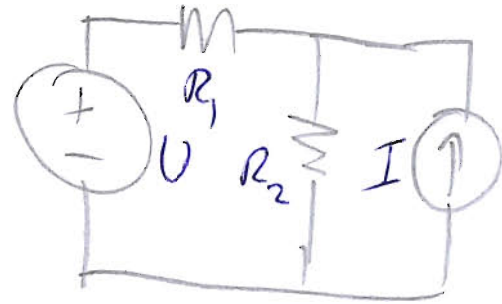③ then add the solutions to find the solution for the complete circuit,





## FURTHER POINTS

- ① doesn't really have to be "one at a time"  
(can do any groups as long as we handle each independent source just once) eg. with 5 sources, could solve for 3 of them together, then 1 then 1 — choose whichever is most useful)
- ② main "open question" (until next page):  
What do we do with the other sources when solving for one?
- ③ important "skill":  
need to be careful to keep track of what's being solved, and to add our solutions at the end

What ~~do~~ do we do to the other sources when solving for one of them?   
 (independent sources)   
 When solving


⇒ We SET THEM TO ZERO

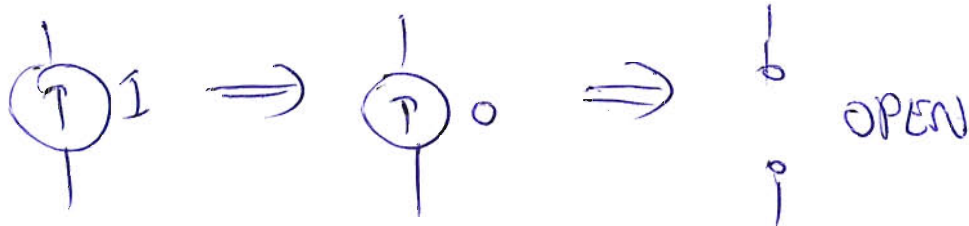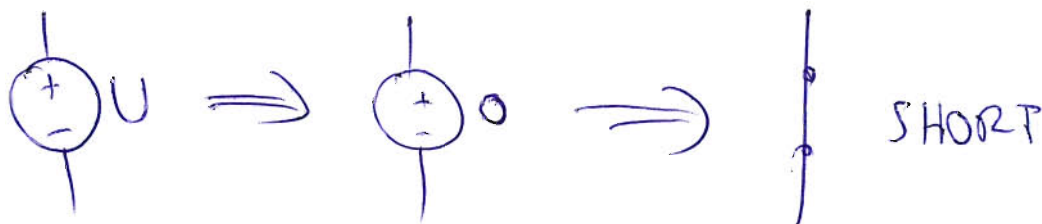

IMPORTANT

"obvious" but a common error is to confuse these cases !!

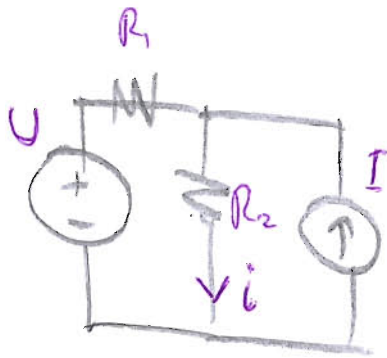EXAMPLE: let's try it with the earlier circuit.




"find  $i$ "

There are two independent sources.


To use superposition, we solve two different circuits (or "superposition states"):

$U$  active

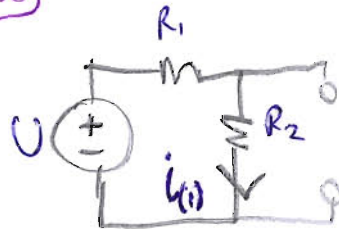

$$\hat{i}_{(1)} = \frac{U}{R_1 + R_2}$$

$I$  active

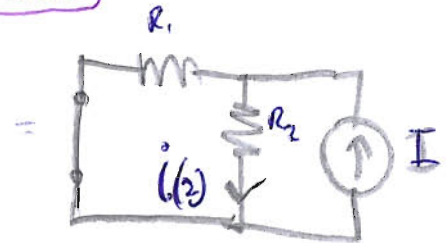

$$\hat{i}_{(2)} = \frac{I R_1}{R_1 + R_2}$$

Then add the results:

$$i = i_{(1)} + i_{(2)} = \frac{U}{R_1 + R_2} + \frac{I R_1}{R_1 + R_2} = \frac{U + I R_1}{R_1 + R_2}$$


the solution,  
by superposition,

So, that was quite an easy idea!

- sometimes good for getting solutions
- sometimes not as easy as e.g. nodal analysis
- particularly useful as a concept for proofs, even if not always best for quick solutions.

Now the usual question:

What about DEPENDENT SOURCES ?

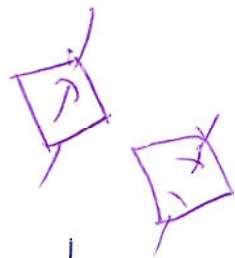


Answer: the usual approach is to leave these active in the circuit in each calculation (like the resistors) —  
(we add the solutions of independent sources acting separately)




complete
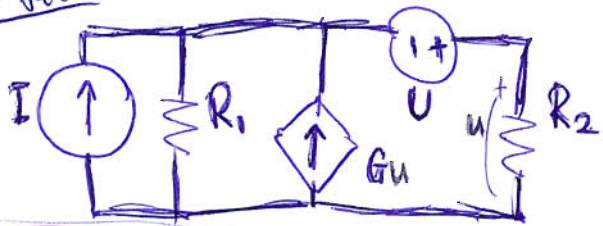
# EXAMPLE with DEPENDENT SOURCE and superposition



'I' active

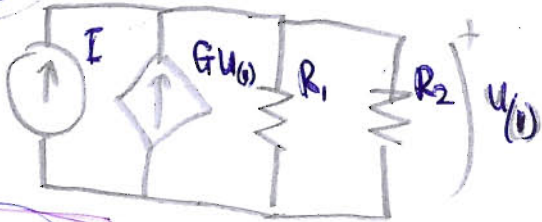


$$u(1) = (I + Gu(1)) \frac{R_1 R_2}{R_1 + R_2}$$

$$u(1) \left( 1 - \frac{G R_1 R_2}{R_1 + R_2} \right) = \frac{I R_1 R_2}{R_1 + R_2}$$

$$u(1) = \frac{I R_1 R_2}{R_1 + R_2 - G R_1 R_2}$$

solution for  
state 1

'U' active

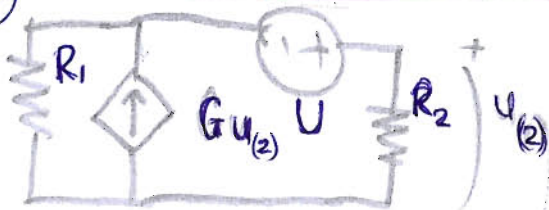

$$\frac{u(2)}{R_2} + \frac{u(2) - U}{R_1} - Gu(2) = 0 \quad \leftarrow (KCL)$$

$$R_1 u(2) \left( \frac{1}{R_1} + \frac{1}{R_2} - G \right) = U$$

$$u(2) = \frac{U R_2}{R_1 + R_2 - G R_1 R_2}$$

solution for  
state 2

add



(continued)

$$U = U_{(1)} + U_{(2)} = \frac{(U + IR_1) R_2}{R_1 + R_2 - GR_1R_2}$$

That might seem neat.

But in this case, nodal analysis (KCL) on the whole circuit including both sources <sup>↑</sup> independent would probably have been

quicker and easier ... try it!

(Just add a "-I" term in the start of the state(e) solution on the previous page!)