

TWO-TERMINAL EQUIVALENTS


and

MAXIMUM POWER


equivol ekvivalent, Helmholtz-Thevenin theorem

maximal effektoverföning

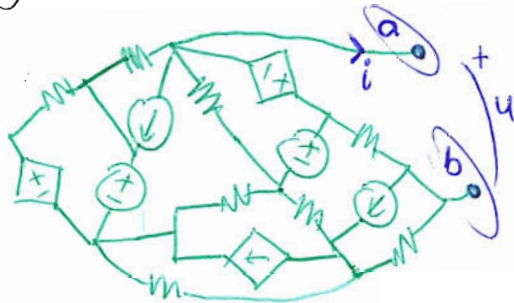A very deep, useful, "powerful" circuit theorem is that any **linear dc circuit's** behaviour at two terminals (relation of U & i) can be **equivalently modelled** by a **Thevenin or Norton source!**





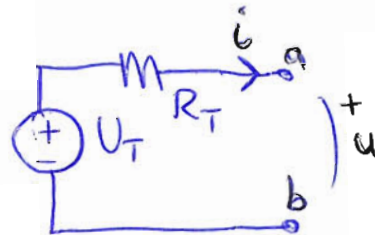And, for a Thevenin source (and thus for a Norton source or any two terminal dc linear circuit) one choice of **voltage** or **current** or **resistance** at its terminals results in **maximum possible power output**.



suitable choice of U_T, R_T makes this equivalent in its U, i relation.

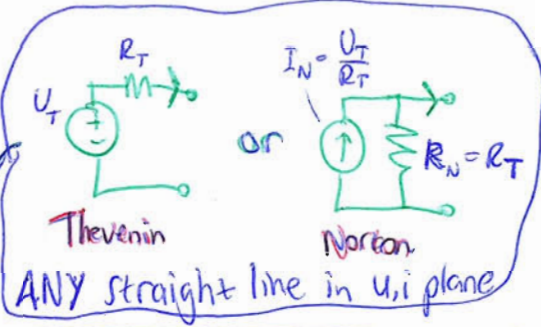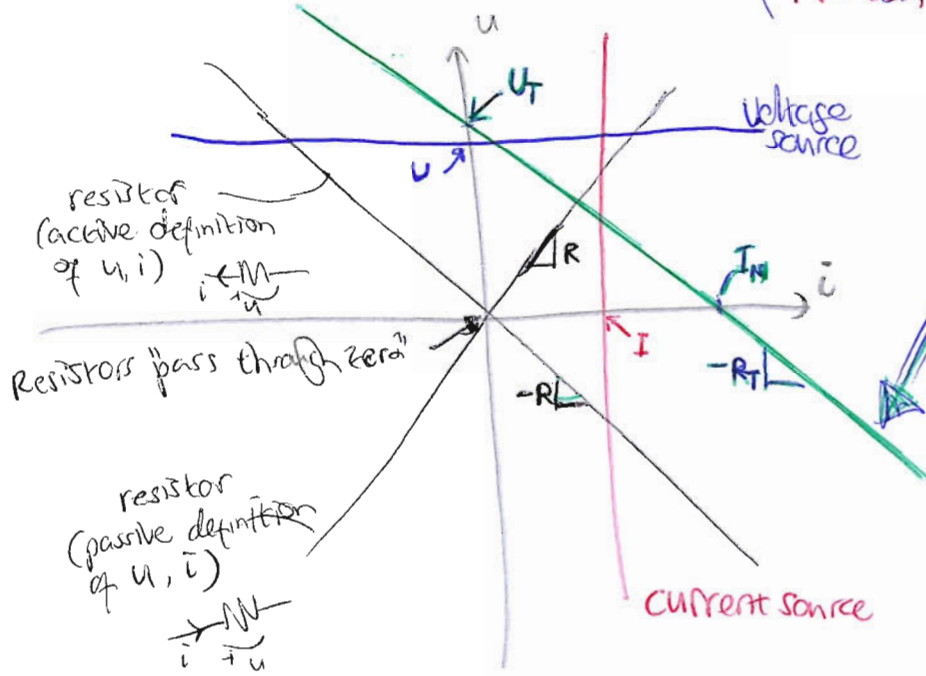Another way of describing the $\left\{ \begin{array}{l} \text{Thevenin equivalent} \\ \text{or} \\ \text{Norton equivalent} \end{array} \right\}$ concept:



IGNORE THIS \uparrow if you don't like diagrams!

"the u, i relation for any linear 2-terminal dc circuit is a straight line"
 (So how do we work out what line, from the circuit?)


Pause: Why is it useful to find a $\left\{ \begin{array}{l} \text{Thevenin} \\ \text{Norton} \end{array} \right\}$ equivalent?

Lots of reasons! (it really **is** useful) -- here are a few --

- simplify all of a big circuit except for a little part that we are designing/changing/studying --- then our analysis is with just our little part and a Thevenin/Norton source
- conceptual understanding: by seeing how the equivalent changes (es. R_T changes) when we change something in the original circuit, we see how we can expect other things connected to the circuit's terminals to be affected.
- practical connections — the idea of output resistance (amplifier) or source impedance (power) is basically Thevenin resistance; we can determine it by measurement as well as calculation

How can we find the values of $U_T R_T$ (or $I_N R_N$)
to make a Thevenin or Norton equivalent of a given circuit?

There are several choices:

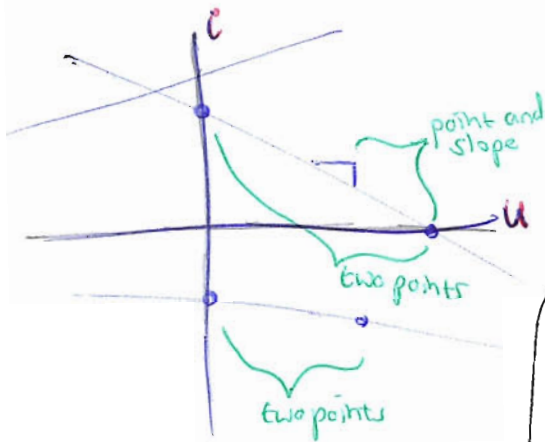


We have to define a line in the u, i plane ... two pieces of information are needed: two points, or point and slope (2 koordinater, eller koordinat och lutning/gradient)

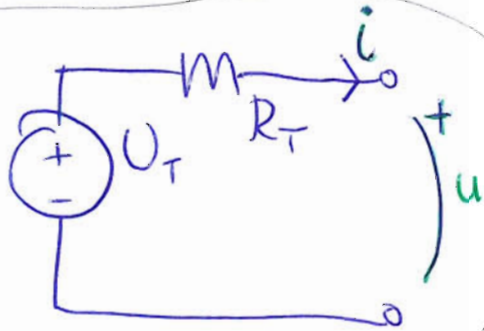Examples of common approaches

- ① derive a $u = \overset{\text{something}}{\text{something}} + \overset{\text{something}}{\text{something}} i$ equation for the circuit, and compare to the Thevenin/Norton equation
- ② find shortcircuit current and open circuit voltage (often simpler circuits to solve)
- ③ find one of the above, and find slope directly

Remember U, i relation for Thevenin & Norton sources



$$u = U_T - R_T i$$

or


$$i = \frac{U_T}{R_T} - \frac{1}{R_T} u$$



for equivalence,

$$R_T = R_N$$

$$U_T = I_N R_N$$

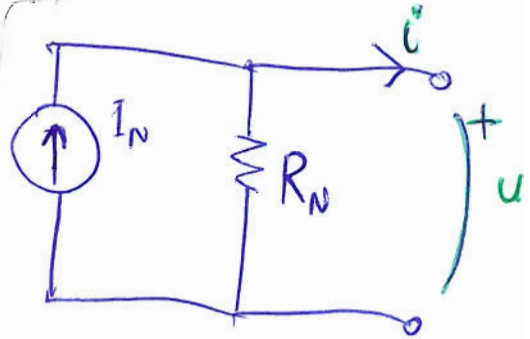

$$u = I_N R_N - R_N i$$

$$i = I_N - \frac{1}{R_N} u$$

Try **deriving** all of these!
(KCL, KVL, Ohm)

Notice the **form**:
of all these equations.

$$y = m x + c$$

straight line

One method direct derivation of u, i relation

- sometimes hard algebra, better by other methods 😞
- sometimes very convenient! 😊
- no limitations (other than difficulty) — works with dependent sources

→ **Get an equation** relating u and i for the circuit:
 might not be easy!

wild example \Rightarrow

$$u = \frac{(I_7 + I_5)R_3 R_4}{R_2 + R_1} + \frac{U_2 R_6}{R_7 + R_8} - \frac{R_1 R_2}{R_2 + R_3} \cdot (1 + k) \cdot i$$


→ **Compare it** to the equation for a Thevenin or Norton source, and thus find the values for the equivalent

$$u = U_T - R_T i \quad (\text{Thevenin source})$$

(Notice $u = U_T - R_T i$ or $u = U_T + R_T i$ depends on chosen definition of u & i)

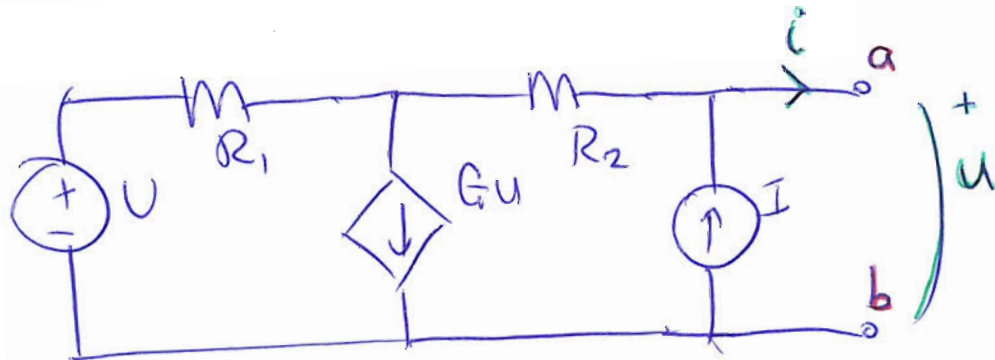Example direct derivation (Quite a hard example)

find the Thevenin equivalent of this circuit,
seen between a-b.




Hmmm. Could try superposition, source transformation, ...?

Let's go for nodal analysis ... often a good choice if no really good simplification is obvious. By supernode or "simplified branch" we only need two equations and unknowns here.

cont'd.

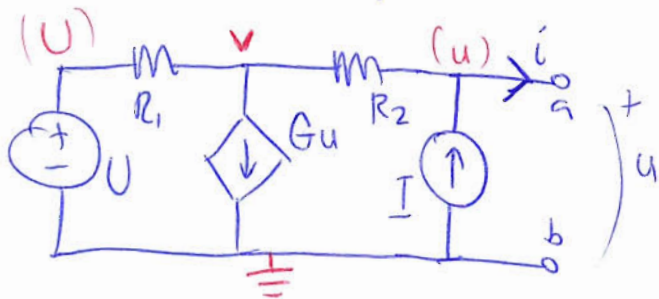define a reference node and a potential v .
the other potentials are either known (U) or marked already (u).



Want to eliminate V_v to have just u and i unknown, in a single equation

$$\text{KCL}(v) \quad \frac{U - U}{R_1} + Gu + \frac{v - u}{R_2} = 0$$

$$v \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + Gu - \frac{U}{R_2} - \frac{U}{R_1} = 0$$

$$\text{KCL}(u) \quad \frac{u - v}{R_2} - I + i = 0$$

$$u - v = -R_2(-I + i)$$

$$v = R_2(i - I) + u$$

substitute this expression for v

contd.

$$\left(R_2 (i - I) + U \right) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + GU - \frac{U}{R_2} - \frac{U}{R_1} = 0$$

collect terms:


$$U \left(\frac{1}{R_1} + \cancel{\frac{1}{R_2}} - \cancel{\frac{1}{R_2}} + G \right) - \frac{U}{R_1} - I R_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + i R_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = 0$$

$$U = \frac{\frac{U}{R_1} + I R_2 \left(\frac{R_1 + R_2}{R_1 R_2} \right) - i R_2 \left(\frac{R_1 + R_2}{R_1 R_2} \right)}{\frac{1}{R_1} + G}$$

$$U = \frac{\frac{U}{R_1} + \frac{I}{R_1} (R_1 + R_2) - \frac{i}{R_1} (R_1 + R_2)}{\frac{1 + GR_1}{R_1}} = \frac{U + I(R_1 + R_2)}{1 + GR_1} - \frac{R_1 + R_2}{1 + GR_1} i$$

U_T R_T

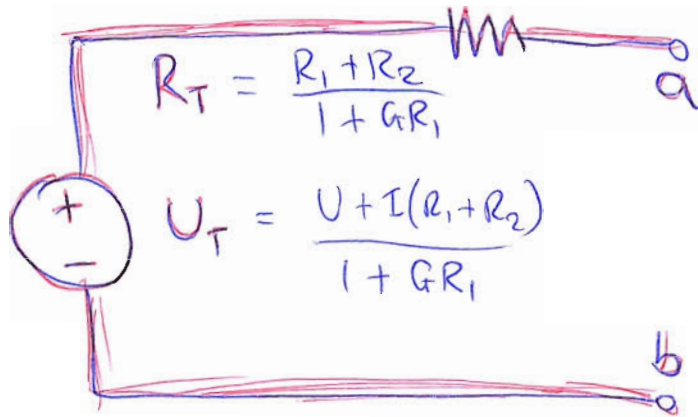The Thevenin equivalent of the original circuit, between a-b, is therefore:





(Careful to get the direction right, with respect to the terminals ... not upside down source)

If we wanted a Norton equivalent, we could use source transformation:

$$I_N = \frac{U_T}{R_T} = \frac{U + I(R_1 + R_2)}{R_1 + R_2}$$
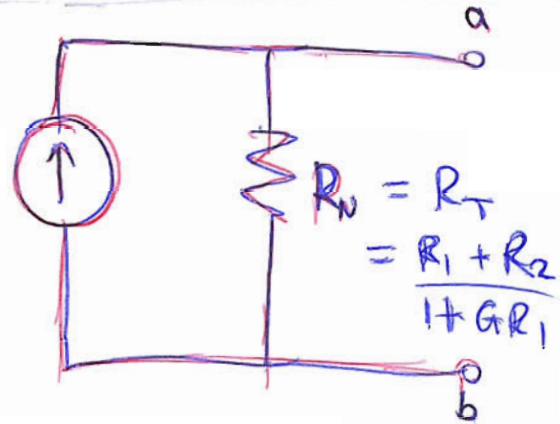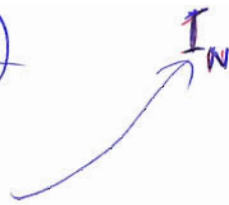
$$\therefore I_N = \frac{U}{R_1 + R_2} + I$$



In some cases, calculating $\frac{U_T}{R_T}$ or $I_N R_N$ may be harder (in algebra).

So we might benefit from looking for an expression in the form $i = I_N - \frac{U}{R_N}$ at the start, (instead of for $u = U_T - R_T i$) if we want a Norton equivalent (instead of Thevenin).


(But we might instead find it's easier to get one form of the equation then convert by source transformation -- depends on the circuit!)

A note: in that last example we had 3 unknowns & 2 equations at the start -- is that ok?

Yes: we are trying to get a relation between u and i , not to solve every unknown... We want one equation to remain.

This is expected, because we haven't defined the circuit fully. There is a "something" connected at $a-b$, and until we define that something we can't solve everything.

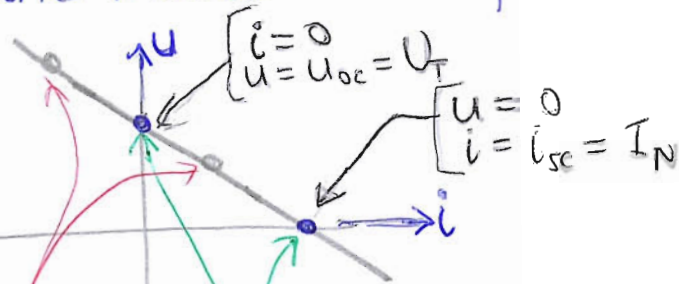Another method: two points ... e.g. $\begin{cases} \text{open circuit voltage } U_{oc} \\ \text{short circuit current } I_{sc} \end{cases}$



any two points define the line so that we could find I_N U_T R_T


but these two points are a very nice choice!

Why? ...

If we find I_{sc} , this gives us I_N directly:





And U_{oc} would give U_T directly:

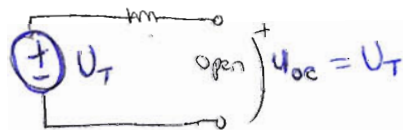

And we know that $R_N = R_T = \frac{U_{oc}}{I_{sc}}$
(source transformation)


A further advantage of choosing the open circuit voltage and short circuit current is that adding shorts or opens can make the circuit simpler to solve than with a generic "u, i" relation. (The down-side is that two different circuits have to be solved.)

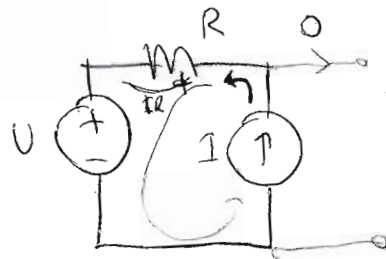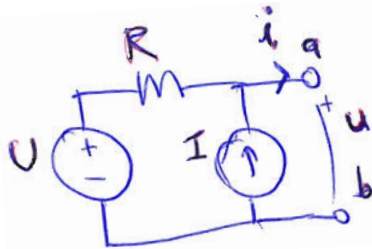example: find Norton equivalent of this circuit.




$$U_{oc} = U + IR$$

simple KVL

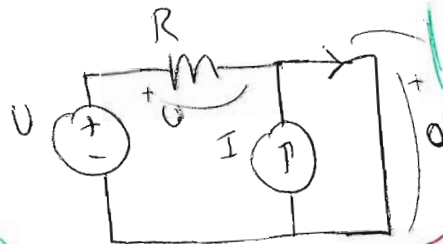

$$I_{sc} = \frac{U}{R} + I$$

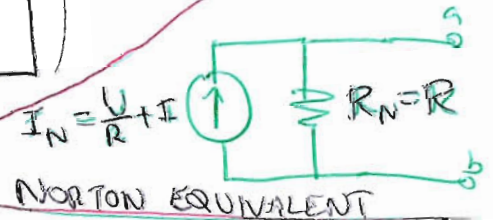
$$\text{So } R_N = \frac{U_{oc}}{I_{sc}} = \frac{U + IR}{\frac{U}{R} + I} = R$$



Another method involves finding either U_{oc} or I_{sc} , then finding the resistance directly.

This is based on superposition: set all independent sources to zero, and see how the circuit behaves at its terminals.

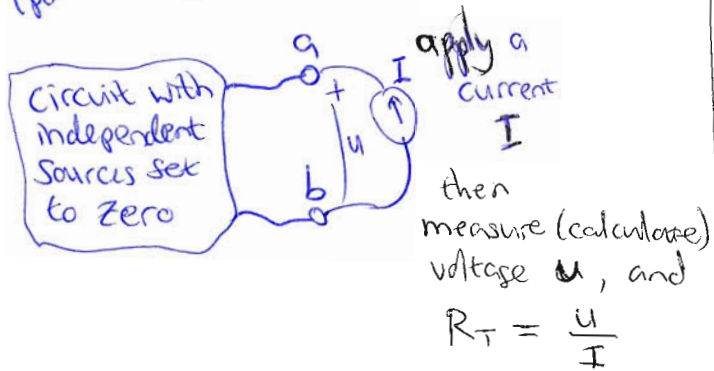General case
(possible dependent sources)




We won't pay much attention to this - probably focus on the short/open method

Very useful case,
with no dependent sources

Set sources to zero, and find equivalent resistance!

It's only resistors remaining ...

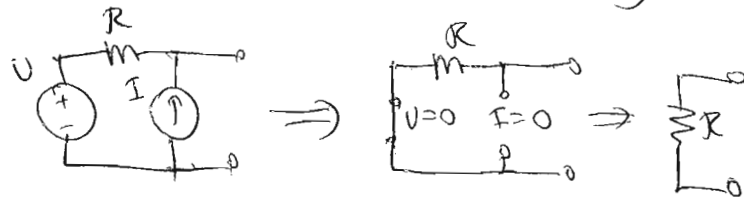

$\therefore R_T = R$ (compare to earlier solution)