
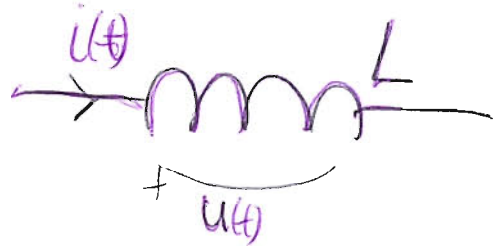


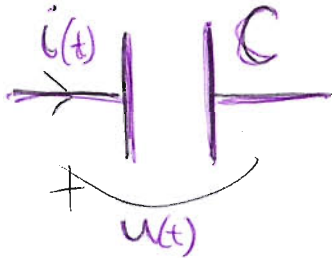New components: CAPACITOR and INDUCTOR
condensator spole (coil)



$$i(t) = C \frac{du(t)}{dt}$$

$$u(t) = L \frac{di(t)}{dt}$$

These are the fundamental definitions ... a bit like a resistor, but with a derivative,


"Now you know all you need to know"
(as long as you can do the maths...)

(again ... but we need to practise about how they behave)

Relation to earlier knowledge ---

Capacitor stores charge.
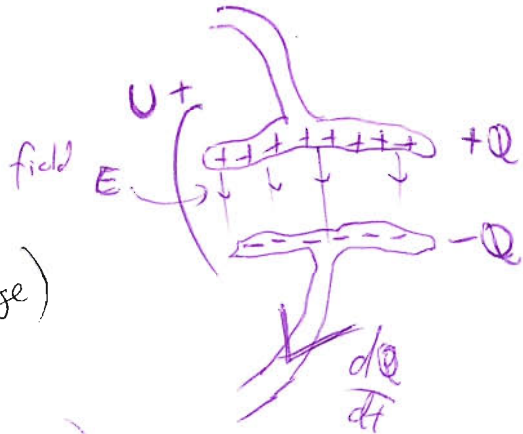
$$C = \frac{Q}{U} \quad (\text{charge per unit voltage})$$



$$\text{Thus } \frac{d(Q)}{dt} = \frac{d(CU)}{dt} \implies \frac{dQ}{dt} = C \frac{dU}{dt}$$

(for inductor, there isn't such an easy physical concept as "charge" --- but if you use a voltage \times time product you can do the same sorts of calculations.)

Now our equations will be **differential** equations instead of just **algebraic** as in dc circuits with U, I, R .

These "reactive" components (C, L) store energy $\left\{ \begin{array}{l} \text{electric field (in } C) \\ \text{magnetic field (in } L) \end{array} \right.$

This stored energy **cannot be instantaneously changed**.

... it takes time ... we see an **inertia** (tröghet)

The components (by their energy) have a "memory".

CAPACITOR \rightarrow electric field energy \rightarrow **Voltage** doesn't change easily
spännings trög

INDUCTOR \rightarrow magnetic field energy \rightarrow **Current** doesn't change easily
ströms trög

$$i = C \frac{du}{dt}$$


$$\int i dt = \int C \frac{du(t)}{dt} dt$$

integrate both sides
of the $i-v$ relation

$$\Rightarrow u(t) = \frac{1}{C} \int_{t_0}^t i(t) dt + u(t_0)$$


value now

the change
between t_0
and now (t)

some known
value at
time t_0

this shows how the "continuous" (trig) ~~variables~~
quantity has a value depending on all of the past

Similarly for inductor;

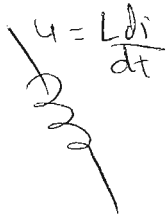
$$u = L \frac{di}{dt}$$


$$\int u(t) dt = \int L \frac{di(t)}{dt} dt \Rightarrow i(t) = \frac{1}{L} \int_{t_0}^t u(t) dt + i(t_0)$$


integrate both sides

We used the term "Continuous quantity" for the energy-storing variable (the trög one)
kontinuerlig storhet

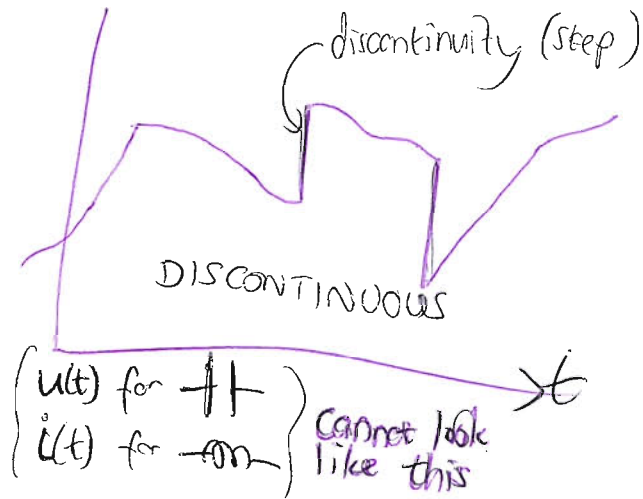
That means it doesn't 'jump' — it changes gradually, needing time for energy to move in or out.




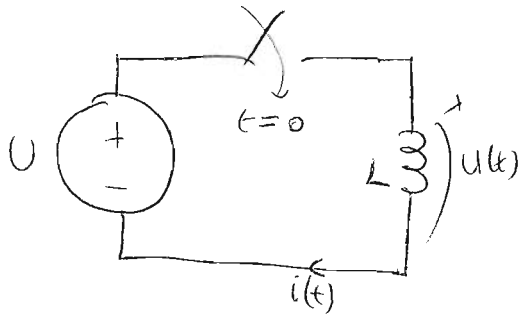
Let's test our confidence in the component definitions
and in simple graphical calculus!



plot $u(t)$ & $i(t)$
for each case.

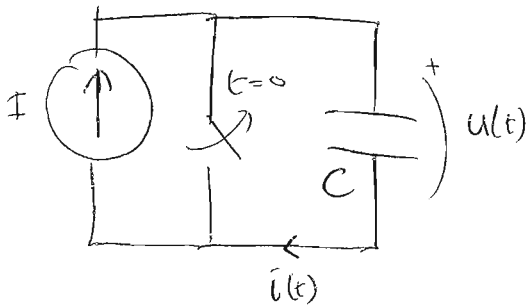

assume $u(0) = i(0) = 0$

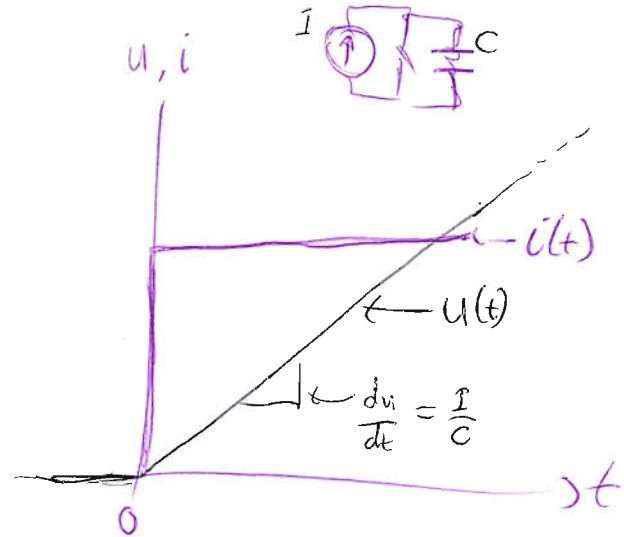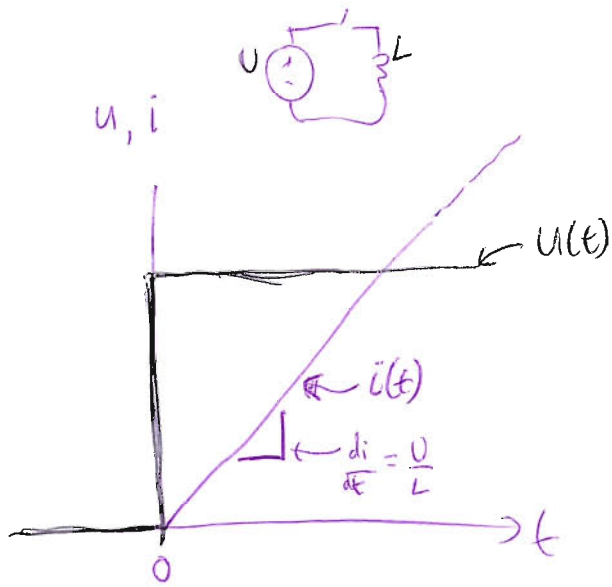


So these cases (keep pumping more and more energy in!
 (not of practical interest ... resistance becomes significant!)

Note the contrast of continuous / noncontinuous quantities.


How about these?

time-varying sources.


a

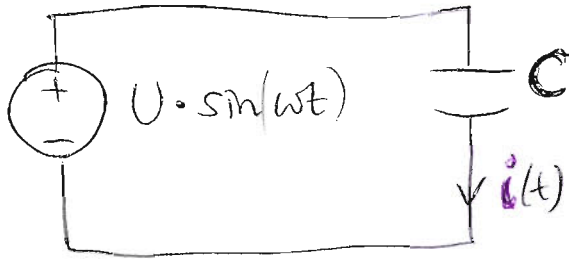

c

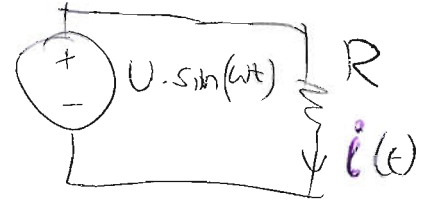


b

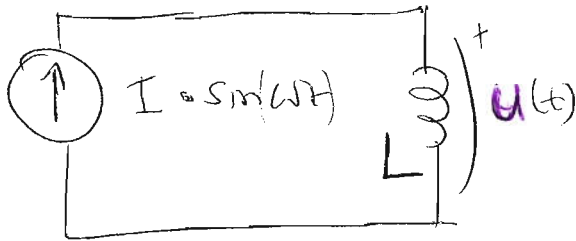

find $i(t)$ or $u(t)$
in each case!

d

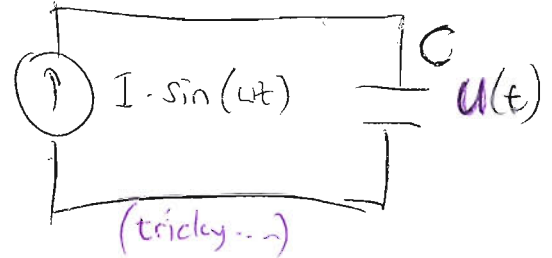

Answers:

(a) $i = C \frac{dn}{dt} = C \frac{d}{dt}(U \sin \omega t) = \omega C U \cos(\omega t)$

(b) "same, by duality" (swap $\{i, u\}$, $\{L, C\}$)

$$u = L \frac{di}{dt} = L \frac{d}{dt}(I \sin(\omega t)) = \omega L I \cos(\omega t)$$

(c) $i(t) = \frac{u(t)}{R} = \frac{U \cdot \sin \omega t}{R} = \frac{U}{R} \sin(\omega t)$ ← easy — no "dynamics" — ie. no memory.

(d) Trickier! $i(t) = I \sin(\omega t) = C \frac{du}{dt}$ integrate both sides


$$u(t) = \frac{I}{\omega C} \int \sin(\omega t) dt + \underbrace{u_k}_{\text{integration constant}} = \frac{-I}{\omega C} \cos(\omega t) + u_k$$

Here we'd need more information to solve completely.

Eg. "assume $u(0) = 0$ " (which tells us that $u_k = \frac{I}{\omega C}$)
at $t=0$
 $u(0) = 0 = \frac{-I}{\omega C} \cos 0 + u_k$




We weren't given enough information to find this!

finally ...

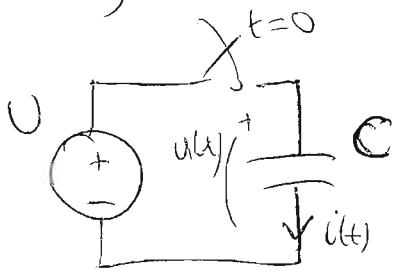


let $u(0) = 0$

plot $u(t)$ e $i(t)$
in both cases.

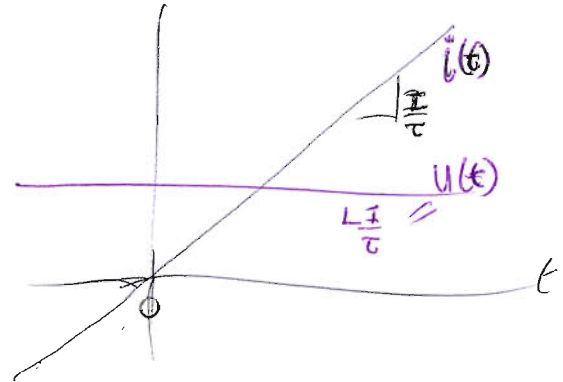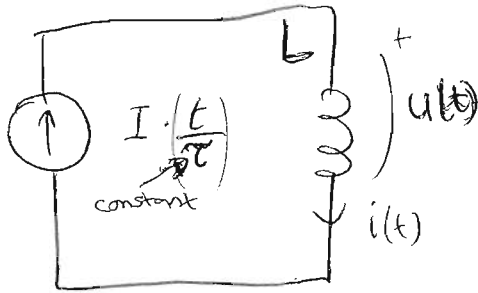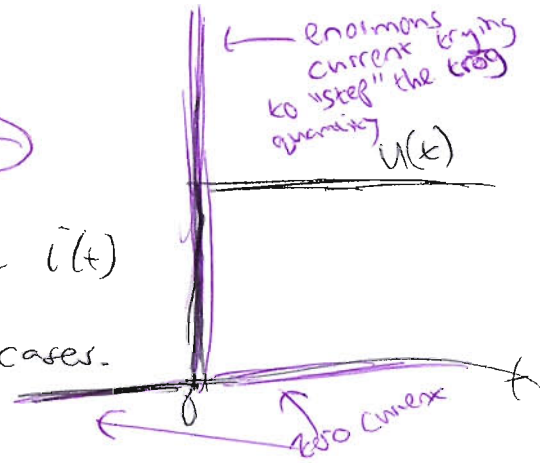

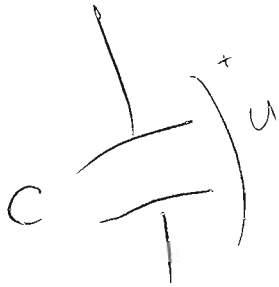Energy in capacitor and inductor ... depends on the continuous quantity
(~~not~~ a mere coincidence!)



$$W = \frac{1}{2} L i^2$$

$$W = \frac{1}{2} C u^2$$

"Work" or energy
(we often use this, letter,
as E is used for
electric field)

Reminded of anything
from mechanics?

how to derive the energy ...

take an uncharged capacitor ... $q=0$, so $U=0$, no energy.

keep pushing charges dq into it!

the work needed to push each one on is $(dW) = (U) dq$
energy voltage charge

do this until we reach charge Q

total energy to do this is $\int 1 dW = \int U dq = \int \frac{q}{C} dq$

sloppy
but shows the
principle!

$$W = \left(\frac{1}{C} \frac{1}{2} q^2 \right) \Big|_0^Q = \frac{1}{2} \frac{1}{C} Q^2 + \text{const}$$

Zero as
we started
at zero
energy





Now substitute the final voltage: $U = \frac{Q}{C}$ i.e. $Q = UC$

$$W = \frac{1}{2} \frac{1}{C} (Q)^2 = \frac{1}{2} \frac{1}{C} U^2 C^2 = \frac{1}{2} C U^2$$

Similarly for inductor energy (but again we
don't have a nice word/concept like "charge"
for the $\int \dot{u} dt$ product)

Parallel and series.

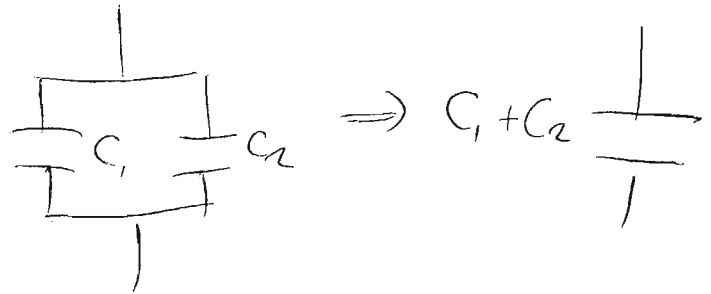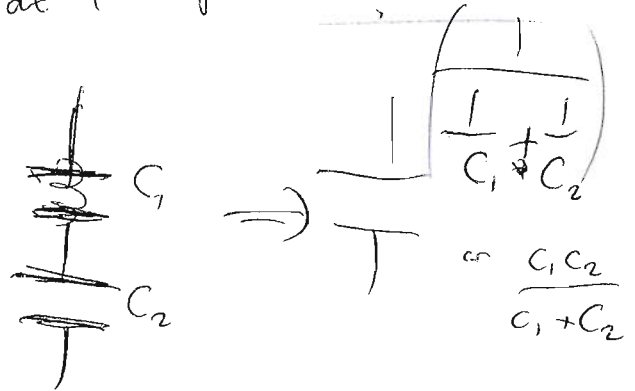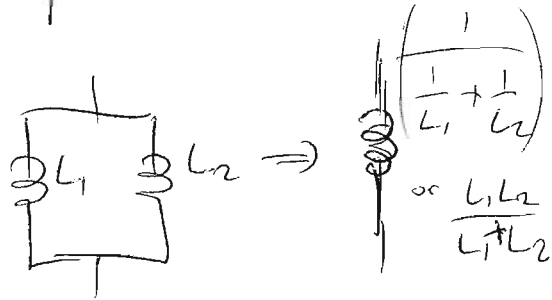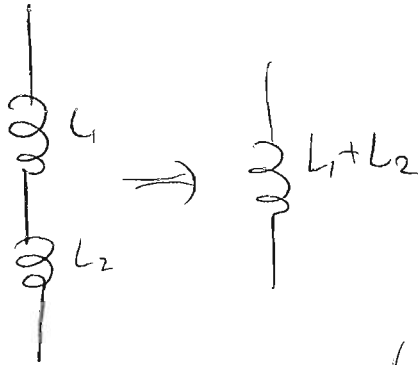
The same derivations can be used as for resistors, but with
e.s. $\frac{di}{dt}$ for inductor (instead of i) or $\frac{dq}{dt}$ for capacitor



Unit step and Switch

function $\mathbf{1}(t)$: $\overset{\vee \text{ one}}{1}$ if $t \geq 0$
 0 if $t < 0$

es.

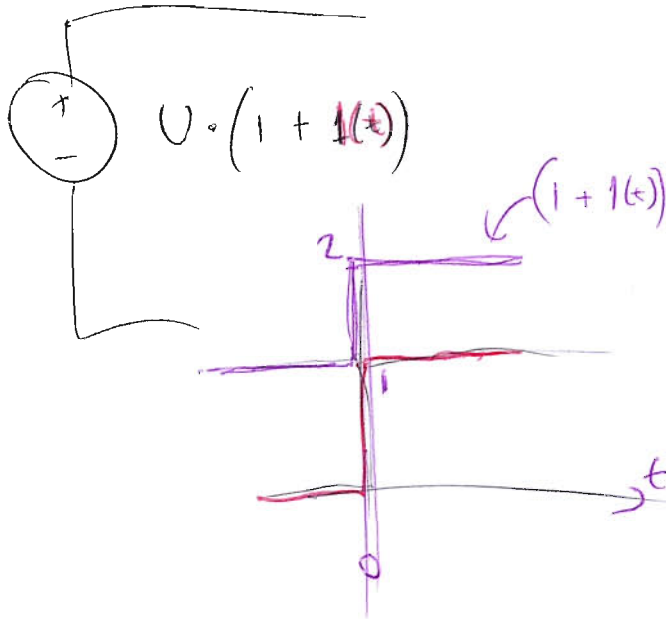

close at time 0



open at time t_0