

EQUILIBRIUM in circuits with C & L

(jämavikt)


(and U, I, R)
(and dependent source)
(and opamp ...)

"the story so far" (since we introduced C & L) —

basics

Last time

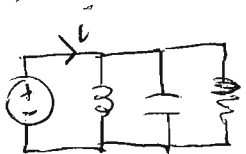
"conveniently" chosen circuits where we can solve currents or voltages quite independently,
eg.



equilibrium and continuity

Now


som

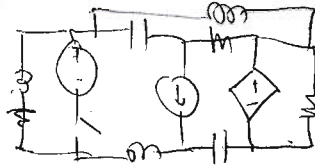

any circuit -- but --
Very limited situations
(just "after long time" or
"immediately after a change")

time functions

final part

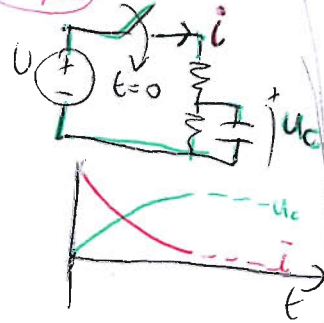


Very limited circuits (else the equations are hard)

Basic principle of equilibrium:

If all sources are constant (dc)

and we wait a long time

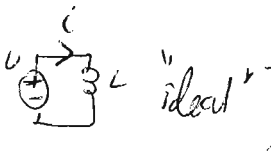and the circuit is ~~realistic~~ stable (not constantly rising like  "ideal")

... then all u & i will settle to constant EQUILIBRIUM VALUES
Jämlikhetläge

and this means $\frac{du}{dt} = 0$, $\frac{di}{dt} = 0$

which means


$$\left. \begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} \right) u = \frac{di}{dt} L = 0L = 0$$

like a SHORTCIRCUIT.


$$\begin{array}{c} \downarrow \\ \text{---} \\ \text{---} \end{array} i = \frac{du}{dt} C = 0 \cdot C = 0$$

like an OPEN CIRCUIT.

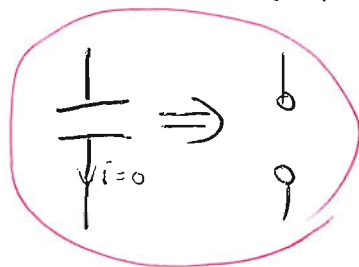
So: to find circuit quantities in the equilibrium state after all sources have been constant for a long time, we just replace



and

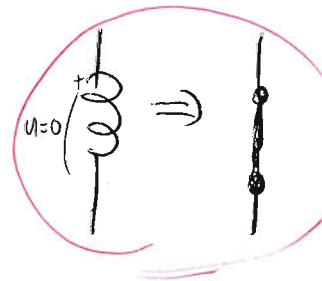

Actually quite easy!
A dc circuit

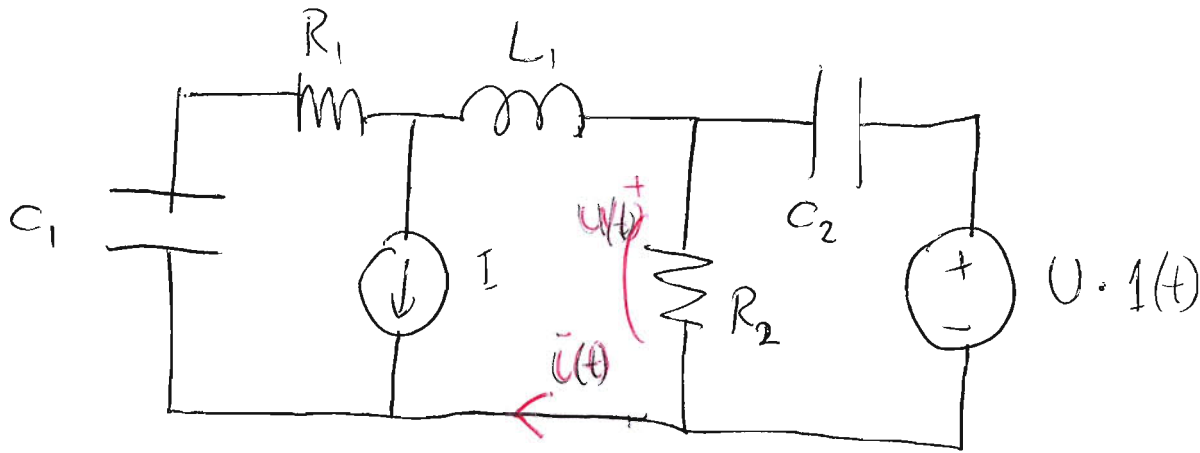


find $u(0^-)$ } " 0^- " means the time just before 0,
 $i(0^-)$ } (eller en syngasjon) and 0^+ is just after.

$u(\infty)$ }
 $i(\infty)$ } i.e. a long time after the change of $U \cdot 1(t)$

When $t = 0^-$ we assume equilibrium (no change has happened at earlier times) ... therefore

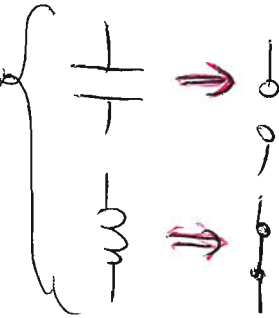
We can also state that $U \cdot I(0^-) = 0$



We redraw with just the relevant information at this time.

$t = 0^-$

$i(0^-) = -I$
 $u(0^-) = -IR_2$

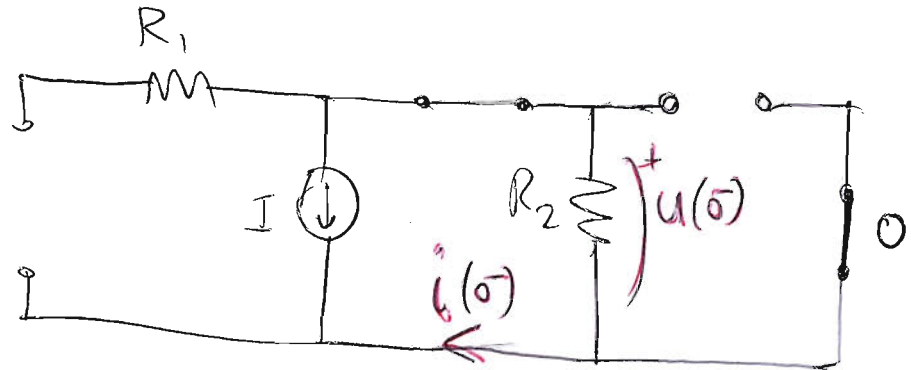


When $t \rightarrow \infty$ we get the same result: the voltage source is now 0 instead of U ; but it is 'isolated' by C_2 (which is open-circuit in equilibrium)

$t \rightarrow \infty$

$i = -I$

$u = -IR_2$

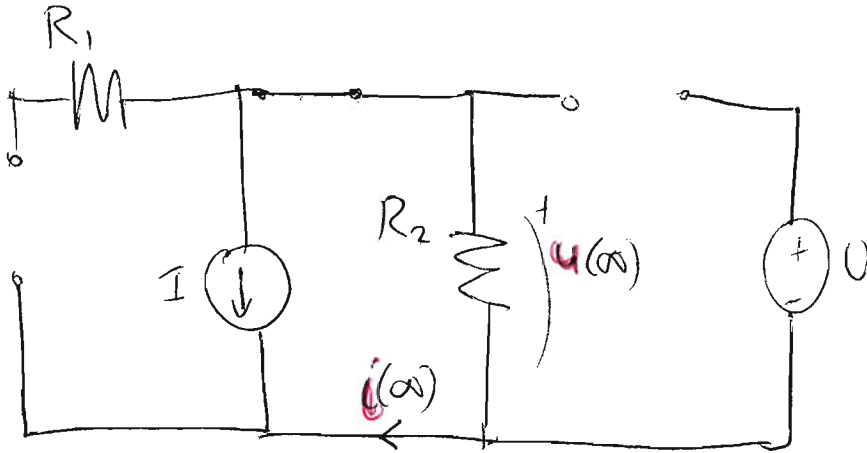

And there's it! Equilibrium, finished.

It's a simple principle, involving an assumption (stable circuit) and using dc circuit skills.

It's needed as a **starting point** for the following topics:
on **CONTINUITY** (e.g. $u(0^+)$ and $i(0^+)$ in our example)
and **TIME FUNCTIONS** (to give an initial condition)

Many E and EM exams have a Q4 or Q5 with equilibrium (and continuity) situations.