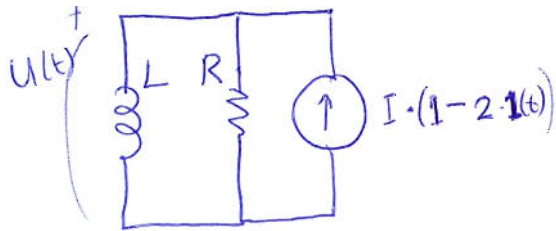


CONTINUITY (the second part of topic 7)

We're still thinking of complicated circuits: many C & L, etc.

Now we go beyond equilibria, to the case where a sudden change has happened to a circuit that had known values of capacitor voltages and inductor currents before the change.


Typically this means there was an equilibrium, and then something happened to disturb it (a switch, or step).



Here we can find $U(0^-)$
 $U(\infty)$ } equilibrium solutions
but what about $U(0^+)$ } ← Now: continuity
or $U(t) \ t > 0$
 $U(zs)$ etc] next week (for C or L components)


CONTINUITY is about CONTINUOUS VARIABLES:

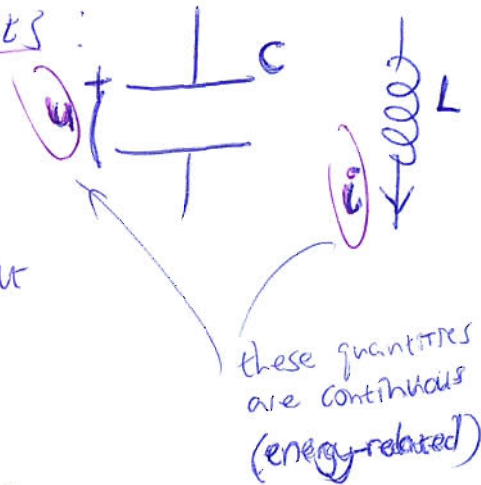We know that these do not change without energy having been moved in or out of the component... it takes time ... So immediately after a change in the circuit, the continuous variables still have the same value (practically) as before the change.



⇒ If we know the values of continuous quantities before a change, then we know the capacitor voltages and inductor currents just after the change, too!

What about the other quantities?

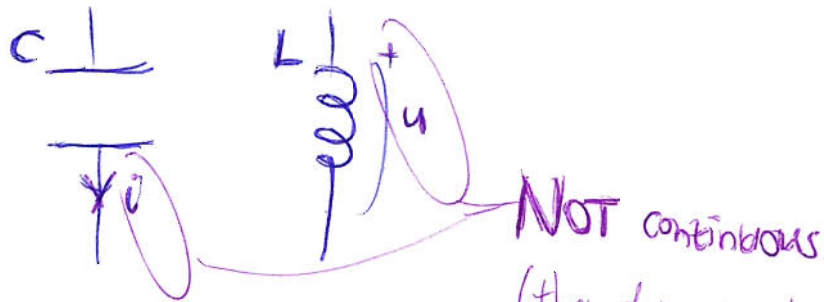

NOT continuous
(they determine how quickly the continuous quantities change: $i_C = \frac{dv_C}{dt}$)



We can't say anything about these based on what they were before the change -- they can jump (step).

But if we solve the rest of the circuit based on the known continuous quantities, we can solve for these.

It sounds like sources !!

- know one quantity fully
- do not know the other — rest of circuit decides

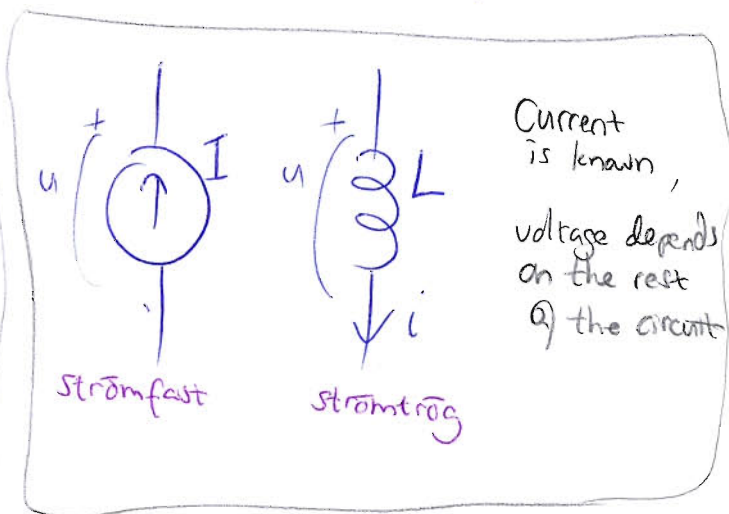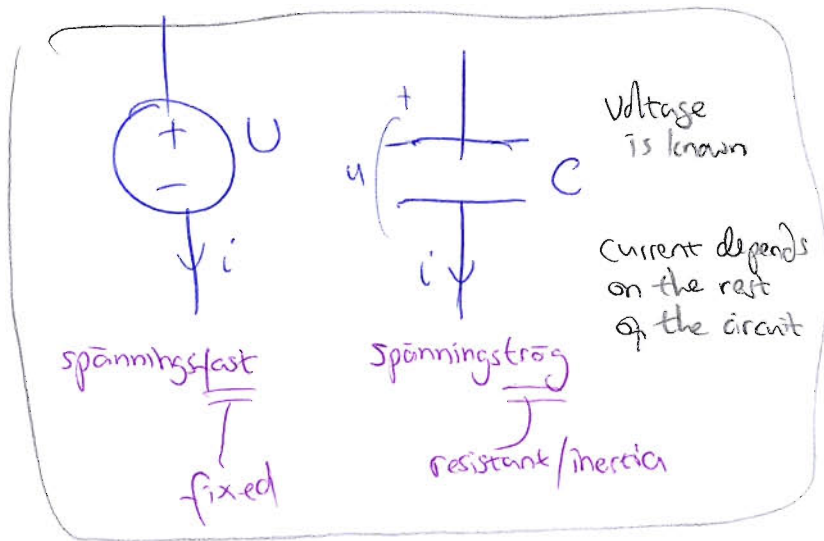"In a short time [just after a change] it's hard to distinguish a big inertia from a fixed object" (i.e. Trägheit from Fartheit)



So we can replace a capacitor charged to U , by a source " U ",
Similarly, we can replace an inductor with current i by a source " i "


* This is only true for the short times before significant change happens !!

Rather like last time (equilibrium) "that's all there is to it".

It's not a hard process to describe, for doing calculations of circuit quantities after a step change, based on continuity.

The difficulties are in the **dc circuit solutions**, and in **carefully keeping track of the continuous variables** that determine the sources that can replace C and L components just after a change.

Example

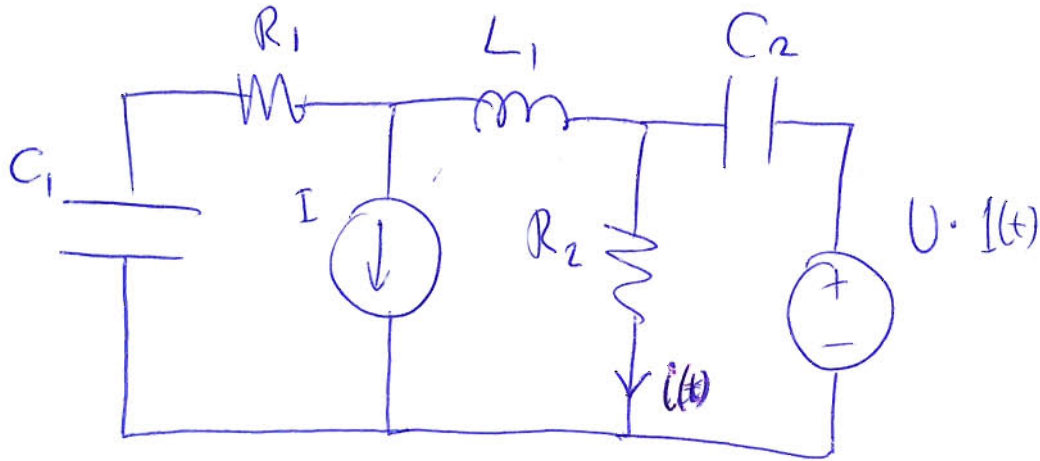


" find $i(0^+)$ " (0^+ is the time just after the step function)



We can't just consider the circuit diagram at $t = 0^+$.
It depends on the stored energy from the earlier times.

for $t = 0^+$ we can draw the circuit with substitutions:


Simplification

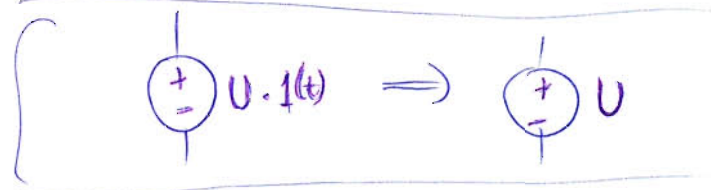

Continuity assumption

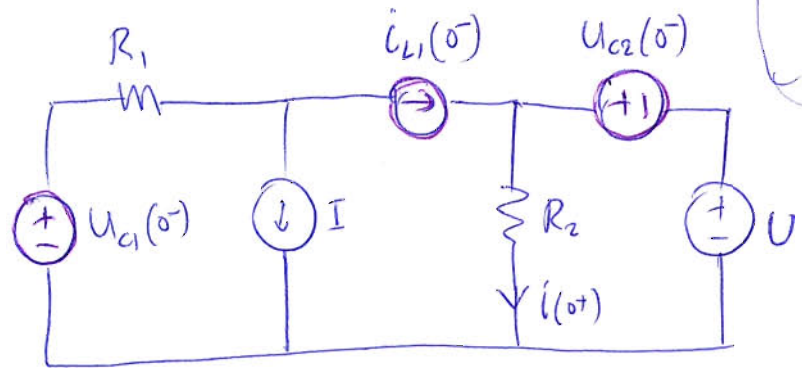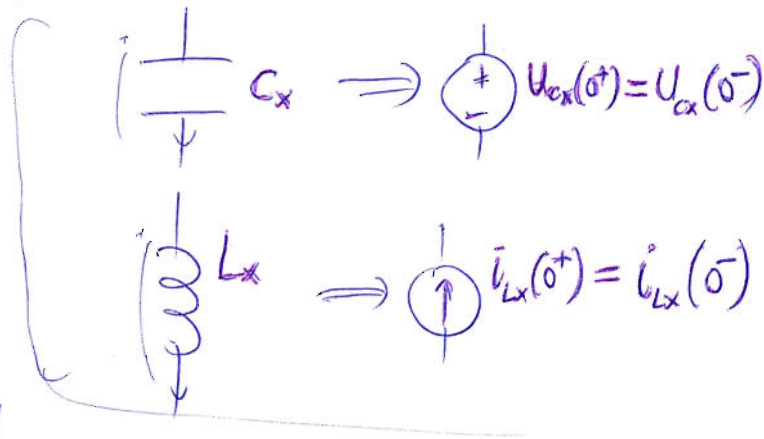

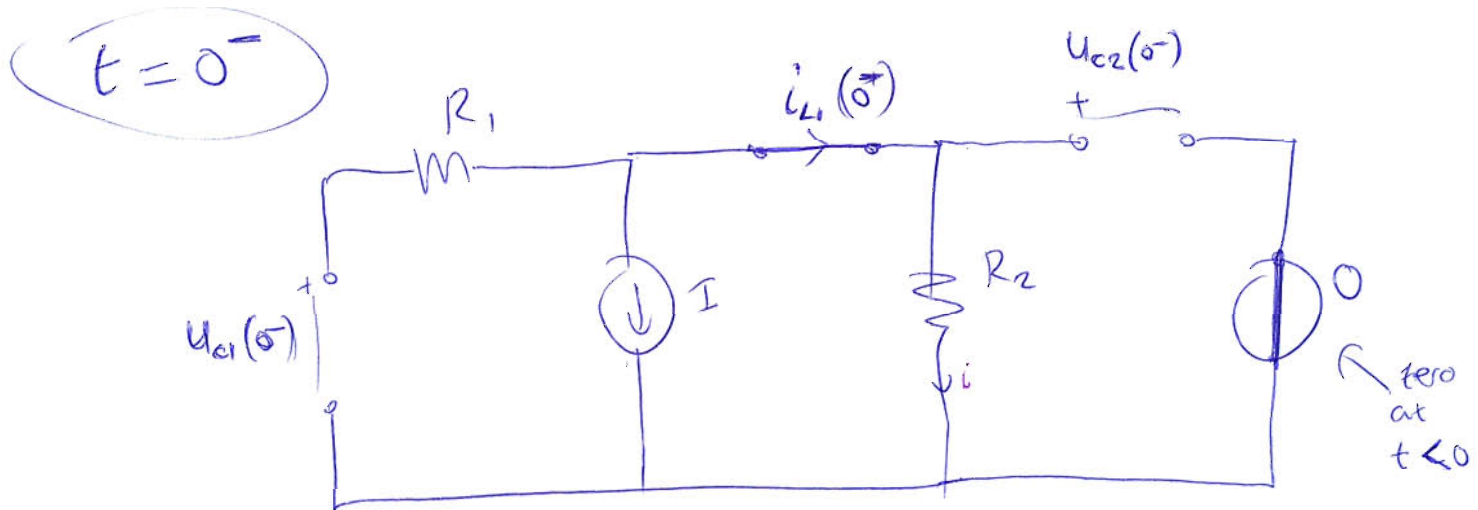Now find the equilibrium values ($t=0^-$) of continuous quantities, which will give the source values (of sources replacing C & L) in the $t=0^+$ circuit.



$$i_{L1}(0^-) = -I \quad (\text{kCL})$$


$$U_{c1}(0^-) = -IR_2 \quad (\text{Ohm, kVL})$$

$$U_{c2}(0^-) = -IR_2 \quad (\text{Ohm, kVL})$$

Actually if we look at the $t=0^+$ circuit carefully we see that only $U_{c2}(0^+)$ is relevant to $i(0^+)$ --- we could have ignored U_{c1} and i_1

Putting this solution back, we get

$$t = 0^+$$

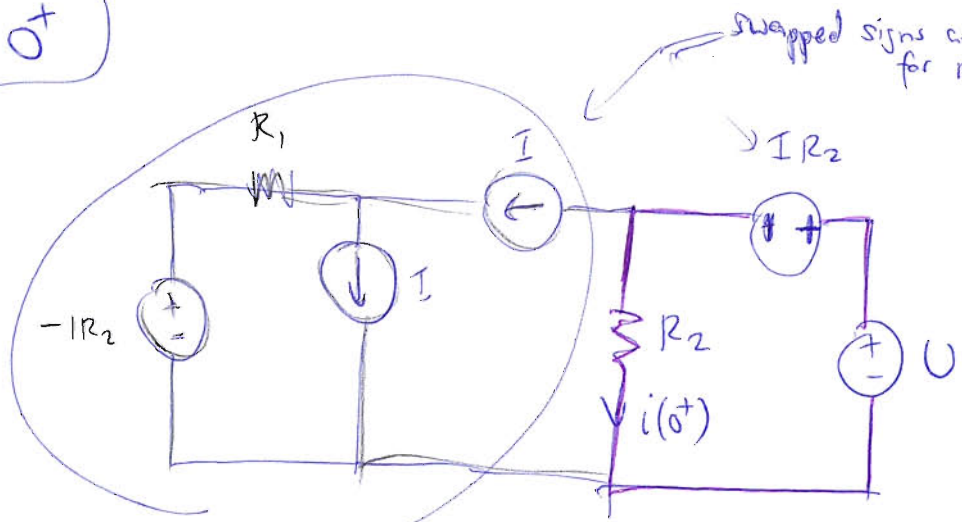

swapped signs and directions for more neatness

not relevant to $i(0^+)$ (as R_2 is given a fixed voltage by the source U and capacitor C)

$$i(0^+) = \frac{U - IR_2}{R_2}$$