


TIME FUNCTIONS (cont.d)

We continue with the "first-order, constant forcing-function" circuits
(only one capacitor or inductor; sources constant except for step/switch at start)

Previously we aimed to find a differential equation, and solve it.
(we noted that a good safe choice is to use the continuous variable of the capacitor or inductor as the equation's dependent variable)

- * **Now** we consider converting all of the circuit except the inductor or capacitor into a **Thevenin** or **Norton equivalent**, then solving this simpler case.
- * We then consider a "quick cheat" method (for these "first order" circuits) of finding { **initial value**, **final value**, **time constant** } and plugging these into a solution.

Does this strike terror into the heart?

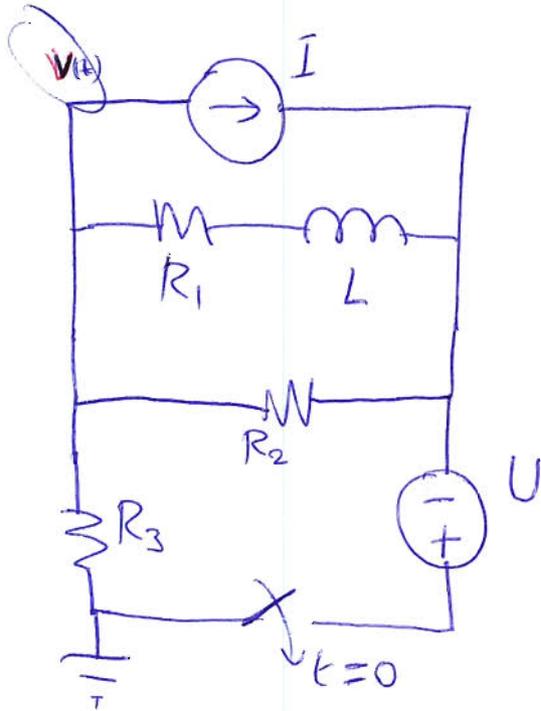


find $V(t)$ for $t > 0$

It probably should cause worry.
It gives nastier expressions
than we would normally
expect in an exam.
(It would be much neater if
we were using numeric values
and a computer)

As usual ... when worried, step back, think of breaking it down, follow established rules you've seen before, ... and redraw (if useful) !!

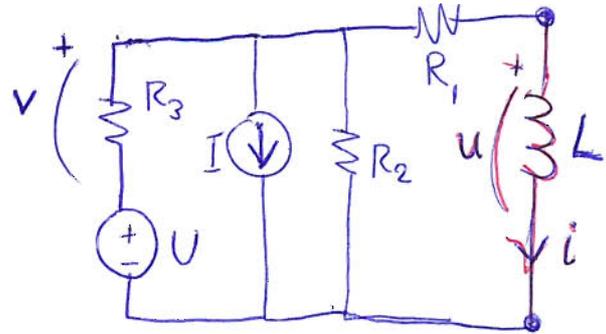
1) let's start by **redrawing** for $t \geq 0$


we'll do this in a way that clearly separates the inductor from the rest of the circuit.



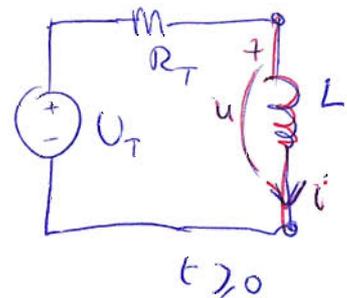
2) Now we'll solve for the continuous variable $i(t)$.

To break the work into easier parts, let's first **convert** the circuit to Thevenin form, for which we can more easily solve $i(t)$.



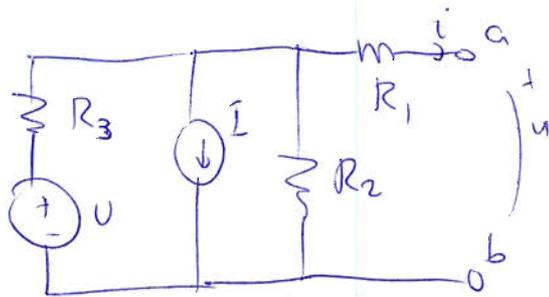


original

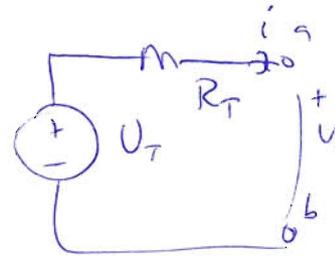


Thevenin equivalent

U_T : (solve open-circuit)

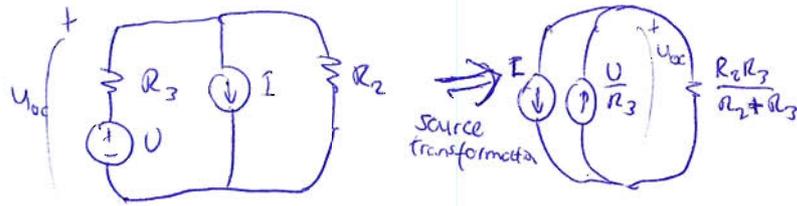


$$U_{oc} = U_T = \frac{\left(\frac{U}{R_3} - I\right) R_2 R_3}{R_2 + R_3} = \frac{UR_2 - IR_2 R_3}{R_2 + R_3}$$

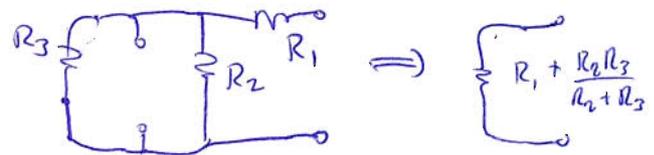R_T : no dependent sources, so easily found by "set all sources to zero"



$$R_T = R_1 + \frac{R_2 R_3}{R_2 + R_3} = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2 + R_3}$$

for the Thevenin circuit,

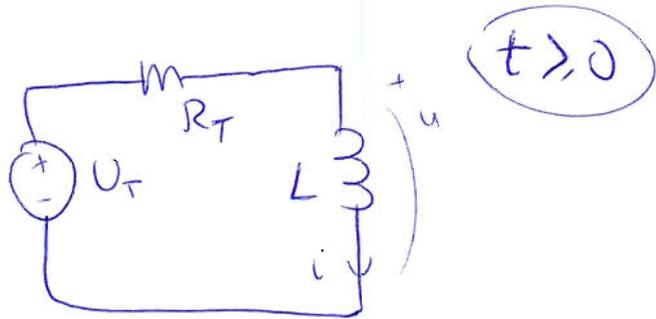

KVL: $U_T = iR_T + \frac{di}{dt} L$

$$\frac{di}{dt} + \frac{R_T}{L} i = \frac{U_T}{L}$$

$$i(t) = \frac{U_T \cancel{L}}{R_T \cancel{L}} + k e^{-\frac{R_T}{L} t}$$


to be determined!

How do we find the initial condition?

The Thevenin circuit was only derived for $t \geq 0$, not $t \leq 0$ (it would in our case be a different U_T and R_T then)

We could make a different Thevenin circuit ... or else just solve the equilibrium directly. \rightarrow ugv

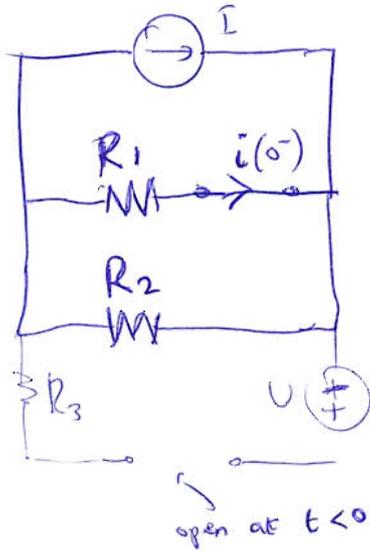In the equilibrium at $t = 0^-$, find the inductor's current



$$\dot{i}(0^-) = -I \frac{R_2}{R_1 + R_2}$$

by continuity $i(0^+) = i(0^-)$

So at $t = 0^+$, use this initial condition to find k

$$\dot{i}(0^+) = -I \frac{R_2}{R_1 + R_2} = \frac{U_T}{R_T} + k e^{-\frac{t R_T}{L}} \stackrel{= 1 \text{ as } t=0}{}$$

Now is the time to insert the real U_T & R_T values.

$$\frac{U_T}{R_T} = \frac{UR_2 - IR_2R_3}{R_1R_2 + R_1R_3 + R_2R_3} = \frac{UR_2 - IR_2R_3}{R_1R_2 + R_1R_3 + R_2R_3}$$

$$\text{So } i(\sigma^+) = \frac{U_T}{R_T} + k \Rightarrow k = \frac{-IR_2}{R_1 + R_2} - \frac{UR_2 - IR_2R_3}{R_1R_2 + R_1R_3 + R_2R_3}$$

Put this into the time function:

$$i(t) = \frac{UR_2 - IR_2R_3}{R_1R_2 + R_1R_3 + R_2R_3} - \left(\frac{UR_2 - IR_2R_3}{R_1R_2 + R_1R_3 + R_2R_3} + \frac{IR_2}{R_1 + R_2} \right) e^{-t/\tau}$$

$[t > 0]$ *important limitation!*


where $\tau = \frac{L}{R_T} = \frac{L(R_2 + R_3)}{R_1R_2 + R_1R_3 + R_2R_3}$

We can check this solution in several ways:

- dimensional analysis
- does it give the expected initial (0^+) and final ($\rightarrow \infty$) values?
- solve in a different way, and compare
e.g. write an ODE directly, without the Thevenin equivalent
In our circuit a single KCL would be a good starting point.

But we're still **not finished!**

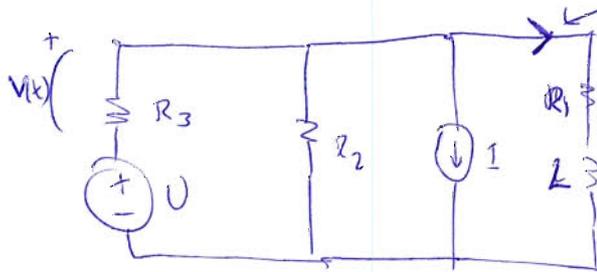We were supposed to find a potential $V(t)$ ($t > 0$),
which is the voltage across R_3



$i(t)$ that we solved on the previous page.

$$\text{KCL} \quad \frac{V}{R_3} + \frac{U+V}{R_2} + I + i = 0 \quad \Rightarrow \quad V(t) = \frac{-UR_3 - (I+i)R_2R_3}{R_2 + R_3}$$

$$V(t) = \frac{-UR_3 - IR_2R_3 - \left(\frac{UR_2 - IR_2R_3}{R_1R_2 + R_1R_3 + R_2R_3} \right) R_2R_3}{R_2 + R_3} + \frac{R_2R_3}{R_2 + R_3} \left(\frac{UR_2 - IR_2R_3}{R_1R_2 + R_1R_3 + R_2R_3} + \frac{IR_2}{R_1 + R_2} \right) e^{-t/\tau}$$

horrible! (and do check for the algebra, critically). But the method was the main point!


In both of these solutions ($v(t)$ and $i(t)$) we saw a general feature/form of the time function:

$$f(t) = p + q e^{-t/\tau}$$


function, such as v or i

(constants)

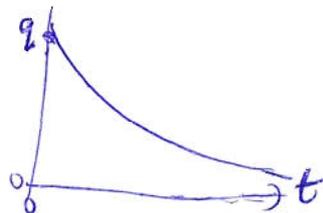
The $q e^{-t/\tau}$ is a decaying exponential!



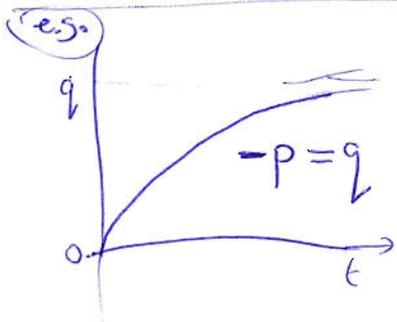We get various possible $f(t)$ from our circuits, all using this basic shape (if they're not "forbidden cases" with impulses or constant rise)



or

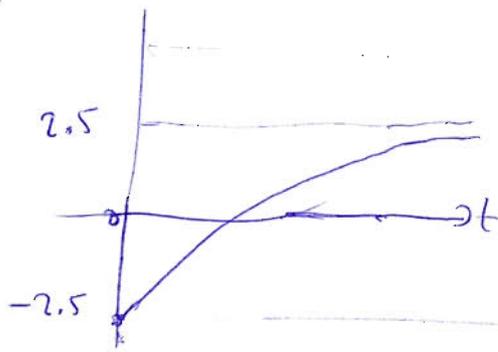

$$p = 2.5$$

$$q = -5$$

highly relevant to lab 3!

We can instead think of an
(instead of the full ODE solution)

{ initial value $f(0^+)$
and final value $f(\infty)$
and time constant τ

Then to build our exponentially changing function from $f(0^+)$ to $f(\infty)$,

$$f(t) = \underbrace{f(\infty)}_{\text{final value}} + \underbrace{\left(f(0^+) - f(\infty)\right)}_{\text{difference between final and initial}} e^{-t/\tau}$$

has quickly the transition happens

How to find values:

$f(0^+)$: usually by equilibrium & continuity





(if it's not a continuous variable, need to solve based on inductor currents and capacitor voltages found at equilibrium)

$f(\infty)$: equilibrium

τ : often easiest by finding Thevenin resistance of the rest of the circuit.


Summary of Thevenin/Norton method, and "curve fitting".

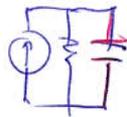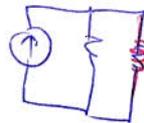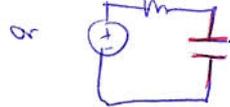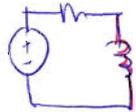It may help to reduce the circuit (at the time period of interest) to its equivalent, then solve a simple case of




(Initial conditions can come from the original circuit's equilibrium).

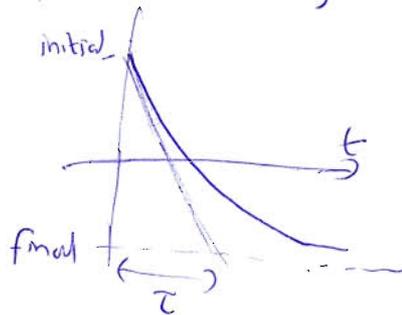
If we just want the solution, for a first-order circuit we can find {initial value, final value, time constant} and fit a decaying exponential to these:



or

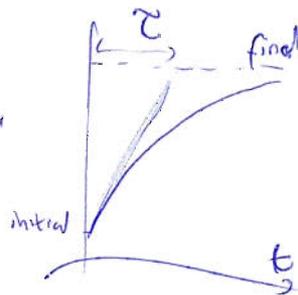

Let's take a simpler, lab-relevant case!

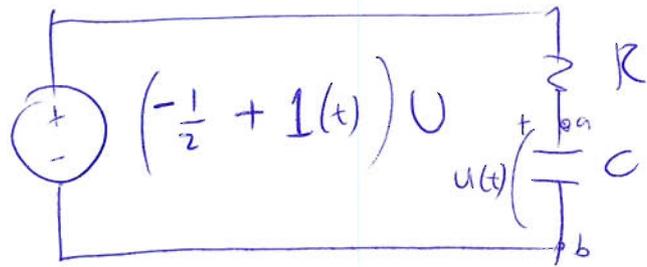

$$\begin{cases} U = 5\text{V} \\ R = 10\text{ k}\Omega \\ C = 100\text{ nF} \end{cases}$$


This is already in Thevenin form.

Determine the initial and final values and time-constant.

Thereby, find an expression for $u(t)$ at $t \geq 0$.

(see lab for more detail!)

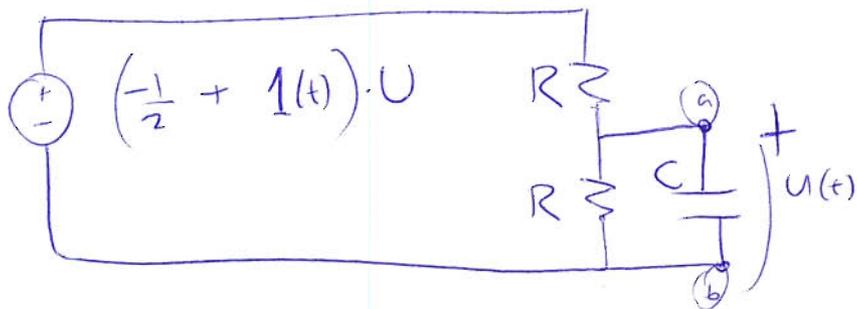Now consider a change (by adding a resistor parallel with the capacitor)



By considering how the Thevenin equivalent has changed at terminals a-b by adding the extra resistor, find the new function of $U(t)$.

(Notice the convenience of thinking in terms of the Thevenin source ... we more easily see how a change in the circuit will affect the time function.)