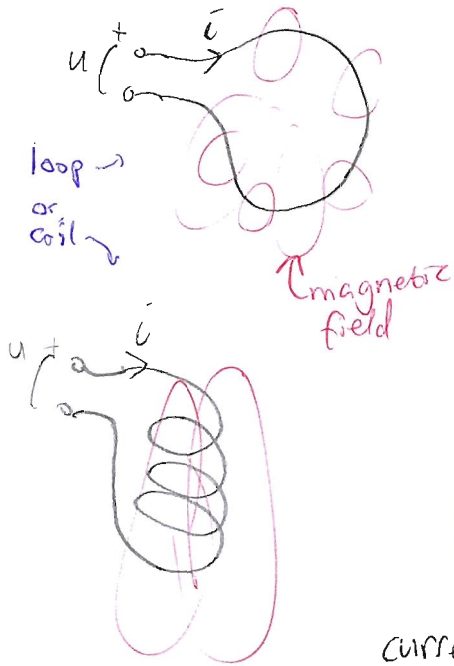


Mutual Inductance and Transformers

What we've seen already: inductors (separately)




$$\frac{u(t)}{di(t)/dt} = L \quad \text{general case (time domain)}$$

$$\frac{u(\omega)}{j\omega i(\omega)} = L \quad \text{phasor}$$


(self) inductance

current \Rightarrow magnetic field
 changing magnetic field \Rightarrow voltage.

What we now study:

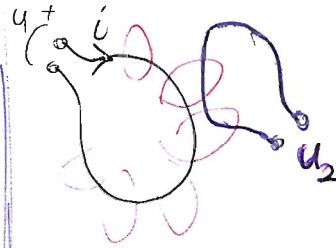

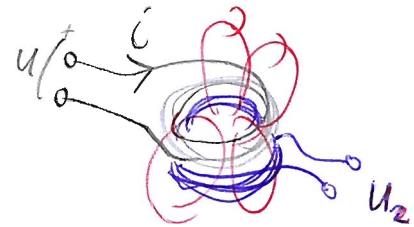Relation of u & i
 between different "coils"
 that have some magnetic linking.




MUTUAL INDUCTANCE


consider two "coils"

↑
could even be
a single loop

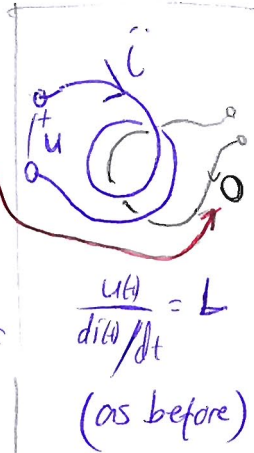if one is "open circuit"
it has no current, so
does not make magnetiz
field, so does not affect
the other ... then
the other is a simple
inductor.



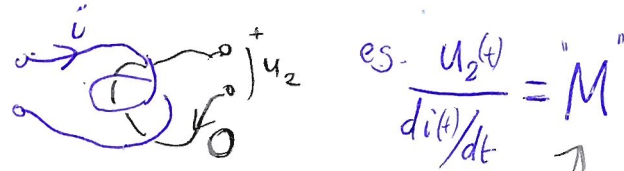-- but, when current flows
in one coil it can induce voltage
in the other due to the
coupled magnetiz field
(linked)




mutual inductance
(Gegenseitiginduktanz)

similar to L , but relates one coil's
current to another's voltage

(sometimes called L_{12})
(between inductors i.e.2)

Definitions for two coupled inductors:

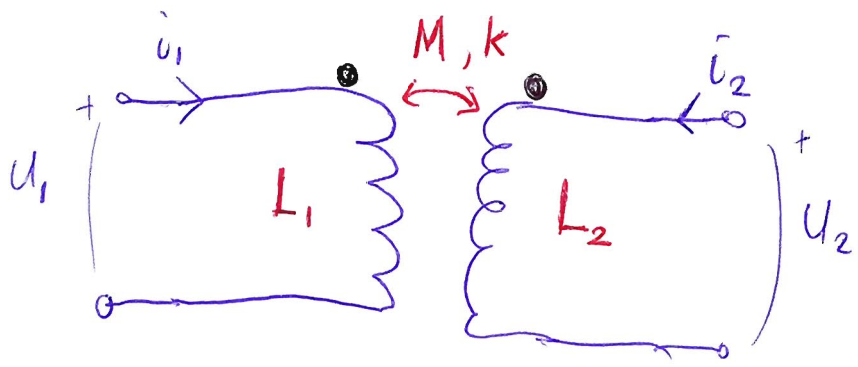

L_1
 L_2 } self inductances
of the individual
coils alone.

M mutual inductance
between the coils

k coupling coefficient
(or factor)

$$U_1 = j\omega i_1 L_1 + j\omega i_2 M$$

$$U_2 = j\omega i_2 L_2 + j\omega i_1 M$$

same
mutual
inductance
for both
directions
 $1 \rightarrow 2, 2 \rightarrow 1$

the part we
have used earlier
with simple inductors

the part due
to the "other"
currents magnetic field

These aren't independent:

$$M = k \sqrt{L_1 L_2}$$

the "dots" show
the relative
directions of the
two coils
(more on this later!)


for a plain inductor, relative direction of u & i definitions determines the sign in the component's equation:



$$u = +j\omega L i$$


passive

convention

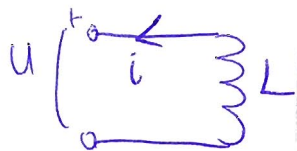

$$u = -j\omega L i \quad \text{active}$$

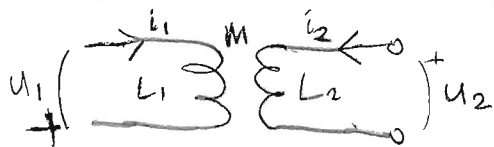The same is true for each separate ^{inductor} (coil) in coupled inductors:



$$u_1 = -j\omega L_1 i_1 + j\omega M i_2$$


$$u_2 = +j\omega L_2 i_2 + j\omega M i_1$$

no dots to show the relative direction

can see from the "convention"

? what are the relative directions of the "coils"

The dots

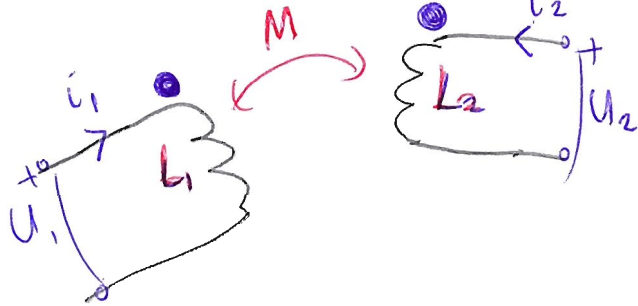


If current i_1 going into the dot on L_1 makes a positive term in the voltage U_1 equation, then current i_2 into the dot on L_2 also makes a positive term in this equation.

$$U_1 = (+) j\omega L_1 i_1 + (+) j\omega M i_2$$

because of directions of i_1 , U_1 (passive)

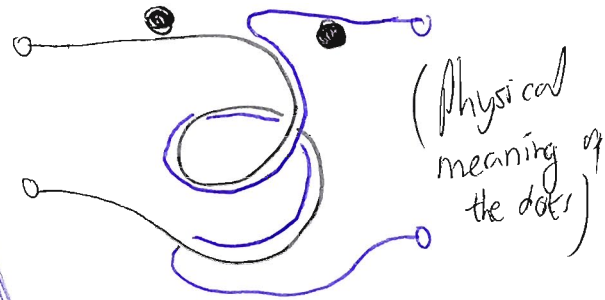same sign because i_1 & i_2 have same direction relative to dots




(Physical meaning of the dots)

In this simple geometry the dots mean "these ends of the inductors are at the same end of the magnetic path"

--- currents into the dots travel the same direction

--- induced voltages have the same direction relative to the dots.

examples with dots

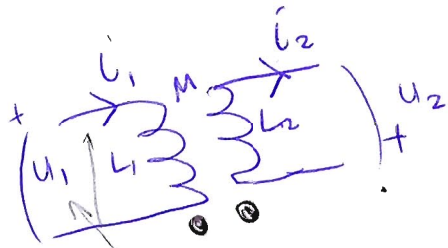

passive convention on L_1


$$u_1 = +j\omega L_1 i_1 - j\omega M i_2$$

passive convention on L_2

$$u_2 = +j\omega L_2 i_2 - j\omega M i_1$$

i_2 goes "in" to the dot on L_2 but i_1 goes "out" of the dot on L_1

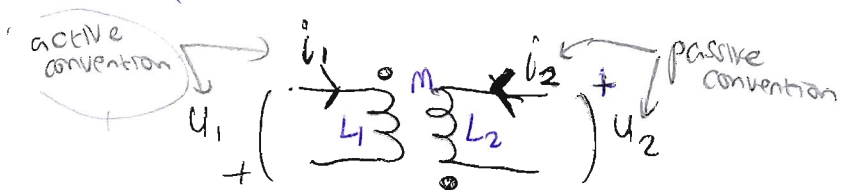sign of i_2 term is opposite to sign of i_1 term



active convention

passive convention

$$u_1 = -j\omega L_1 i_1 + j\omega M i_2$$


$$u_2 = +j\omega L_2 i_2 - j\omega M i_1$$

currents go opposite, relative to the dots, so the signs of the i_2 terms are opposite to those of the i_1 terms

Another way to think of mutual inductance (in terms of already known components)

from the equations:
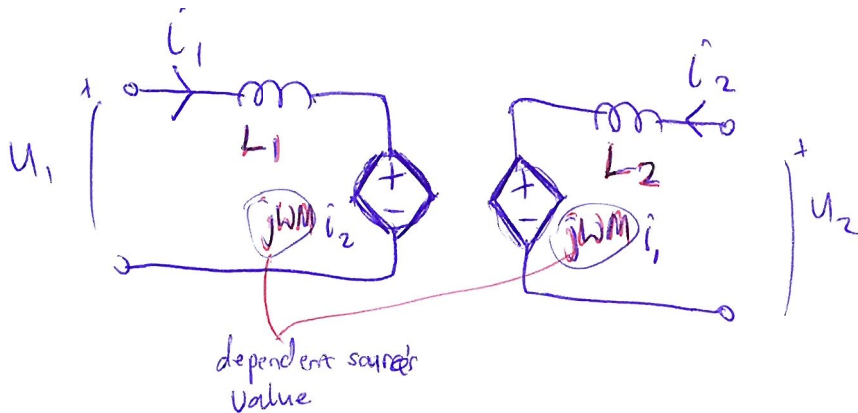
$$\begin{cases} u_1 = j\omega L_1 i_1 + j\omega M i_2 \\ u_2 = j\omega L_2 i_2 + j\omega M i_1 \end{cases}$$



Nothing special --- no great insight --- just another way to think of it, that some people might like.

Calculations with mutual inductances.

If you only know ^{coupling} (k) , L_1 , L_2 then find $\underline{M} = k\sqrt{L_1 L_2}$

As usual: * calmly write all your knowledge of the circuit.

— define any unknown u or i that are needed

— write equation for mutual inductance: $\begin{cases} u_1 = j\omega L_1 i_1 + j\omega M i_2 \\ u_2 = \dots \end{cases}$

— write other circuit equations
(parts outside the mutual inductance)


Careful about signs
dots

* then try to solve
(e check dimensions!)


KVL is often useful, taken at each side of the ~~mutual~~ inductors.
not always

TRANSFORMERS

— the ideal transformer

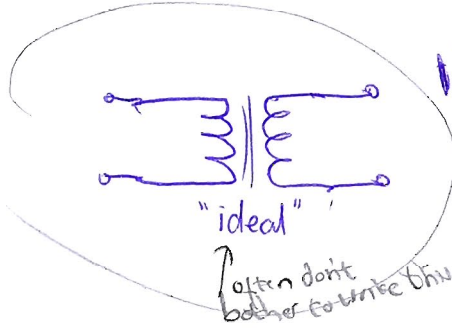


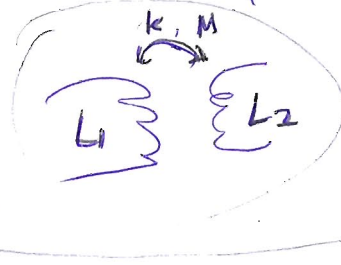Ideal transformer
can be
expressed as
mutual inductors
where



$$\left\{ L_1, L_2 \right\} \rightarrow \infty$$
$$k = 1$$
$$M \rightarrow \infty$$

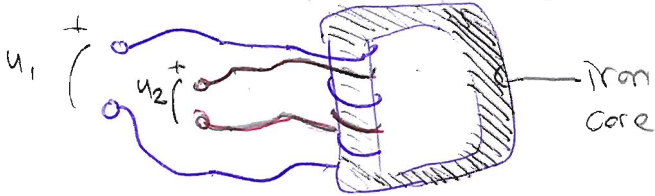- Practically :
- good "magnetic circuit" (iron) — thick, short, high μ_0
 - linking both inductors closely
 - (not much path for flux to "leak" (link one winding but not the other))



describe the number of turns
on each coil as N_1 & N_2

Now, with N_1 "turns" around the magnetic core on one side ("primary") and N_2 on the other ("secondary"), and with each turn linking around all the magnetic field (perfect coupling), ...

Each turn has the same voltage induced (same magnetic field)

$$\rightarrow \frac{U_1}{N_1} = \frac{U_2}{N_2} \Rightarrow \boxed{\frac{U_2}{U_1} = \frac{N_2}{N_1}}$$


Currents must practically cancel each other,

i.e. total current around the magnetic core ≈ 0 , else


the very permeable material would carry big magnetic field

leading to big voltage that forces the currents to reach balance.
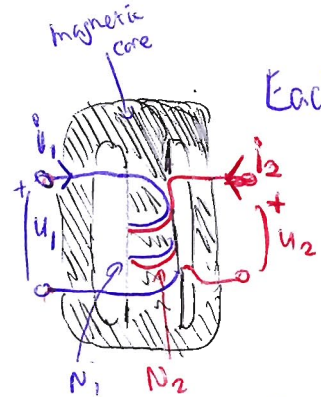
$$i_1 N_1 + i_2 N_2 \approx 0 \Rightarrow \boxed{\frac{i_2}{i_1} = -\frac{N_1}{N_2}}$$



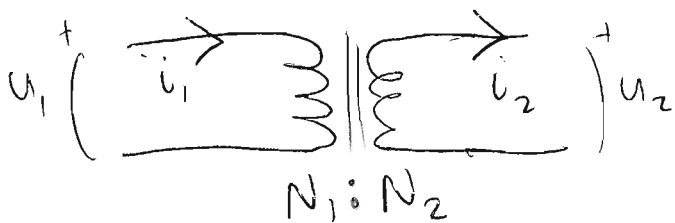Commonly we define one current "out" to avoid the negative:



or define $1:r$ where $r = \frac{N_2}{N_1}$
ratio

$$\frac{U_2}{U_1} = \frac{N_2}{N_1}$$
$$\frac{i_2}{i_1} = \frac{N_1}{N_2}$$

opposite
"scaling"
factors



$U \uparrow \Rightarrow i \downarrow$
(same power
out both sides)

Notice: ideal transformer
is defined purely by its
"turns ratio" e.g. N_2/N_1 ,




\Rightarrow a single number instead of three (L, L_2, M).

If nothing is connected to one side (open) no current flows in the other.

"Transferring across" the transformer.

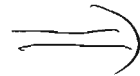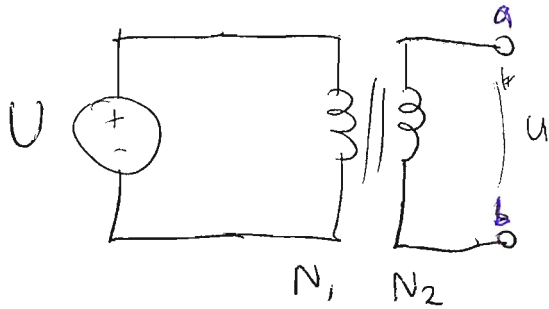


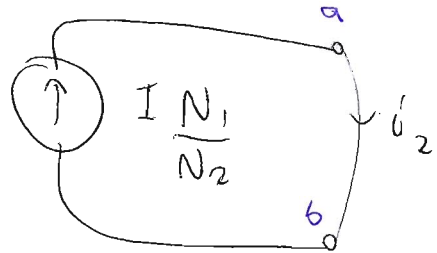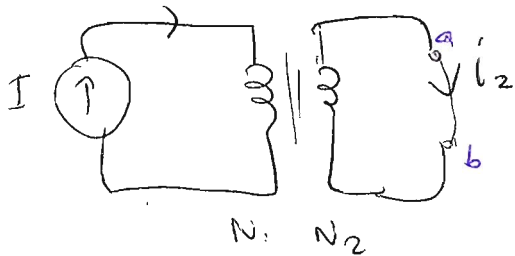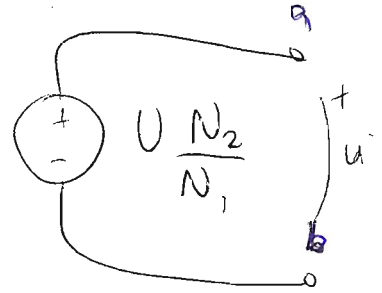seen at
the terminals
 a - b this
is the same as




Transferring an impedance

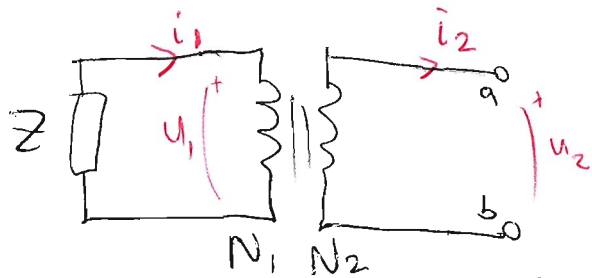First, a derivation based on the same circuits as used with the sources (then we get some negative signs because of having relative directions of u & i in the "active convention").



equivalent
at a-b

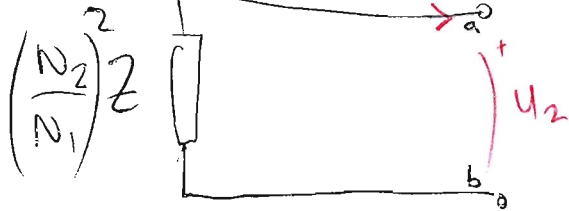


$$\left. \begin{aligned} i_2 &= \frac{N_1}{N_2} i_1 \\ u_1 &= \frac{N_1}{N_2} u_2 \\ i_1 &= \frac{-u_1}{Z} \end{aligned} \right\} \begin{array}{l} \text{transformer equations} \\ \text{Ohm's law (active convention)} \end{array}$$

Putting these together,


$$i_2 = \frac{N_1}{N_2} \cdot \frac{N_1}{N_2} \cdot \frac{-u_2}{Z}$$

$$\boxed{\frac{S_0}{i_2} \cdot \frac{-u_2}{i_2} = \left(\frac{N_2}{N_1}\right)^2 Z}$$

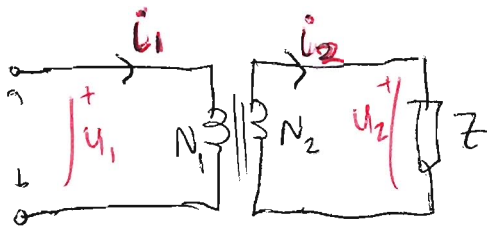alternatively, we can be more conventional, putting the impedance on the right-hand side (classic "load", with source on the left).



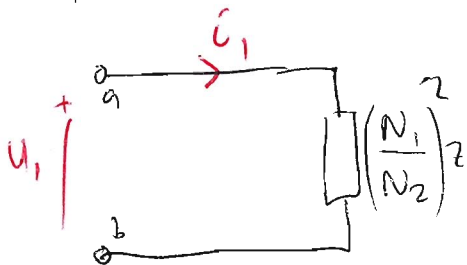equivalent when seen at the terminals a-b.



$$\left. \begin{aligned} i_1 &= \frac{N_2}{N_1} i_2 \\ U_2 &= \frac{N_2}{N_1} U_1 \\ i_2 &= \frac{U_2}{Z} \end{aligned} \right\} \begin{array}{l} \text{transformer} \\ \\ \text{Ohm's law} \end{array}$$




$$i_1 = \frac{N_2}{N_1} \frac{N_2}{N_1} \frac{U_1}{Z}$$

$$\frac{S_1}{U_1} = \left(\frac{N_1}{N_2} \right)^2 Z$$


the impedance that behaves the same as the original impedance did when on the N_2 side of an $N_1:N_2$ transformer.

In some cases (typically when only interested in a solution at one side) it is helpful to "remove" the transformer after converting all components on the other side according to the turns ratio.

Ex. find Thevenin a-b.

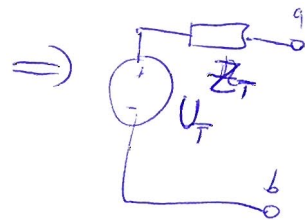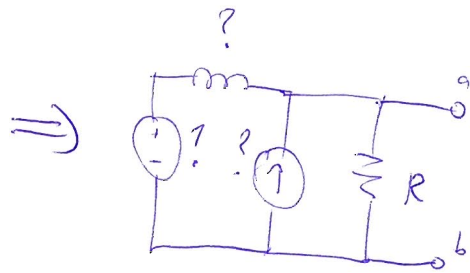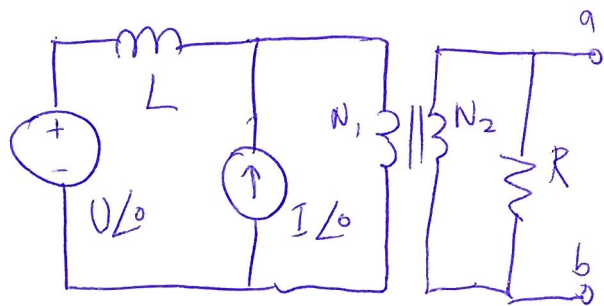



See next.

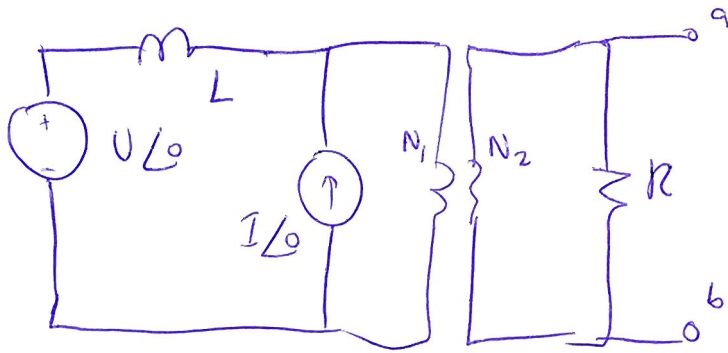

now transfer U, I, L
to the other side:

$$U' = \frac{N_2}{N_1} U \quad I' = \frac{N_1}{N_2} I$$
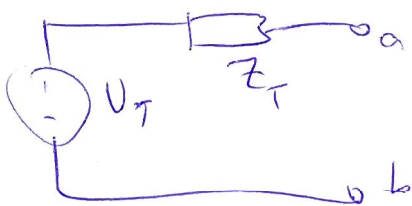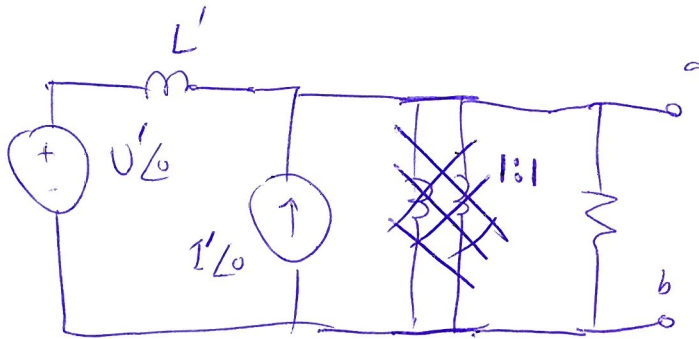
$$j\omega L' = j\omega \left(\frac{N_2}{N_1}\right)^2 L$$



$$U_{ab(oc)} = U_T$$


$$\text{KCL: } \frac{u_x}{R} + \frac{u_x - U'}{j\omega L'} - I = 0$$

$$\Rightarrow u_x = \frac{(U' + j\omega L' I) R}{1 + j\omega L' / R}$$

$$\therefore U_T = \frac{\frac{N_2}{N_1} U + j\omega L I \frac{N_2^2 N_1}{N_1^2 N_2}}{1 + j\omega L \left(\frac{N_2}{N_1}\right)^2 / R}$$

$$Z_T = R \parallel j\omega L' = \frac{j\omega \left(\frac{N_2}{N_1}\right)^2 L R}{R + j\omega \left(\frac{N_2}{N_1}\right)^2 L}$$

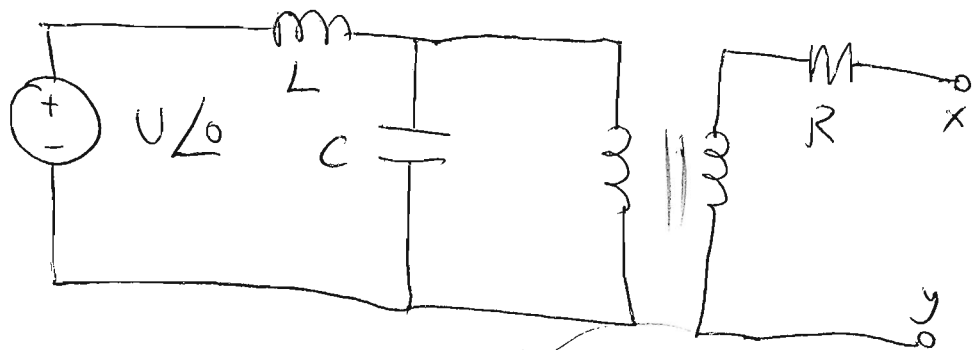Example of transformer solution with "transferring" components.




find Norton equivalent at $x-y$.

$n : 1$
or $N_1 : N_2$


Note that we could equally well have written $1 : n$, in which case the latter solutions would have $\times n$ instead of $\div n$.

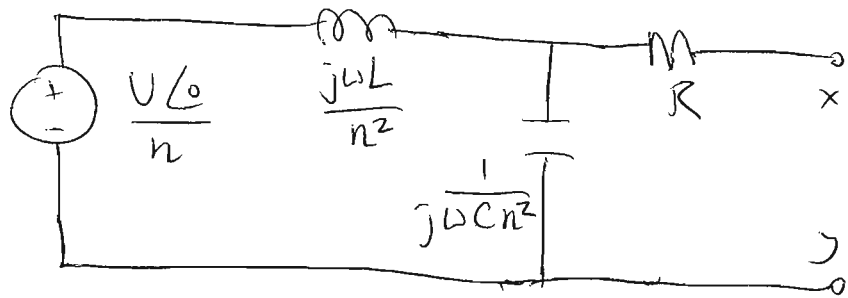We care about what is seen at $x-y$. So let's transfer everything to the right-hand side of the transformer.



(Then solve in the usual way.)

Norton impedance (source set to zero)

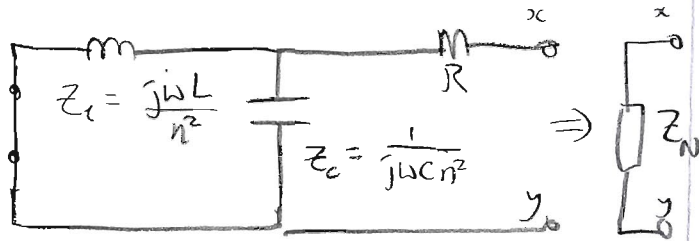


$$Z_N = R + \frac{Z_L Z_C}{Z_L + Z_C} = R + \frac{\left(\frac{j\omega L}{n^2}\right) \left(\frac{1}{j\omega C n^2}\right)}{\frac{j\omega L}{n^2} + \frac{1}{j\omega C n^2}}$$


$$Z_N = R + j \frac{1}{n^2(\omega L - \omega C)}$$

(Note the complexity came from the ac analysis, not from the transformer)

ANSWER

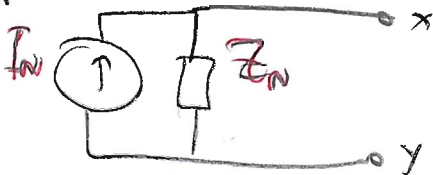

Norton current (short-circuit, x-y)

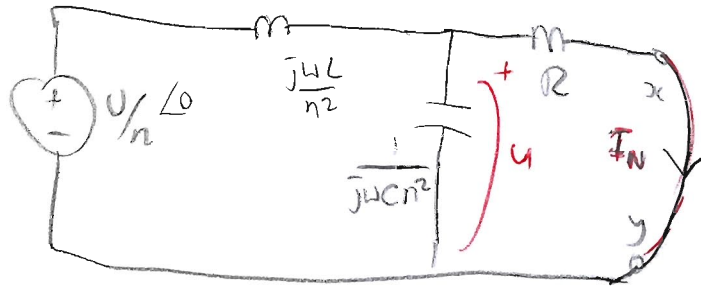

KCL above capacitor:

$$u - \frac{U/n}{j\omega L/n^2} + \frac{u}{1/(j\omega C n^2)} + \frac{u}{R} = 0$$

$$u \left(\frac{n^2}{j\omega L} + j\omega C n^2 + \frac{1}{R} \right) = \frac{U/n}{j\omega L}$$

$$u = \frac{U/n}{j\omega L \left(\frac{n^2}{j\omega L} + j\omega C n^2 + \frac{1}{R} \right)}$$

$$I_N = \frac{u}{R} = \frac{U/n}{nR(1 - \omega^2 LC) + j\omega L/n}$$