


THREE PHASE systems:

Part 2: UNBALANCED conditions

When a three-phase system gets as big as

1 source (3ph)	Very basic.
1 load (3ph)	
1 line (with impedance)	

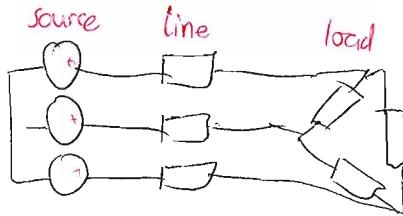We already have 6 impedance components
3 source components
7 or 6 potentials




With all the different angles (phases) this is a lot of calculation if done fully, by hand. (Computers are very useful ...)

That is why we have taken lots of advantage of SYMMETRIES and of STANDARD FORMULAE like $|S| = \sqrt{3} I_{\text{L}} U_{\text{L}}$ to help get solutions, easily.

These were based on the assumption of balance --- which we now REMOVE.


What can make the system unbalanced?

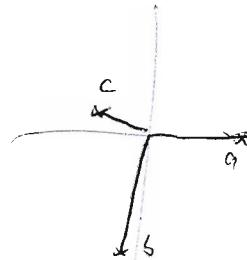{ source has different magnitudes on its phases
has not got 120° phase shift between all phases




{ line or load has different impedances in phases
extreme case: only connected to one or two phases.

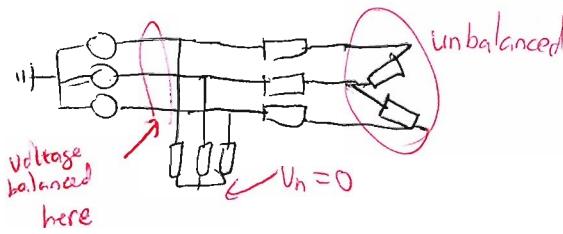One unbalanced component may put the whole system out of balance.
(We might like to estimate if it's enough to matter, for the purpose of our study).



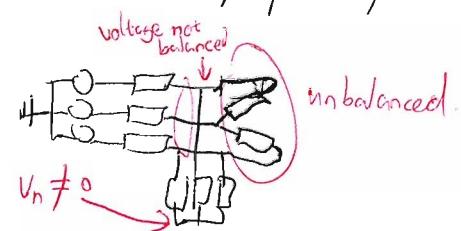In these systems the unbalance only affects the voltage on the right of the line impedance.



Why is it relevant to study this type of situation?

: Ok — many, many studies of three phase systems are based on balanced conditions, especially in high voltage parts where loads are well balanced (lots of load on each phase, averaging out).

But : * faults (short circuit, open circuit, etc) can happen and need to be analysed ... they are often between two lines or from "line to earth" (80% of HV faults is a popular statistic)

* and at the lower parts of the system — like your house — there are many single phase loads connected to the three phase system --- they are seldom balanced,

Methods for handling unbalanced calculations.

Bruke for
(Sledgehammer)
often good
if using a
computer

- ① no reliance on symmetry or on standard formulae of balanced cases
 - ② just calculate with each phase of each source, load or line treated as a separate component
 - ③ we can do this for tiny systems
 - ④ bigger systems need computer help
- { phasor calculation of
every node potential and
every current


Hybrid

- ① identify the unbalanced parts in the system.
- ② try to find a way to solve "most" of the problem by balanced calculation with a smaller unbalanced calculation to take care of the unbalance
- ③ not always possible or useful.

Other

- ④ famous traditional method "symmetric components" involves a transformation of phase -> line quantities and impedances, which usually simplifies calculation (no more on that here --- less necessary in the days of computers, but a useful concept)

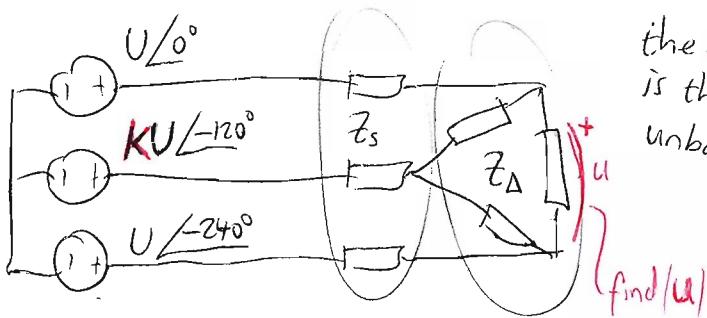
Examples of hybrid-type methods that do work.



the source
is the only
unbalance


replace it with
two superposition
states!

calculate each
and add the
results

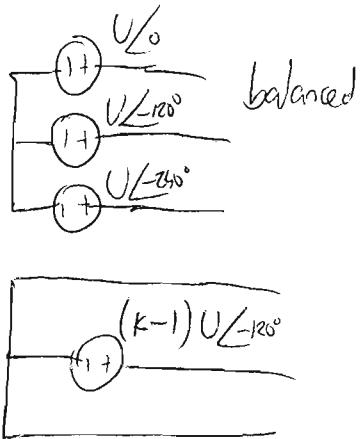

the unbalanced
part


find $|i_b|$ or i_b (if we feel cruel)

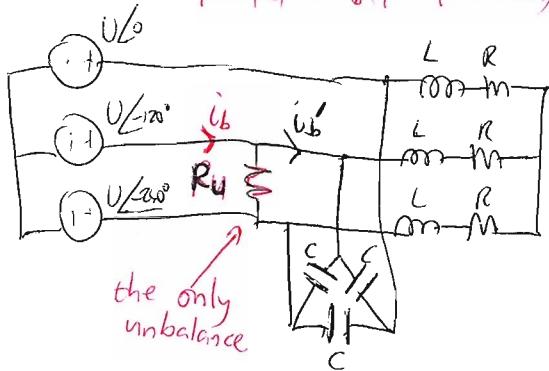

The unbalanced part is connected to an ideal voltage source. So it doesn't affect the voltage applied to the other loads. We can do balanced calculation for i'_b then add (as phaser) the current through R_u .

Example

(next page)

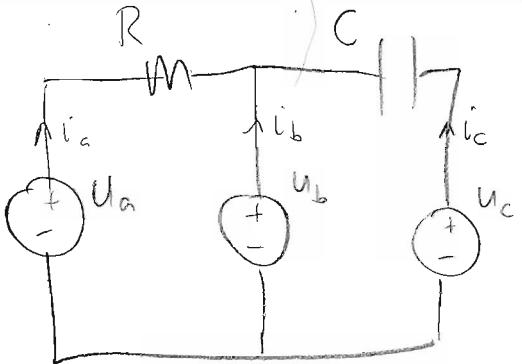

$U_{a,b,c}$ are a balanced 3phase source with line voltage $\sqrt{3}U$ and phase rotation abc

Find the complex power in rectangular form, delivered by each of the components:

$S_a \quad S_b \quad S_c \quad S_R \quad S_C$

(The actual angles don't matter to the power as long as the relative angles are correct ... remember $S = U \cdot i^*$ so any shift of all angles in the circuit is cancelled by affecting U and i^* oppositely.)

Let's call phase a's angle θ .

$$\text{Then } U_a = U \angle 0^\circ \quad U_b = U \angle -120^\circ \quad U_c = U \angle 120^\circ$$

If we find the three currents, we can find the complex powers.

$$i_a = \frac{u_a - u_b}{R} = U \frac{(1\angle 0^\circ - 1\angle -120^\circ)}{R} = \frac{\sqrt{3}U \angle 30^\circ}{R}$$

The complex power into the resistor is $S = |i_a|^2 R = \frac{3U^2}{R}$,
 But we were asked for complex power delivered by each component.

$$\boxed{S_R = -\frac{3U^2}{R}}$$

The complex power from source u_a is $S_a = u_a \cdot i_a^*$ (check the directions of the voltage and current)

$$S_a = U \angle 0^\circ \cdot \frac{\sqrt{3}U \angle -30^\circ}{R} = \frac{\sqrt{3}U^2}{R} \angle -30^\circ$$

$$= \frac{\sqrt{3}U^2}{R} (\cos(-30^\circ) + j \sin(-30^\circ)) = \frac{3}{2} \frac{\sqrt{3}U^2}{R} + j \frac{-1}{2} \cdot \frac{\sqrt{3}U^2}{R}$$

$$\boxed{S_a = \frac{3U^2}{2R} - j \frac{\sqrt{3}U^2}{2R}}$$

Let's take i_c next (it's simpler than i_b).

$$\begin{aligned} \text{KVL} \quad i_c &= \frac{U_c - U_b}{\frac{1}{j\omega C}} = j\omega C U \left(1 \angle -240^\circ - 1 \angle -120^\circ \right) \\ &= j\omega C \sqrt{3} U \angle 90^\circ \\ &= \omega C \sqrt{3} U \angle 180^\circ \end{aligned}$$

$$\begin{aligned} \text{complex power into capacitor} &= |i_c|^2 Z_c = |i_c|^2 \frac{1}{j\omega C} \\ &= \frac{3 \omega^2 C^2 U^2}{j\omega C} = -j 3 U^2 \omega C \end{aligned}$$


\therefore Complex power from capacitor:

$$S_C = +j 3 U^2 \omega C$$

P
bisc

Simplifying $1 \angle 240^\circ - 1 \angle -120^\circ$

You could draw it:

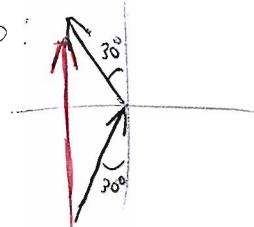

$$\begin{aligned} \text{Or write as } &\cos(-240^\circ) + j \sin(-240^\circ) \\ &- \cos(-120^\circ) - j \sin(-120^\circ) \end{aligned}$$

Or use our rule that for phasors of magnitude 1 and relative angle of 120° ,

$$1 \angle \alpha - 1 \angle \alpha - 120^\circ \Rightarrow \sqrt{3} \angle \alpha + 30^\circ$$

$$1 \angle \alpha - 1 \angle \alpha + 120^\circ \Rightarrow \sqrt{3} \angle \alpha - 30^\circ$$

from which, if $\alpha = -240^\circ$ (or $+120^\circ$)

$$1 \angle \alpha - 1 \angle \alpha + 120^\circ = \sqrt{3} \angle \alpha - 30^\circ$$

$$1 \angle -240^\circ - 1 \angle -120^\circ = \sqrt{3} \angle -270^\circ = \sqrt{3} \angle 90^\circ$$

Delivered by source C,

no imaginary part, so $i_c^* = i_c$

$$S_c = U_c \cdot i_c^* = U \angle -24^\circ \cdot \omega C \sqrt{3} U \angle 180^\circ = \sqrt{3} U^2 \omega C \angle -60^\circ$$

↑
Node C

$$S_c = \sqrt{3} U^2 \omega C \left(\cos(-60^\circ) + j \sin(-60^\circ) \right) = \sqrt{3} U^2 \omega C \left(\frac{1}{2} - j \frac{\sqrt{3}}{2} \right)$$

$$S_c = \frac{\sqrt{3}}{2} U^2 \omega C - j \frac{3}{2} U^2 \omega C$$

Now to source b: by KCL, $i_b = -i_a - i_c = -\frac{\sqrt{3} U}{R} \angle 30^\circ - \omega C \sqrt{3} U \angle 180^\circ$

$$= \frac{\sqrt{3} U}{R} \angle -150^\circ + \omega C \sqrt{3} U \angle 0^\circ$$

$$S_b = U_b \cdot i_b^*$$

We must be careful with what steps to take, to get a solution not too full of $\tan^{-1}()$ etc!

$$S_b = U \angle -120^\circ \cdot \left(\frac{\sqrt{3}U}{R} \angle -150^\circ + wC\sqrt{3}U \angle 0^\circ \right)^*$$

$$= U \angle -120^\circ \cdot \left(\frac{\sqrt{3}U}{R} \angle +150^\circ + wC\sqrt{3}U \angle 0^\circ \right)$$

$$= \sqrt{3}U^2 \left(\frac{1}{R} \angle 30^\circ + wC \angle -120^\circ \right) \quad \text{--- then split into cos+jsin components!}$$

$$= \sqrt{3}U^2 \left(\frac{\sqrt{3}}{2} \frac{1}{R} + j \frac{1}{2} \frac{1}{R} - \frac{1}{2} wC - j \frac{\sqrt{3}}{2} wC \right) = \frac{\sqrt{3}}{2} U^2 \left(\frac{\sqrt{3}}{R} - wC + j \left(\frac{1}{R} - \sqrt{3}wC \right) \right)$$

$$S_b = \frac{\sqrt{3}}{2} U^2 \left(\frac{\sqrt{3}}{R} - wC \right) + j \frac{\sqrt{3}}{2} U^2 \left(\frac{1}{R} - \sqrt{3}wC \right)$$

Because we had a balanced system, and phase U_a was at angle zero, and the capacitor's current was real, our angles were convenient multiples of 30° . In other cases it might not be so easy! (Leave with \cos , \tan etc.)

(Now we can check that


$$S_a + S_b + S_c + S_R + S_C = 0$$

— "conservation" of reactive power ...)

Example

(next page)

Example ('everyday' example!)

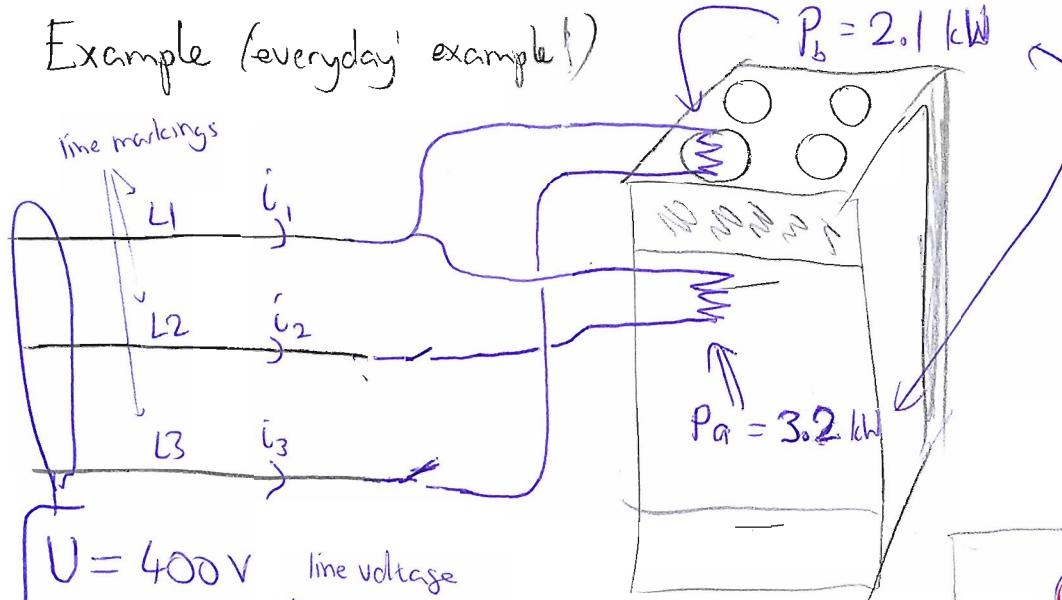

$U = 400 \text{ V}$ line voltage
(linnudspänning)
3ph supply

This shows an electric cooler in which two elements are switched on. They are connected between different pairs of lines: 'a' is $L1 \rightarrow L2$ & 'b' is $L1 \rightarrow L3$.

The powers show the power at "rated voltage" 400 V.
The elements can be treated as resistors.

a) find $|i_b|$
 $|i_c|$
 $|i_a|$

b) assume the source is the following:


$$\frac{U}{\sqrt{3}} \angle 90^\circ \text{ --- } L_1$$

$$\frac{U}{\sqrt{3}} \angle -30^\circ \text{ --- } L_2$$

$$\frac{U}{\sqrt{3}} \angle 150^\circ \text{ --- } L_3$$

find Δi_a

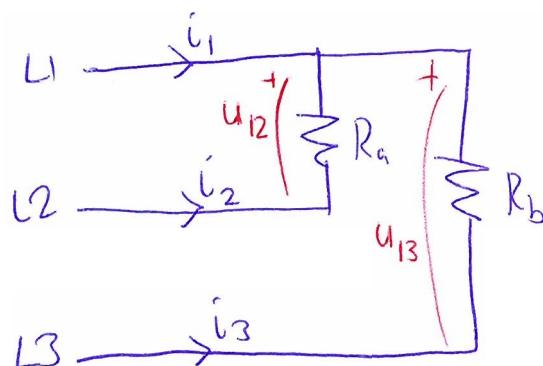first, write the situation more like an "idealised circuit":



$$R_a = \frac{U^2}{P_a}, \quad R_b = \frac{U^2}{P_b}$$

$$|U_{12}| = |U_{13}| = U = 400\text{V}$$

Without thinking about angles, we can find two of the current magnitudes, based on knowing the voltage magnitudes across the resistors:

$$|i_2| = \frac{|U_{12}|}{R_a} = \frac{U}{R_a} = \frac{U P_a}{U^2} = \frac{P_a}{U}$$

$$|i_3| = \frac{P_b}{U} \text{ (by the same method)}$$

} obvious if we think a little:
 $P = |U||i|$ for a resistor,

$$\text{By KCL, } i_1 = -i_2 - i_3$$

$$|i_1| = |i_2 + i_3|$$

phasor sum is needed:


These currents have different angles; we cannot just add magnitudes: $|i_1| \neq |i_2| + |i_3|$

Task D defines specific angles. for task C let's ignore that, and make our own choice of the definition of reference angle; only the relative angles are important for finding the requested magnitudes.

We'll define line voltage U_{12} at zero angle: $\angle U_{12} = 0^\circ$

Assume 'abc' (1,2,3) phase rotation (it doesn't actually affect the resulting magnitudes in our case, as the impedances are the same type, resistive.)

Then:

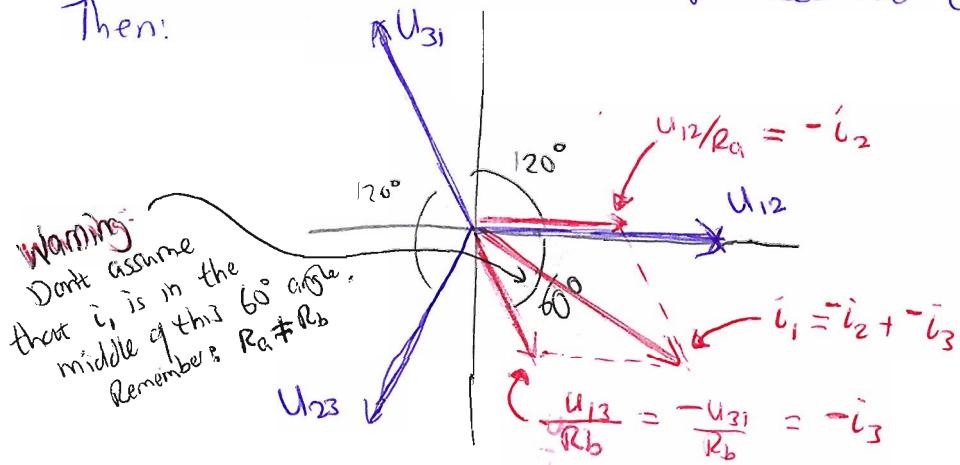

Having defined $\angle U_{12} = 0^\circ$, the next line voltage is $\angle U_{23} = -120^\circ$, then $\angle U_{31} = -240^\circ$

We must be careful to draw the currents in the right directions: careful about the signs

Our task is therefore to find:

$$\begin{aligned} i_1 &= \frac{U}{R_a} \angle 0^\circ + \frac{U}{R_b} \angle -60^\circ = \frac{U}{R_a} + \frac{U}{R_b} \left(\cos(-60^\circ) + j \sin(-60^\circ) \right) \\ &= \frac{U}{R_a} + \frac{U}{2R_b} - j \frac{\sqrt{3}U}{2R_b} \end{aligned}$$

from which $|i_1| = U \sqrt{\left(\frac{1}{R_a} + \frac{1}{2R_b}\right)^2 + \left(\frac{\sqrt{3}}{2R_b}\right)^2}$

Easier by computer:

$$U = 400, P_a = 3.2e3, P_b = 2.1e3, R_a = U \times 2 / P_a, R_b = U \times 2 / P_b$$

$$U_a = U / \sqrt{3}, U_b = U_a / \exp(j \times 2 \times \pi / 3), U_c = U_b / \exp(j \times 2 \times \pi / 3)$$
$$i_{1\text{mag}} = \text{abs}((U_a - U_b) / R_a + (U_a - U_c) / R_b)$$

Putting in the numbers:

$$|i_1| = 11.6 \text{ A}$$

$$|i_2| = 8.0 \text{ A}$$


$$|i_3| = 5.3 \text{ A}$$

(b) Now we find $\angle i_1$. In this part, (b), the angles in the circuit have been specified by defining the phase voltage phasors of a Y connected source. \Rightarrow from this we see that $\angle u_{12} = +120^\circ$.

In part (a) we chose a different definition, $\angle u_{12} = 0^\circ$. Let's initially use that, to find $\angle i_1$ from the phasor diagram in part (a). Then we can shift the angle by $+120^\circ$ to fit the definition used here in part (b). (It's convenient to have the current on the real axis)

$$\begin{array}{l} \text{Given } \frac{u_{12}}{R_a} = \frac{u_{10}}{R_a} \\ \text{and } \frac{u_{13}}{R_b} = \frac{u_{10} - u_{12}}{R_b} = \frac{u_{10}}{R_b} - \frac{u_{12}}{R_b} = \frac{u_{10}}{R_b} \end{array}$$
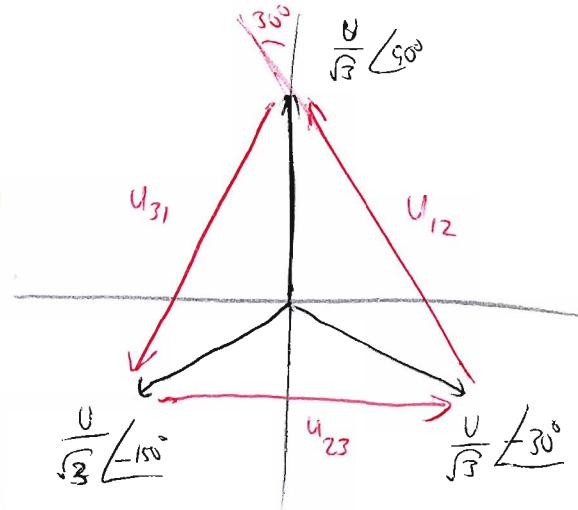
$$\begin{aligned} \sqrt{\frac{u_{12}}{R_a}^2 + \frac{u_{13}}{R_b}^2} &= \sqrt{\frac{1}{R_a^2} + \frac{1}{R_b^2}} \\ &= \tan^{-1} \left(\frac{\sqrt{3} \cdot \frac{1}{R_b}}{\frac{1}{R_a} + \frac{1}{2R_b}} \right) = -\tan^{-1} \left(\frac{\sqrt{3} R_a}{R_a + 2R_b} \right) \end{aligned}$$



$$\begin{aligned} \text{So } i_1 &= \angle u_{12} = \approx 97^\circ \\ &= 120^\circ - \tan^{-1} \left(\frac{\sqrt{3} R_a}{R_a + 2R_b} \right) \end{aligned}$$


in the angle reference specified in part b.

in our arbitrary choice of angle

Example

(next page)

Example

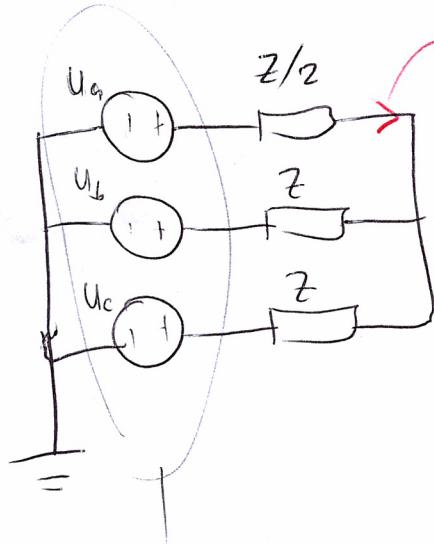

find
 $|i_a|$


We can assume any angle reference for the three-phase source. (e.g. let's say $U_a = U \angle 0^\circ$)

Then assuming the default phase rotation abc,

$$U_b = U \angle -120^\circ \quad \text{and} \quad U_c = U \angle +120^\circ \quad (\text{or } U \angle -240^\circ)$$

If there were a neutral conductor (of no impedance)

this would be easy :

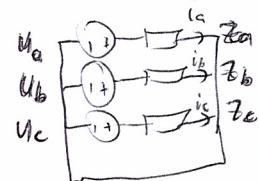


$$i_a = \frac{U_a}{Z_a}$$

But there isn't !
The unbalanced load means
that the load's 'neutral'
point has not the same
potential as the source's
neutral.

One method. Direct solution of the circuit

(Not starting with 3ph simplifications or separating balance/unbalance)

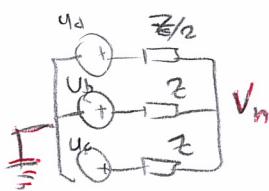Call the potential V_n at the load-neutral (the "star-point" - node at the right).
Then KCL gives:



$$\frac{U_a - V_n}{Z/2} + \frac{U_b - V_n}{Z} + \frac{U_c - V_n}{Z} = 0$$

$$\cancel{\frac{2U_a}{Z}} + \cancel{\frac{U_b}{Z}} + \cancel{\frac{U_c}{Z}} = \cancel{\frac{4V_n}{Z}}$$

$$V_n = \frac{U_a}{4} + \cancel{\frac{1}{4}(U_a + U_b + U_c)} \\ = 0 \text{ as it's balanced 3phase}$$

Ohm's Law:

$$i_a = \frac{U_a - V_n}{Z/2} = \frac{U_a - \frac{U_a}{4}}{Z/2} = \frac{\frac{3}{4}U_a}{Z/2} = \frac{3}{2} \cdot \frac{U_a}{Z}$$


$$\boxed{\text{So } |i_a| = \frac{3U_a}{2Z}}$$

arbitrarily
chosen angle
of Phase a
voltage


Another method.

being cunning (fig, slug)


Note that:

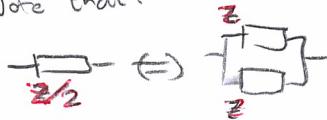



or more generally,

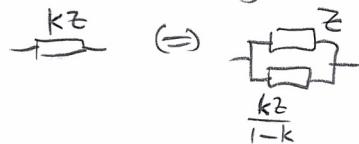

We can draw our circuit as:

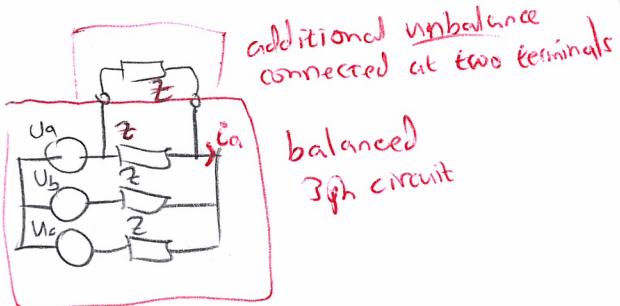


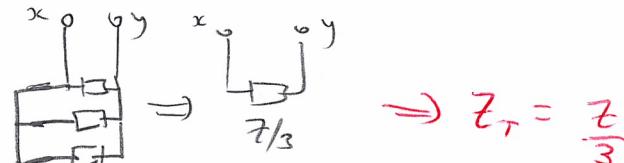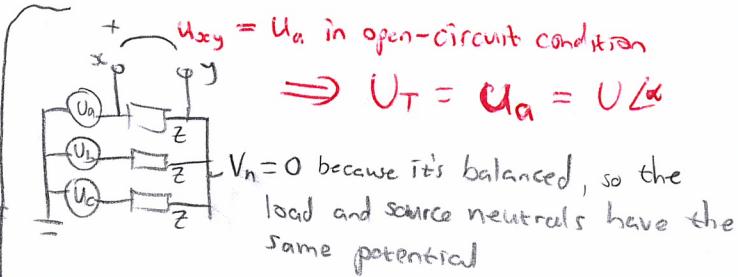Find the
Thevenin
equivalent
of the
balanced part.



So adding the unbalance:
to the balanced Thevenin:

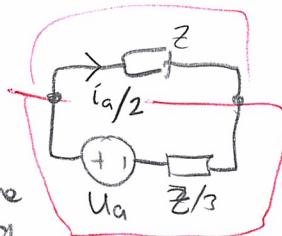Notice that the current in the extra impedance Z is half of the current in the original circuit, as that current is in two parallel impedances Z.




$$\frac{i_a}{2} = \frac{U_a}{Z + Z/3} \quad \therefore i_a = \frac{2U_a}{\frac{4}{3}Z} = \frac{3U_a}{2Z} = \frac{3U}{2Z}$$

$$|i_a| = \frac{3U}{2Z}$$

The first ("direct") method probably looked easier,

But the second method may make it easier to see how a change will affect the solution.

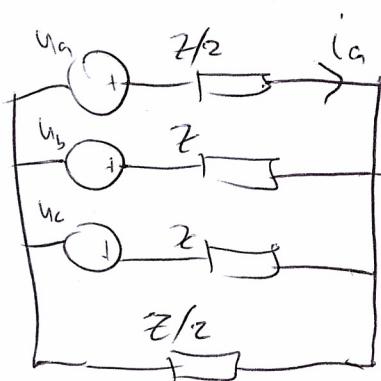E.g. change the question by adding a neutral connection between the source and load star points, with impedance $Z/2$.



By the "Thevenin + balanced-system" method, we see easily that U_T is unchanged and Z_T becomes $Z/5$ instead of $Z/3$. as the neutral adds in parallel.

$$\text{So } i_a = \frac{2U_a}{\frac{6}{5}Z} = \frac{10U_a}{6Z}$$