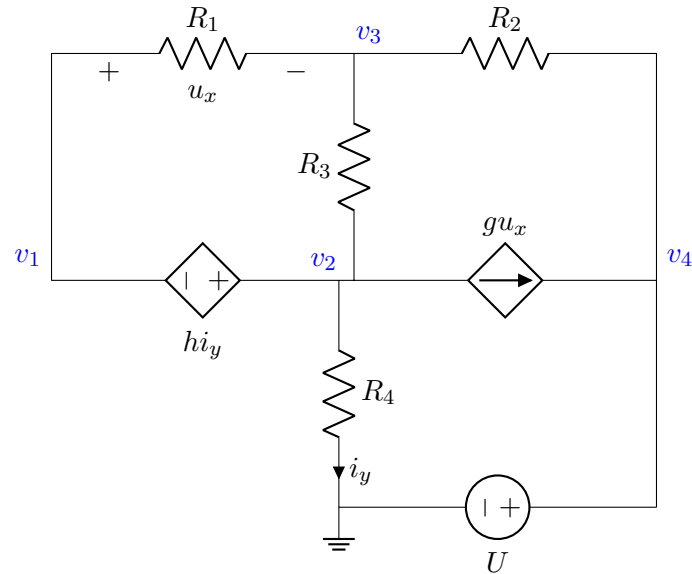


These were in fact old exam questions, from

2014-02_EM_ks1.pdf Question 3 and 2016-03_EM_tenta.pdf Question 2

1.



We'll number the nodes 0 (earth), 1 (left), 2 (centre), 3 (top), 4 (right), as shown above. You might have made different choices.

Extended nodal analysis without simplifications

Define the unknown currents in voltage sources U and hi_y as i_α and i_β respectively, into the sources' + poles (passive).

KCL at all nodes except earth:

$$\text{KCL(1): } 0 = \frac{v_1 - v_3}{R_1} - i_\beta \quad (1)$$

$$\text{KCL(2): } 0 = \frac{v_2 - v_0}{R_4} + i_\beta + gu_x + \frac{v_2 - v_3}{R_3} \quad (2)$$

$$\text{KCL(3): } 0 = \frac{v_3 - v_1}{R_1} + \frac{v_3 - v_2}{R_3} + \frac{v_3 - v_4}{R_2} \quad (3)$$

$$\text{KCL(4): } 0 = \frac{v_4 - v_3}{R_2} - gu_x + i_\alpha \quad (4)$$

Now there are 8 unknowns ($v_0 \dots v_4, u_x, i_\alpha, i_\beta$), and 4 equations. If we use the information that one node (v_0) has been defined as a zero-reference (earth), there's a 5th equation:

$$v_0 = 0. \quad (5)$$

Adding KCL at the earth node does *not* provide a useful equation: with N nodes the N th node's KCL is just a linear combination of the KCL equations, so it provides no extra information. Instead, use the information given by the voltage sources:

$$v_2 - v_1 = h i_y \quad (6)$$

$$v_4 - v_0 = v_4 = U \quad (7)$$

Now there are 7 equations, but 9 unknowns because i_y has been introduced. So define the controlling variables of the dependent sources in terms of existing variables – then there are 9 equations and 9 unknowns.

$$u_x = v_1 - v_3 \quad (8)$$

$$i_y = \frac{v_2}{R_4} \quad (9)$$

The systematic way in which this was done is important! There are plenty of ways to write a sufficient set of equations, but we cannot just be confident that “ n unknowns, n equations, therefore it's all ok” is true. The above method of handling $N-1$ nodes, then earth potential and the information given by voltage-sources, then defining controlling variables in terms of known variables, is one way to develop linearly independent equations.

Supernode and Simplifications method (fewer equations, more thinking)

Nodes 0 and 4 become a supernode (an earth supernode); we choose to always use U instead of v_4 in the equations (and 0 instead of v_0).

Nodes 1 and 2 become another supernode; we choose to define unknown potential v_2 , and always write $(1 - h/R_4)v_2$ instead of v_1 .

Node 3 is a further node, with unknown potential v_3 .

We define the dependent current-source's current in terms of our chosen node potentials as $g u_x = g((1 - h/R_4)v_2 - v_3)$.

There are now only two unknown variables: v_2 and v_3 .

Writing KCL at the two non-earth nodes/supernodes,

$$\text{KCL}(1\&2) : 0 = \frac{v_2}{R_4} + \frac{v_2 - v_3}{R_3} + \frac{(1 - h/R_4)v_2 - v_3}{R_1} + g \left(\left(1 - \frac{h}{R_4}\right) v_2 - v_3 \right) \quad (1)$$


$$\text{KCL}(3) : 0 = \frac{v_3 - (1 - h/R_4)v_2}{R_1} + \frac{v_3 - v_2}{R_3} + \frac{v_3 - U}{R_2} \quad (2)$$

To do as the question required, one should also write as equations the earlier statements that would let us define v_1 and v_4 after the above equations are solved for v_2 and v_3 ,

$$v_1 = \left(1 - \frac{h}{R_4}\right) v_2 \quad (3)$$

$$v_4 = U \quad (4)$$

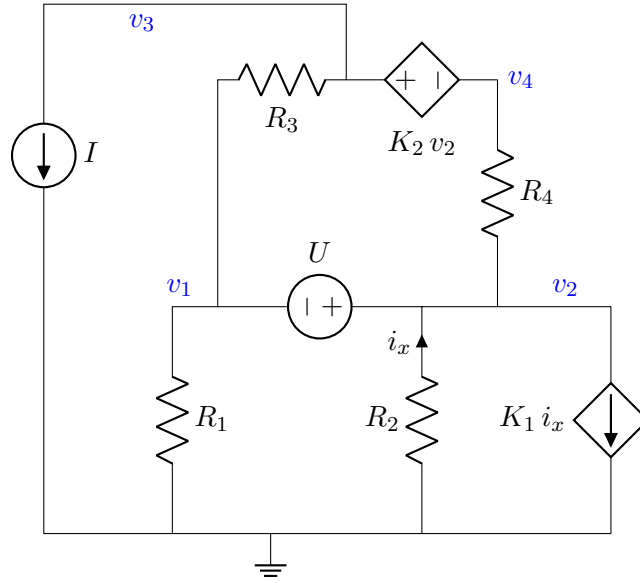2. The nodes in this case are already marked with potentials.



Extended nodal analysis

Let's define the unknown currents in the voltage sources, with the positive direction going into the source's + terminal: i_α in the independent voltage source U , and i_β in the dependent voltage source.

Write KCL (let's take outgoing currents) at all nodes except earth:

$$\text{KCL(1)} : 0 = \frac{v_1}{R_1} + \frac{v_1 - v_3}{R_3} - i_\alpha \quad (1)$$

$$\text{KCL(2)} : 0 = \frac{v_2}{R_2} + \frac{v_2 - v_4}{R_4} + i_\alpha + K_1 i_x \quad (2)$$

$$\text{KCL(3)} : 0 = I + \frac{v_3 - v_1}{R_3} + i_\beta \quad (3)$$

$$\text{KCL(4)} : 0 = \frac{v_4 - v_2}{R_4} - i_\beta. \quad (4)$$

The voltage sources introduced the problem of two extra unknowns in the above equations; they can solve this problem by providing two extra equations without further unknowns:

$$v_2 - v_1 = U \quad (5)$$

$$v_3 - v_4 = K_2 v_2. \quad (6)$$

The controlling variables of the dependent sources need to be defined in terms of the other known or unknown quantities. Our dependent voltage source's controlling variable is the potential v_2 , which is an unknown that we already introduced in the KCL equations: nothing more needs to be done for that. Our dependent current source's controlling variable is a current i_x marked in R_2 . This can be described as

$$i_x = -\frac{v_2}{R_2}. \quad (7)$$

Supernode and Simplifications approach (fewer equations, more thinking)

Identify the supernodes:

Nodes 1 and 2 are joined by source U , so they can be treated as a supernode.

Let's keep potential v_1 in the circuit, and replace v_2 with $v_1 + U$.

Similarly, nodes 3 and 4 are joined by VCVS K_2v_2 .

Let's keep v_4 , and replace v_3 with $v_4 + K_2v_2$.

The only remaining node is the reference node (earth), on which we do not write KCL.

$$\text{KCL}(1\&2) : 0 = \frac{v_1}{R_1} + \frac{v_1 + U}{R_2} - \frac{K_1(v_1 + U)}{R_2} + \frac{v_1 - (v_4 + K_2v_2)}{R_3} + \frac{(v_1 + U) - v_4}{R_4} \quad (1)$$

$$\text{KCL}(3\&4) : 0 = \frac{(v_4 + K_2v_2) - v_1}{R_3} + \frac{v_4 - (v_1 + U)}{R_4} + I \quad (2)$$

In the text above, we mentioned that we'd "replace v_2 with $v_1 + U$ " etc. But we should also ensure this is clearly declared in our equation system — it's essential information to let us find v_2 and v_3 :

$$v_2 = v_1 + U \quad (3)$$

$$v_3 = v_4 + K_2v_2. \quad (4)$$

Together, the above set of 4 equations in the 4 unknown node potentials should be able to give our solution.

3. If you tried question 8 from this Topic's "exercises" file, then see the solution in the same file.