
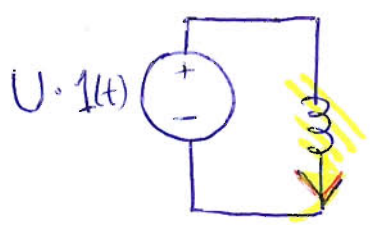


Identify any current or voltage (anywhere in a circuit) that is either changing forever (no equilibrium) or has an impulse (very big pulse, "delta")


(a)

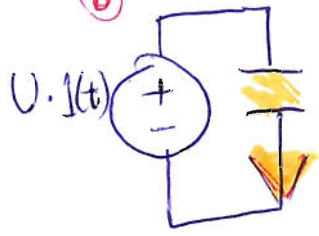



(b)

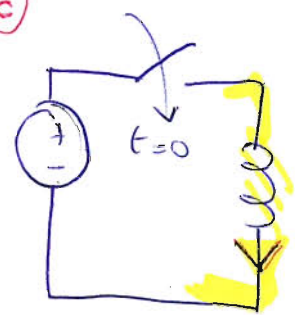


(c)




impulse (at $t=0$) 

continuously changing 

oscillating forever 

(KEY)


(d)

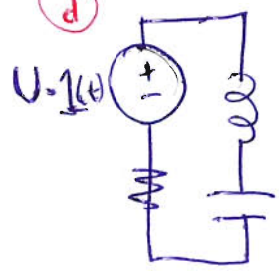


(e) $U \cdot 1(t)$

currents & voltages oscillate


(f)

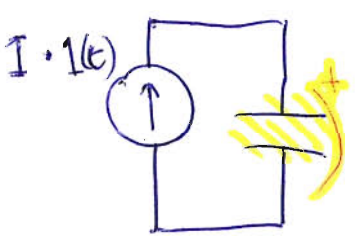


(g)

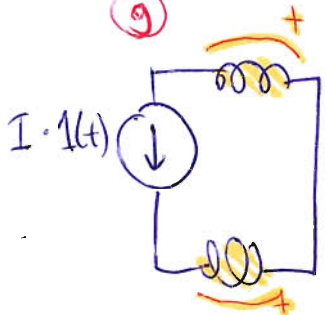

(h)

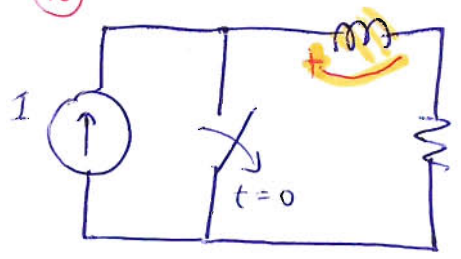


(i)

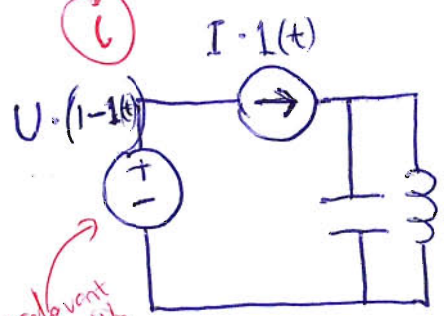


irrelevant (series with I)


(j)

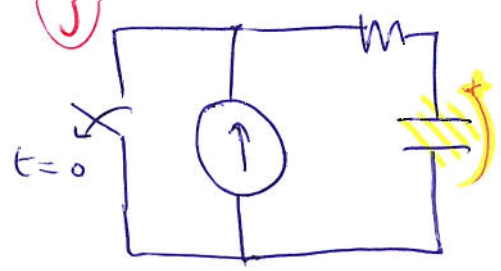


(k)

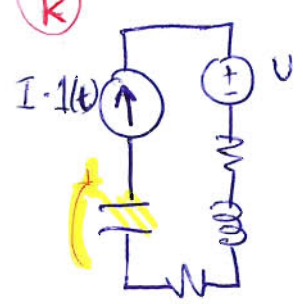


(l)

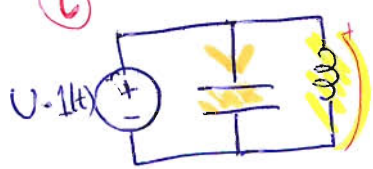

(m)

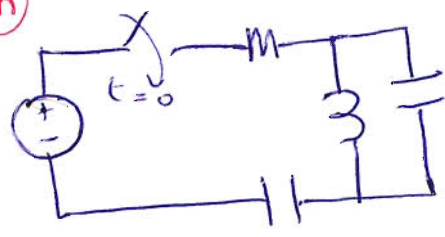

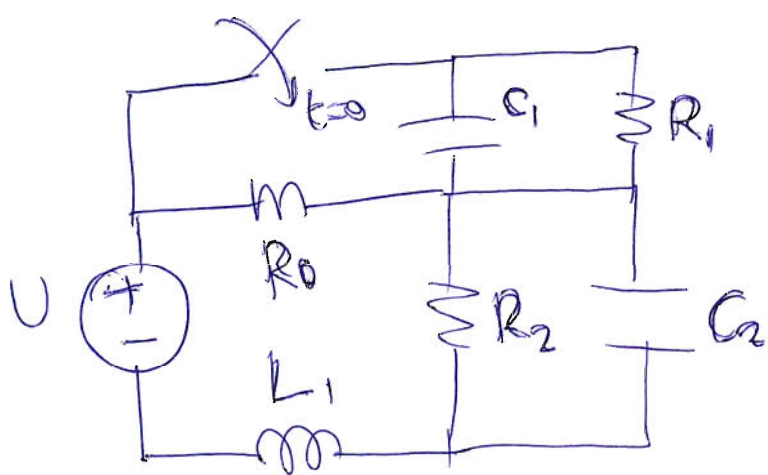
It's just an exercise in thinking about integration, differentiation, and basic circuits (switch, step, LF)



find the power in R_2 at times $t=0^-$
 charge on C_1 at times $t=\infty$

REDRAW!


$t=0^-$

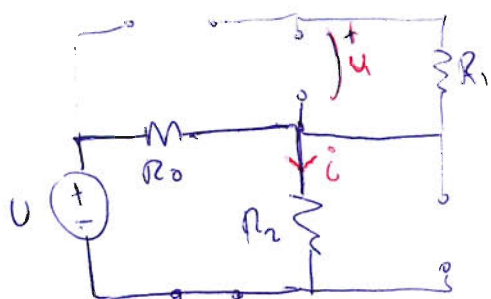

$$i = \frac{U}{R_0 + R_2} \Rightarrow P_{R_2} = i^2 R_2 = \frac{U^2 R_2}{(R_0 + R_2)^2}$$

$$u = 0 \Rightarrow Q_{C_1} = UC_1 = 0$$

$t \Rightarrow \infty$

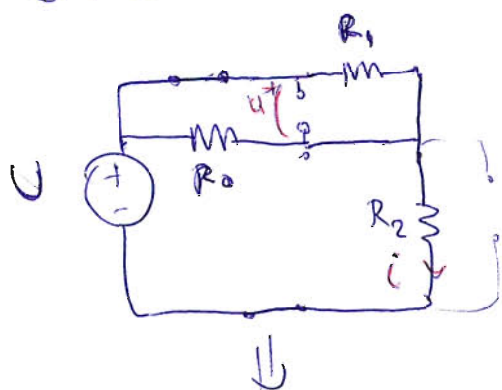


$$i = \frac{U}{R_2 + \frac{R_0 R_1}{R_0 + R_1}} = \frac{U(R_0 + R_1)}{R_0 R_1 + R_0 R_2 + R_1 R_2}$$

$$P_{R_2} = i^2 R_2 = \frac{U^2 R_2 (R_0 + R_1)^2}{(R_0 R_1 + R_0 R_2 + R_1 R_2)^2}$$


$$u = \frac{R_0 R_1}{R_0 + R_1} \cdot i = \frac{U}{1 + \frac{R_2 (R_0 + R_1)}{R_0 R_1}}$$
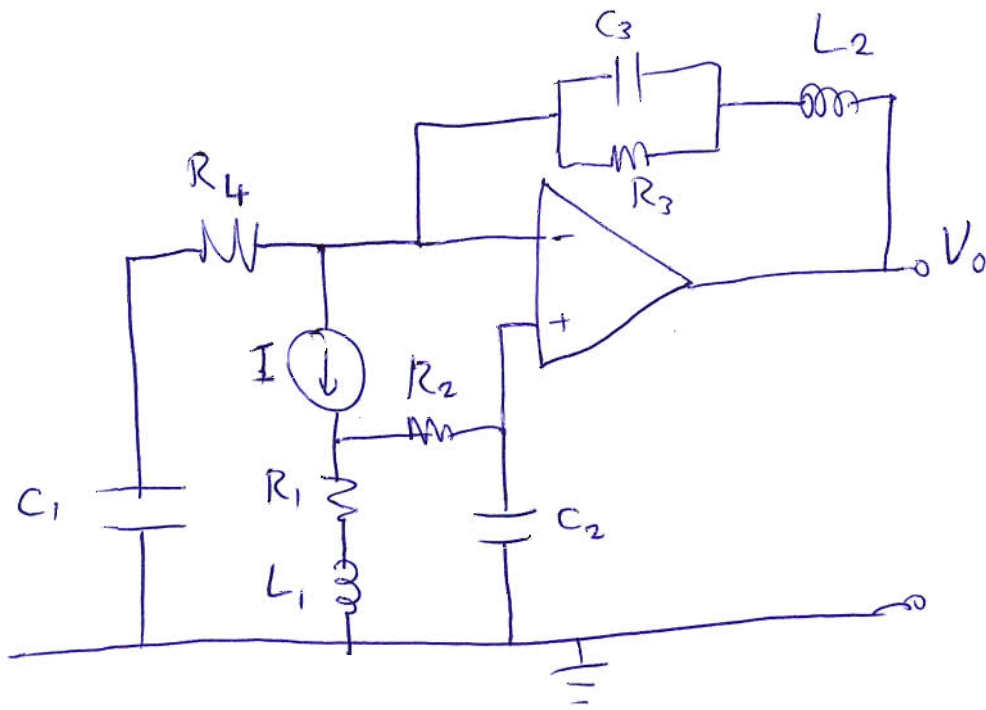
$$Q_{C_1} = UC_1 = \frac{UC_1 R_0 R_1}{R_0 R_1 + R_0 R_2 + R_1 R_2}$$



find the equilibrium value of V_0

RE-DRAW

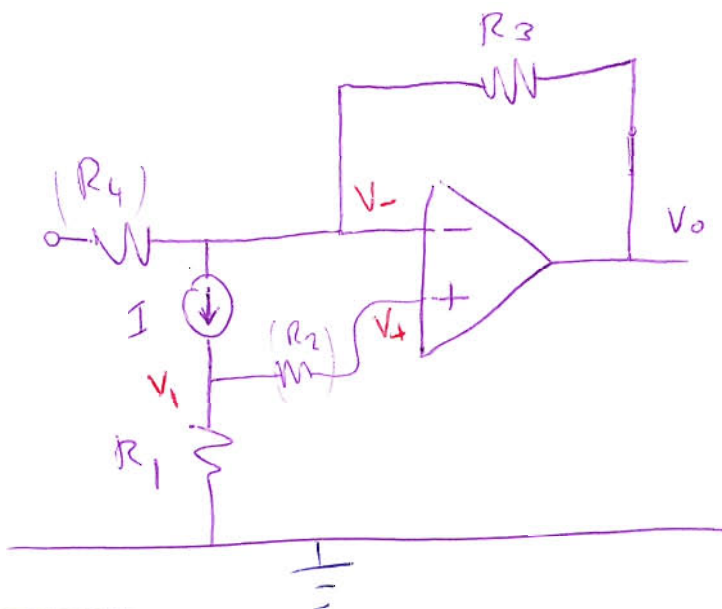

$$V_1 = IR_1 \quad (\text{ohm's law})$$

$$V_+ = V_1 \quad (\text{no current in } R_2, \text{ so no voltage})$$


$$V_- = V_+ \quad (\text{opamp neg. fb.})$$

$$\frac{V_- - V_0}{R_3} + I = 0 \quad (\text{kcl})$$

$$V_0 = V_- + IR_3$$



$$\boxed{V_0 = I(R_1 + R_3)}$$

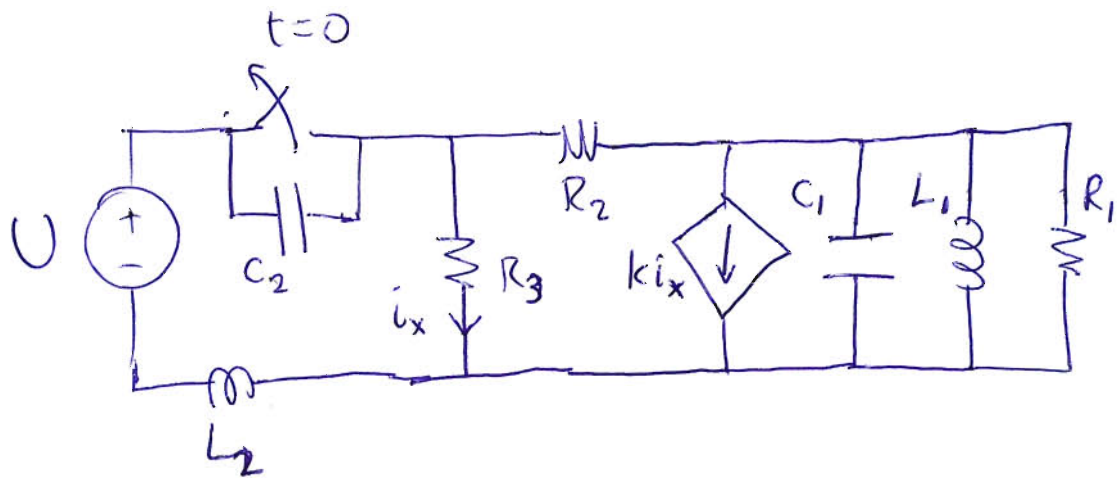Danger! The zero voltage across the current source is because of the opamp! In general, a current source can have nonzero voltage.



find at $\left\{ \begin{array}{l} t=0^- \\ \text{and} \\ t \rightarrow \infty \end{array} \right\}$ the $\left\{ \begin{array}{l} \text{value of } i_x \\ \text{energy in } C_2 \end{array} \right\}$

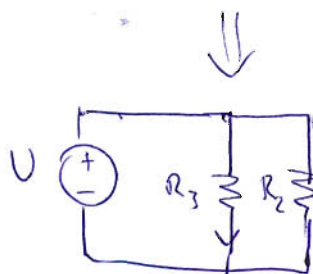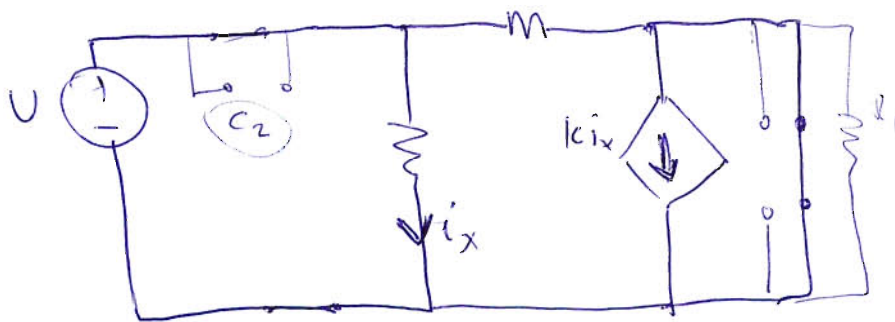$t=0^-$ redraw (with switch closed, and C, L replaced by open/short)



$$i_x = \frac{U}{R_3}$$


from parallel connection to voltage source U.

and energy in C_2 is zero

from short circuit by switch:
 $\frac{1}{2} U^2 C = \frac{1}{2} 0^2 C = 0$

(cont.)

$t \rightarrow \infty$

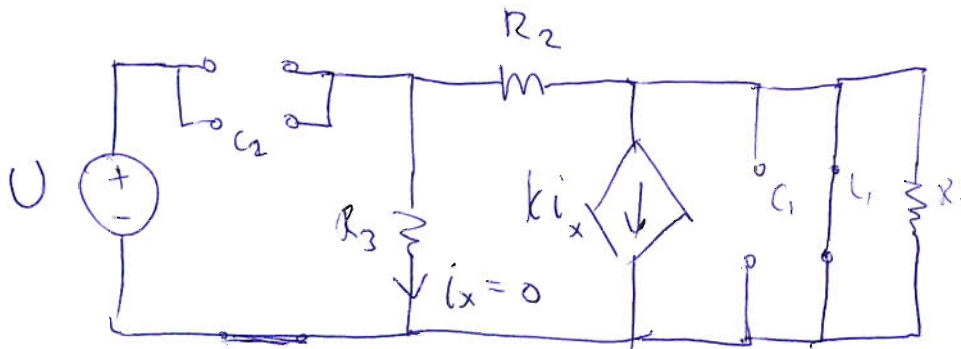

This has two separate parts. The part on the right (everything except U, C_2) has no independent source, (as it only connects to U by one node).

So we assume nothing happens on the right: all voltages and currents are zero, as there is no independent source to stimulate the controlling variable of the dependent source (this is a general principle about independent and dependent sources).

(Alternatively we can take KVL around the loop of L_1, R_2, R_3 to prove $u_{R3} = 0$).

So a voltage U exists across the capacitor C_2 .
Its stored energy is $\frac{1}{2} C_2 U^2$.

And $i_x = 0$