

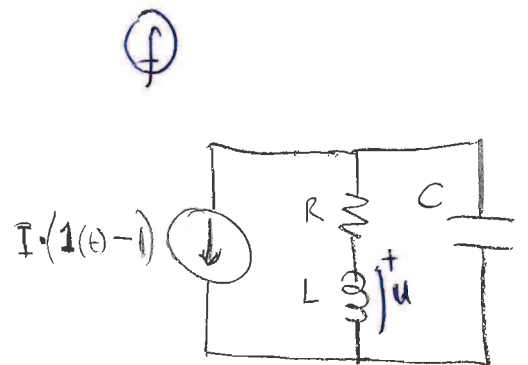
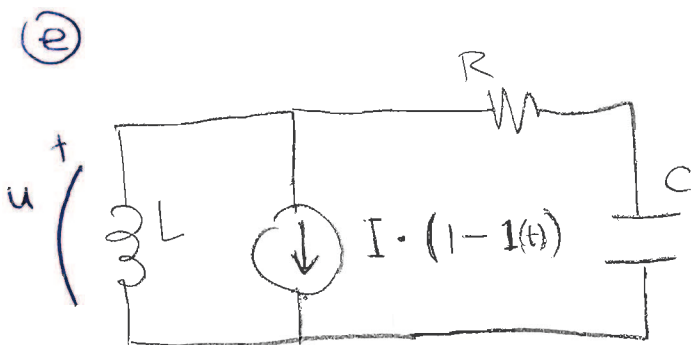
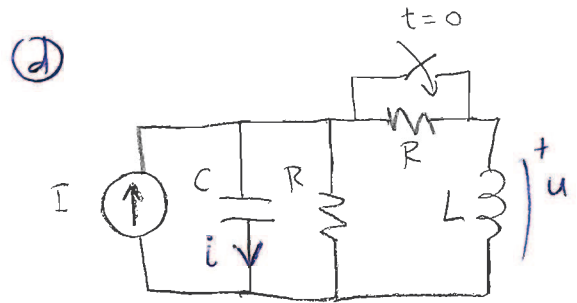
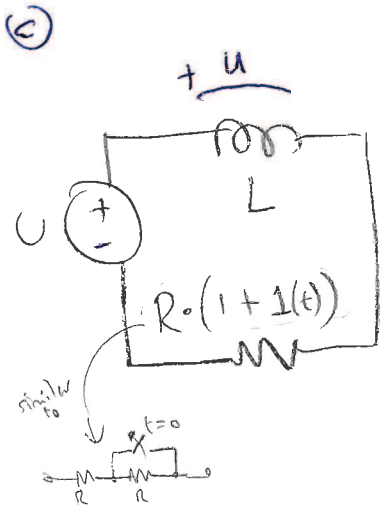
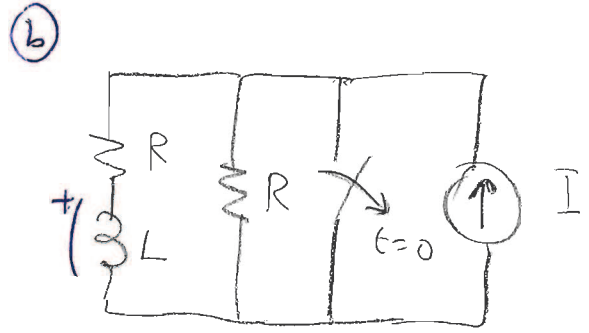


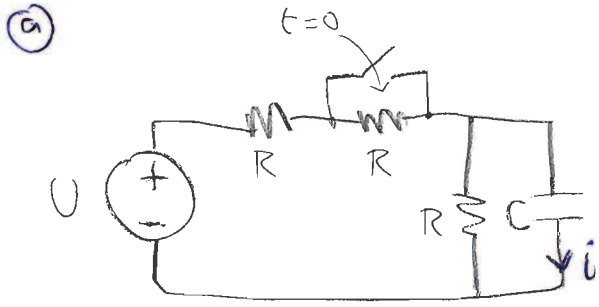Find the marked u and/or i , in these circuits, at $t = 0^+$



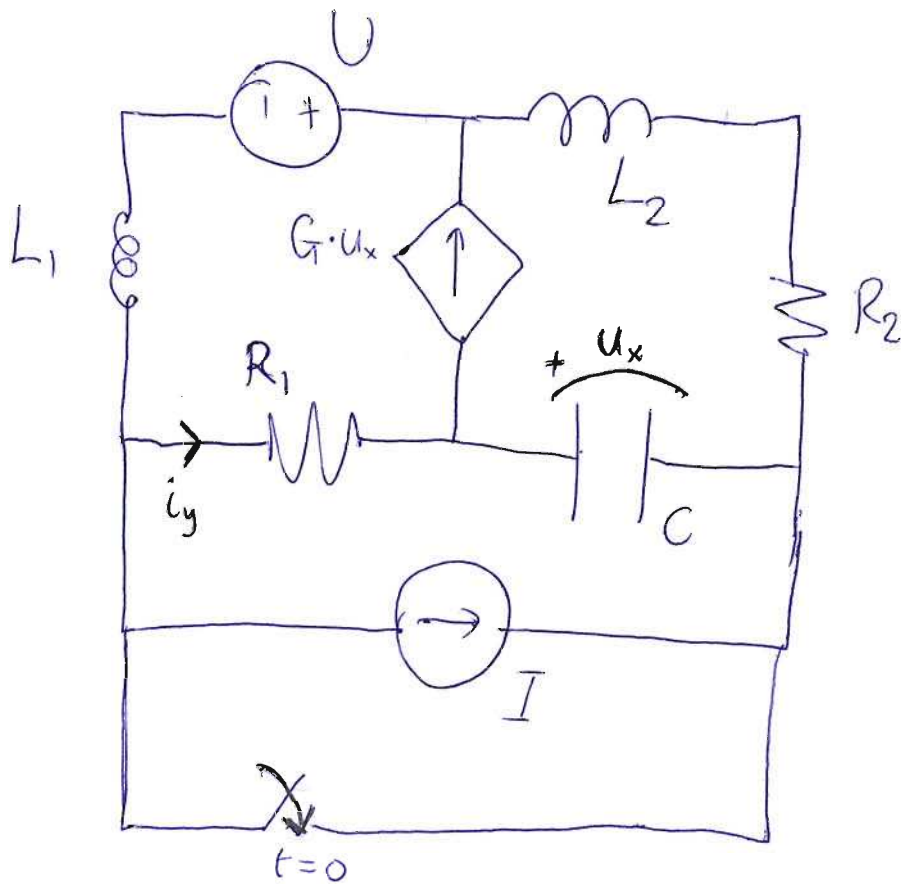

find the usual things!

$$\left. \begin{matrix} u_x \\ i_y \end{matrix} \right\} \text{ at } \begin{cases} t=0^- \\ t=0^+ \end{cases}$$