

Solutions for Tutorial: Continuity

Page 1, first circuit.

$$i(0^+) = i(0^-) = 0$$

a)

Initial value: $i(0^+) = 0$.

Final value: $i(\infty) = U/R_1$.

Time-constant: $\tau = \frac{L(R_1+R_2)}{R_1R_2}$,

based on the Thevenin resistance of the circuit that the inductor 'sees'.

So, for $t > 0$,

$$i(t) = \frac{U}{R_1} + \left(0 - \frac{U}{R_1}\right) \exp\left(\frac{-R_1R_2 t}{L(R_1 + R_2)}\right) = \frac{U}{R_1} \left(1 - \exp\left(\frac{-R_1R_2 t}{L(R_1 + R_2)}\right)\right).$$

b)

Initial value: $u(0^+) = \frac{R_2}{R_1+R_2}U$.

Final value: $u(\infty) = 0$.

Time-constant: $\tau = \frac{L(R_1+R_2)}{R_1R_2}$.

Note that this is the same as above. It will be true for any time-changing quantities in this circuit, as there's only the one continuous variable that's undergoing the time-variation. (Consider that integration or differentiation of $e^{-t/\tau}$ leaves this same term in the result.)

$$u(t) = 0 + \left(\frac{R_2}{R_1 + R_2}U - 0\right) \exp\left(\frac{-R_1R_2 t}{L(R_1 + R_2)}\right) = \frac{UR_2}{R_1 + R_2} \exp\left(\frac{-R_1R_2 t}{L(R_1 + R_2)}\right).$$

c)

Initial value: $i_2(0^+) = \frac{U}{R_1+R_2}$.

This is found by considering that $i(0^+) = 0$, and therefore the right-hand branch can be ignored at $t = 0^+$.

Final value: $i_2(\infty) = 0$.

In this equilibrium, R_2 is 'shorted' by the inductor.

Time-constant: as before (same reason).

$$i_2(t) = \frac{U}{R_1 + R_2} \exp\left(\frac{-R_1R_2 t}{L(R_1 + R_2)}\right).$$

Page 1, second circuit.

$$u(t) = -U + IR_2 e^{\frac{-t}{CR_1}}$$

$$i(t) = \frac{U + u(t)}{R_1} + \frac{U}{R_0} = \frac{U}{R_0} + \frac{R_2}{R_1} I e^{\frac{-t}{CR_1}}.$$

Page 2.

$$i(t) = \frac{U}{R_1 + (1+k)R_2} \left(2e^{-\frac{R_1+(1+k)R_2}{L}t} - 1 \right) \quad (t \geq 0).$$

This question is 2016-03 EM tenta Q5.

See a solution on that link.

Page 3.

$$i_c(t) = \frac{-IR_1}{R_1 + R_2} e^{-\frac{t}{C(R_1+R_2)}} \quad (t \geq 0).$$

This question is 2014-02 EM ks2 Q1.

See a longer solution on that link.